

**Question 1** (10 points)

U mreži sa 6 grana i 4 čvora broj linearno nezavisnih jednažbi struja(KZS) i napona(KZN) je:

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. KZS=5, KZN=5
-50.0%			b. KZN=5, KZS=3
100.0%			c. KZS=3, KZN=3
-50.0%			d. KZN=3, KZS=5
-50.0%			e. ne može se odrediti bez poznavanja topološke strukture mreže

Score: 10 / 10

**Question 2** (10 points)

O čemu ovisi broj linearno nezavisnih jednažbi KZS ?

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. o broju elemenata u granama
-50.0%			b. o broju grana
100.0%			c. o broju čvorova
-50.0%			d. o broju čvorova i grana
-50.0%			e. ništa od navedenog

Score: 10 / 10

**Question 3** (10 points)

Otpor R u grani neke mreže priključen je na čvorove A i B. Čvor B je na većem potencijalu od čvora A, a pretpostavljeni smjer struje kroz granu je od čvora A prema čvoru B. Izraz za opis struje  $I_r$  je:

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. $I_r = (U_b - U_a)/R$
-50.0%			b. $I_r = -(U_b + U_a)/R$
100.0%			c. $I_r = (U_a - U_b)/R$
-50.0%			d. $I_r = (U_b + U_a)/R$

Score: 10 / 10

#### Question 4 (10 points)

Matrica impedancije bit će simetrična ako je mreža

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
50.0%			a. sastavljena od kapaciteta, induktiviteta, otpora i neovisnih izvora
50.0%			b. recipročna
0.0%			c. bez induktiviteta i kapaciteta

Score: 5 / 10

#### Question 5 (10 points)

Postavi jednadžbu prve i druge petlje mreže na slici u Laplace-ovoj domeni.

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
100.0%			a. a)
-50.0%			b. b)
-50.0%			c. c)
-50.0%			d. d)



Score: 10 / 10

Total score: 45 / 50 = 90.0%

### Question 1 (10 points)

Kako glasi matricna impedancija petlji?

Student response:





Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. $Z_m(s) = Z_b(s) * B^T$
-50.0%			b. $Z_m(s) = A * Z_b(s) * A^T$
100.0%			c. $Z_m(s) = B * Z_b(s) * B^T$
-50.0%			d. $Z_m(s) = A * Z_b(s)$

Score: 10 / 10

### Question 2 (10 points)

Koje su tvrdnje ispravne?

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
50.0%			a. Čvorište i grana koja spaja to čvorište incidentni su jedan s drugim.
50.0%			b. Broj koji kaže koliko je grana incidentno s nekim čvorištem, naziva se red čvorišta.
-50.0%			c. Dvije su grane u seriji, ako su incidentne s istim parom čvorišta.

-50.0%			d. Dvije grane su paralelne, ako imaju točno jedno zajedničko čvorište, koje nije incidentno ni s jednom daljnjom granom.
-50.0%			e. Nijedna od navedenih.

Score: 10 / 10

### Question 3 (10 points)

Ako je broj čvorova 4, a broj grana 5, koliko jednadžbi KZS nam je potrebno?

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
100.0%			a. 3 od 4
-50.0%			b. 3 od 5
-50.0%			c. 4 od 5
-50.0%			d. 4 od 4


Score: 10 / 10

### Question 4 (10 points)

Koliko graf ima stablenih grana?

Student response:


Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. 0
-50.0%			b. 1
-50.0%			c. 2
100.0%			d. 3
-50.0%			e. 4

 

Score: 10 / 10

**Question 5** (10 points)

Koliko ima spona u zadanom grafu?

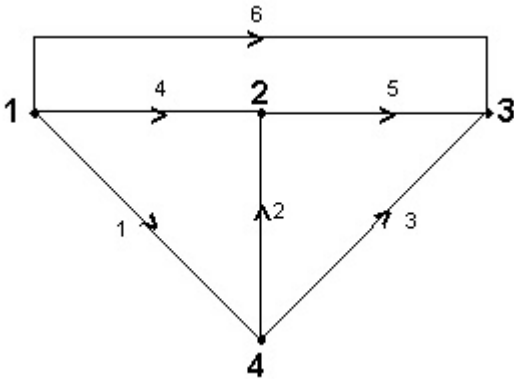

Student response:

Percent Value	Correct Response	Student Response	Answer Choices	
-50.0%			a.	1
-50.0%			b.	2
100.0%	▶	▶	c.	3
-50.0%			d.	4
-50.0%			e.	6



Score: 10 / 10

**Total score:** 50 / 50 = 100.0%

**Question 1** (10 points)

Pretpostavimo li da rješavamo mrežu od  $N_b$  grana i  $N_v$  čvorova. Za točno rješenje mreže dobili bi :

Student response:



Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. $N_v$ napona grana i $N_b$ struja grana
100.0%			b. $N_b$ napona grana i $N_b$ struja grana
-50.0%			c. $N_v$ napona grana i $N_v$ struja grana
-50.0%			d. $N_b$ napona grana i $N_v$ struja grana
-50.0%			e. ništa od navedenog

Score: -5 / 10

**Question 2** (10 points)

Ako nije zadan, kako se odabire referentni čvor korištenjem KZN?

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. na čvoru na kojem je spojena negativna stezaljka naponskog ili strujnog izvora
-50.0%			b. na čvoru u koji ulazi najviše struja
100.0%			c. proizvoljno



-50.0%			d. na čvoru iz kojeg izlazi najviše struja
-50.0%			e. ništa od navedenog

Score: 10 / 10

### Question 3 (10 points)

Koje su od navedenih tvrdnji istinite?

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. Ako postoji više čvorova u nekoj el. mreži, odabirom dva referentna na suprotnim stranama mreže postupak rješavanja KZN se pojednostavljuje.
-50.0%			b. Ako tražimo samo struju jedne grane u el. mreži možemo koristiti samo one linearno nezavisne jednačbe u kojima se pojavljuju konturne struje koja prolaze određenom granom.
100.0%			c. Ako u nekoj grani mreže postoji nezavisni izvor koji daje struju $I_a$ , iznos konturne struje koja obilazi i tu granu je $I_a$ .
-50.0%			d. Da bi odredili napon grane neke el. mreže uvijek oduzimamo napon čvora na većem potencijalu od

			napona čvora na manjem potencijalu.

Score: 10 / 10

#### Question 4 (10 points)

Za mrežu na slici odredi jednadžbe petlji.

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
100.0%			a. $I_1 (R_g + 1/j\omega C) = U_0$ $I_2 (R_k + R_p + R_l) = -U_g$
-50.0%			b. $I_1 (R_g + 1/j\omega C) = U_0 + U_z$ $I_2 (R_k + R_p + R_l) = -U_g$
-50.0%			c. $I_1 (R_g + 1/j\omega C) = U_0$ $I_2 (R_k + R_p + R_l) = -U_g + U_z$
-50.0%			d. $I_1 (R_g + 1/j\omega C) = U_0 + U_z$ $I_2 (R_k + R_p + R_l) = -U_g + U_z$
-50.0%			e. Točan odgovor nije ponuđen.

Score: 10 / 10

#### Question 5 (10 points)

Postavi jednadžbu treće petlje mreže na slici u Laplace-ovoj domeni.

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
100.0%			a. a)
-50.0%			b. b)



-50.0%			c.	c)
-50.0%			d.	d)
-50.0%			e.	e)

Score: 10 / 10

**Total score: 35 / 50 = 70.0%**

KZN u matričnoj normi glasi:

Student response:	Percent Value	Correct Response	Student Response	Answer Choices
	100.0%			a. $U_b(s) = U_g(s) + Z_b(s) * I_b(s) + u_c(0)/s - L_b * i_b(0)$
	-50.0%			b. $U_b(s) = U_g(s) + Z_b(s) * I_b(s)$
	-50.0%			c. $U_b(s) = U_g(s) + Z_b(s) * I_b(s) + u_c(0)/s$
	-50.0%			d. $0 = U_g(s) + Z_b(s) * I_b(s) + u_c(0)/s - L_b * i_b(0)$

Score: -5 / 10

### Question 2 (10 points)

Da li je slijedeća definicija ispravna?

Pod grafom smatramo skup čvorova zajedno sa skupom grana sa takovim svojstvima, da svaka grana završava na svakom kraju sa čvorom.

Student response:	Percent Value	Correct Response	Student Response	Answer Choices
	100.0%			a. točno
	-50.0%			b. netočno

Score: 10 / 10

**Question 3** (10 points)

Pišući KZS za neku mrežu, pišemo sistem linearnih jednažbi za sve čvorove. Što su varijable, a što koeficijenti?

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
100.0%			a. varijable su struje u granama, koeficijenti 1, -1, 0
-50.0%			b. varijable su samo struje u sponama, koeficijenti mogu biti bilo koji brojevi
-50.0%			c. varijable su naponi u čvorovima, koeficijenti mogu biti bilo koji brojevi
-50.0%			d. varijable su struje u granama, koeficijenti mogu biti bilo koji brojevi

Score: 10 / 10

**Question 4** (10 points)

Koliko graf ima spona?


Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. 0
100.0%			b. 1
-50.0%			c. 2
-50.0%			d. 3
-50.0%			e. 4

Score: 10 / 10

**Question 5** (10 points)

Koliko ima spona u zadanom grafu?

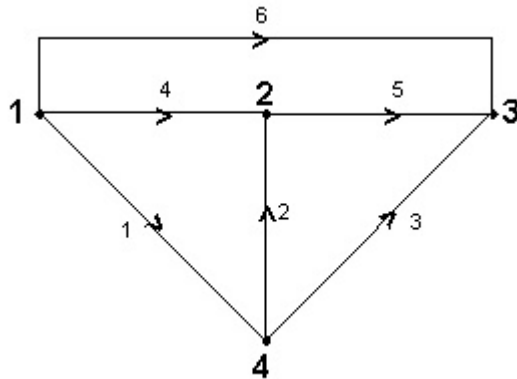

Student response:

Percent Value	Correct Response	Student Response	Answer Choices	
-50.0%			a.	1
-50.0%			b.	2
100.0%	▶	▶	c.	3
-50.0%			d.	4
-50.0%			e.	6

Score: 10 / 10

**Question 1** (10 points)

Koje su nepoznate varijable u jednađzbama stanja?

Student response:

Percent Value	Correct Response	Student Response	Answer Choices	
-50.0%			a.	naponi
-50.0%			b.	struje
100.0%	▶	▶	c.	početni uvjeti
-50.0%			d.	izvori

-50.0%

e. naponi i struje

Score: 10 / 10

### Question 2 (10 points)

Da li prilikom rješavanja mreže uzimamo u obzir zavisne izvore?

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. ne, njih naknadno uvrštavamo
-50.0%			b. ako postoje zavisni strujni izvori, tada mrežu ne možemo riješiti pomoću KZN ili KZS
-50.0%			c. samo ako mrežu rješavamo korištenjem KZN
-50.0%			d. samo ako mrežu rješavamo korištenjem KZS
100.0%			e. da, opisujemo ih pomoću parametara o kojima ovise

Score: 10 / 10

### Question 3 (10 points)

Od koliko se grana sastoji mreža od 4 čvora, ako smo analizirajući mrežu dobili 3 linearno nezavisne jednačbe napona ?

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
100.0%			a. 6
-50.0%			b. 4
-50.0%			c. 2


-50.0%			d. ne možemo odrediti bez poznavanja broja linearno nezavisnih jednažbi napona
--------	--	--	--

Score: 10 / 10

#### Question 4 (10 points)

Odredi struju  $i(t)$  za  $t < 0$  ako je:  $R=C=2$   $U_o(t) = 2 \sin(2t)$  za  $t < 0$   $U_o(t) = 2$  za  $t > 0$


Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. $2t - e^{2t}$
-50.0%			b. $0.64 \cos 2t$
-50.0%			c. $t^2 - 2t$
100.0%			d. $0.98 \sin(2t - 7^\circ)$

Score: 0 / 10 (Question not answered.)
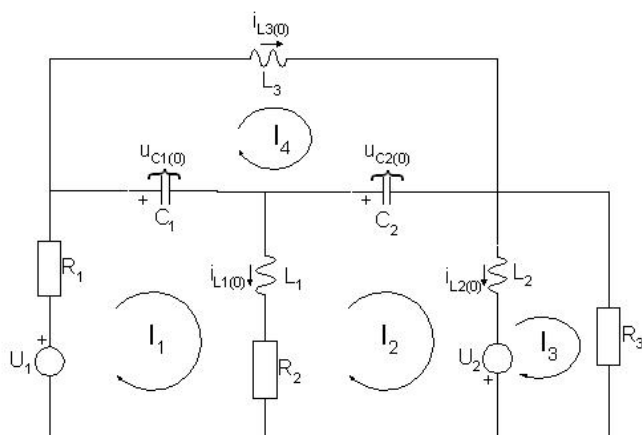
#### Question 5 (10 points)

Postavi jednažbu četvrte petlje mreže na slici.



- a)  $\frac{1}{C_1} \int_{-\infty}^t [i_4(\tau) - i_1(\tau)] d\tau + L_3 \frac{di_4}{dt} + \frac{1}{C_2} \int_{-\infty}^t [i_4(\tau) - i_2(\tau)] d\tau = 0$
- b)  $\frac{1}{C_1} \int_{-\infty}^t [i_4(\tau) - i_1(\tau)] d\tau + L_3 \frac{di_4}{dt} + \frac{1}{C_2} \int_{-\infty}^t [i_4(\tau) - i_1(\tau)] d\tau = 0$
- c)  $-\frac{1}{C_1} \int_{-\infty}^t [i_4(\tau) - i_1(\tau)] d\tau + L_3 \frac{di_4}{dt} - \frac{1}{C_2} \int_{-\infty}^t [i_4(\tau) - i_2(\tau)] d\tau = 0$
- d)  $\frac{1}{C_2} \int_{-\infty}^t [i_4(\tau) - i_1(\tau)] d\tau + L_3 \frac{di_4}{dt} + \frac{1}{C_2} \int_{-\infty}^t [i_4(\tau) - i_2(\tau)] d\tau = 0$

Student response:

Percent Value	Correct Response	Student Response	Answer Choices	
100.0%	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	a.	a)
-50.0%	<input type="checkbox"/>	<input type="checkbox"/>	b.	b)
-50.0%	<input type="checkbox"/>	<input type="checkbox"/>	c.	c)
-50.0%	<input type="checkbox"/>	<input type="checkbox"/>	d.	d)

Score: 10 / 10

Total score: 40 / 50 = 80.0%

### Question 1 (10 points)

Kojom relacijom smo preslikali napone grana u napone čvorova?

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%	<input type="checkbox"/>	<input type="checkbox"/>	a. $i_b(t) = B^T * i_m(t)$
100.0%	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	b. $u_b(t) = A^T * u_n(t)$

-50.0%

c.  $B * ub(t) = 0$

-50.0%



d.  $A * ib(t) = 0$

Score: 10 / 10

### Question 2 (10 points)

Koliki je broj temeljnih petlji, ako je Nb ukupni broj grana, a Nv broj čvorova?

Student response:



Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. $Nb -(Nv + 1)$
100.0%			b. $Nb -(Nv - 1)$
-50.0%			c. $Nb +(Nv + 1)$

Score: 10 / 10

### Question 3 (10 points)

Osnovni tip algebarskih jednažbi mreža u matricnoj formi je:

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. samo opće jednažbe petlji
-50.0%			b. samo opće jednažbe čvorova
100.0%			c. opće jednažbe petlji i čvorova
-50.0%			d. ne postoji osnovni tip

Score: 10 / 10

### Question 4 (10 points)

Koliko ima stablenih grana u zadanom grafu?

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. 1
-50.0%			b. 2
-50.0%			c. 3
100.0%			d. 5
-50.0%			e. 7

Score: 10 / 10

### Question 5 (10 points)

Kako glasi spojna matrica za zadani graf? (2,5,6 su spone)

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
25.0%			a. $\begin{bmatrix} 1 & 1 & 0 & -1 & 0 & 0 \\ -1 & 0 & -1 & 1 & 1 & 0 \\ -1 & 0 & -1 & 0 & 0 & 1 \end{bmatrix}$
25.0%			b. $\begin{bmatrix} -1 & -1 & 0 & 1 & 0 & 0 \\ -1 & 0 & -1 & 1 & 1 & 0 \\ -1 & 0 & -1 & 0 & 0 & 1 \end{bmatrix}$
25.0%			c. $\begin{bmatrix} 1 & 1 & 0 & -1 & 0 & 0 \\ 1 & 0 & 1 & -1 & -1 & 0 \\ 1 & 0 & 1 & 0 & 0 & -1 \end{bmatrix}$
25.0%			d. $\begin{bmatrix} 1 & 1 & 0 & -1 & 0 & 0 \\ -1 & 0 & -1 & 1 & 1 & 0 \\ 1 & 0 & 1 & 0 & 0 & -1 \end{bmatrix}$
-50.0%			e. $\begin{bmatrix} -1 & -1 & 0 & 1 & 0 & 0 \\ 1 & 0 & 1 & 1 & -1 & 0 \\ -1 & 0 & 1 & 0 & 0 & -1 \end{bmatrix}$

Score: 2.5 / 10



Total score: 42.5 / 50 = 85.0%

**Question 1** (10 points)

Da bi riješili mrežu, koji od navedenih uvjeta nam nije potreban ?

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
100.0%			a. poznavanje KZN
-50.0%			b. topološka konfiguracija mreže
-50.0%			c. eventualno postojanje ili nepostojanje početnih stanja mreže
-50.0%			d. izvori
-50.0%			e. vrsta i parametri elemenata u mreži

Score: -5 / 10

**Question 2** (10 points)

Koje su nepoznate varijable u jednadžbama čvorova?

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
100.0%			a. naponi
-50.0%			b. struje
-50.0%			c. početni uvjeti
-50.0%			d. izvori
-50.0%			e. naponi i struje



Score: 10 / 10

**Question 3** (10 points)

Koje su od navedenih tvrdnji istinite?

Student response:

Percent	Correct	Student	Answer Choices
---------	---------	---------	----------------

Value	Response	Response	
-50.0%			a. Ako postoji više čvorova u nekoj el. mreži, odabirom dva referentna na suprotnim stranama mreže postupak rješavanja KZN se pojednostavljuje.
-50.0%			b. Ako tražimo samo struju jedne grane u el. mreži možemo koristiti samo one linearno nezavisne jednačbe u kojima se pojavljuju konturne struje koja prolaze određenom granom.
100.0%			c. Ako u nekoj grani mreže postoji nezavisni izvor koji daje struju $I_a$ , iznos konturne struje koja obilazi i tu granu je $I_a$ .
-50.0%			d. Da bi odredili napon grane neke el. mreže uvijek oduzimamo napon čvora na većem potencijalu od napona čvora na manjem potencijalu.

Score: 10 / 10

#### Question 4 (10 points)

Iz slike slijedi ...

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
50.0%			a. napon grane 1 = - napon čvora 1
-50.0%			b. napon grane 2 = napon čvora 1 + napon čvora 3
50.0%			c. napon grane 4 = napon čvora 2 - napon čvora 3
-50.0%			d. svi odgovori su točni !

Score: 5 / 10

### Question 5 (10 points)

Za mrežu na slici vrijedi

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. $uv3/R4 - C5 \frac{d(uv4 - uv3)}{dt} - (uv3 - uv4)/R6 = 0$
100.0%			b. $uv3/R4 - C5 \frac{d(uv4 - uv3)}{dt} - (uv4 - uv3)/R6 = 0$
-50.0%			c. $uv3/R4 - C5 \frac{d(uv3 - uv4)}{dt} - (uv4 - uv3)/R6 = 0$
-50.0%			d. $uv3/R4 - C5 \frac{d(uv3 - uv4)}{dt} - (uv3 - uv4)/R6 = 0$

Score: 10 / 10

**Total score:** 30 / 50 = 60.0%

[View Results](#)

**Osnovi topološke analize električnih mreža.**

**User ID:** iflis

**Attempt:** 1 / 1

**Out of:** 50



**Started:** April 8, 2004 11:26 **Finished:** April 8, 2004 11:30 **Time spent:** 3 min. 49 sec.

Student finished 6 min. 11 sec. ahead of the 10 min. time limit.

**Question 1** (10 points)

Matrična jednadžba KZN glasi:

Student response:



Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. $A \cdot i_b(t) = 0$
100.0%			b. $B \cdot u_b(t) = 0$
-50.0%			c. $A \cdot u_b(t) = 0$
-50.0%			d. $B \cdot i_b(t) = 0$

Score: 10 / 10

**Question 2** (10 points)

Usmjerenost je čvrsto svojstvo grafa, a vrh strelice smatra se:

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
100.0%			a. smjerom strujne referencije
-50.0%			b. plusom naponske referencije

Score: 10 / 10

**Question 3** (10 points)

Matrična jednačba KZS glasi:

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
100.0%			a. $A * ib(t) = 0$
-50.0%			b. $B * ub(t) = 0$
-50.0%			c. $A * ub(t) = 0$
-50.0%			d. $B * ib(t) = 0$

Score: 10 / 10

**Question 4** (10 points)

Koliko graf ima stablenih grana?

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. 0
-50.0%			b. 1
-50.0%			c. 2
100.0%			d. 3
-50.0%			e. 4

Score: 10 / 10

**Question 5** (10 points)

Zadana je reducirana matrica incidencije grafa.

```




1  1  0  0  0  0  1
-1 -1  1  0  0  0  0
0  0 -1  0  1  0  0
0  0  0 -1 -1 -1  0

```

Da li grane 1,3,5,6 sacinjavaju stablo?

Student response:

Percent	Correct	Student	Answer Choices
---------	---------	---------	----------------

Value	Response	Response	
50.0%			a. Da
-50.0%			b. Ne
50.0%			c. Da, jer je njihova determinanta submatrice razlicita od nule
-50.0%			d. Ne, jer je njihova determinanta submatrice jednaka nuli

Score: -5 / 10

---

**Total score:** 35 / 50 = 70.0%

**View Results**

### Jednadžbe mreža.

User ID: mlojina

Attempt: 1 / 1

Out of: 50

Started: April 8, 2004 11:45

Finished: April 8, 2004 11:53



Time spent: 8 min. 48 sec.

Student finished 1 min. 12 sec. ahead of the 10 min. time limit.

### Question 1 (10 points)

Koliko iznosi broj linearno nezavisnih jednadžbi napona u mreži sa 5 čvorova?

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. 4
-50.0%			b. 5
100.0%			c. ne može se odrediti bez poznavanja broja

			grana u mreži
-50.0%			d. 3
-50.0%			e. ne može se odrediti bez poznavanja topološke strukture mreže

Score: 10 / 10

### Question 2 (10 points)

Koliko iznosi najveći broj linearno nezavisnih jednažbi KZS za mrežu od  $N_b$  grana i  $N_v$  čvorova?

Student response:	Percent Value	Correct Response	Student Response	Answer Choices
	-50.0%			a. $N_b - (N_v + 1)$
	-50.0%			b. $N_b - N_v$
	100.0%			c. $N_v - 1$
	-50.0%			d. $N_b - (N_v - 1)$
	-50.0%			e. $N_v - (N_b - 1)$

Score: 10 / 10

### Question 3 (10 points)

Jednažbe stanja koristimo u analizi nekih električnih mreža da bi:

Student response:	Percent Value	Correct Response	Student Response	Answer Choices
	-50.0%			a. odredili izraze za struje i napone
	100.0%			b. odredili izraze za početne uvjete
	-50.0%			c. odredili iznose početnih struja i napona na L i C
	-50.0%			d. odredili linearnost odnosno nelinearnost

			mreže

Score: 10 / 10

**Question 4** (10 points)

Za mrežu zadanu slikom vrijedi:

Student response:	<b>Percent Value</b>	<b>Correct Response</b>	<b>Student Response</b>	<b>Answer Choices</b>
	50.0%			a. $-(uv1(s)-uv3(s))/R3 - (uv2(s)-uv3(s))/R4 + uv3(s)/R6 = 0$
	-50.0%			b. $-(uv1(s)-uv3(s))/R3 - (uv2(s)-uv3(s))/R4 - uv3(s)/R6 = 0$
	-50.0%			c. $(uv1(s)-uv3(s))/R3 - (uv2(s)-uv3(s))/R4 - uv3(s)/R6 = 0$
	50.0%			d. $-(uv1-uv3)/R3 - (uv2-uv3)/R4 + uv3/R6 = 0$

Score: 5 / 10

**Question 5** (10 points)

Postavi jednađžbu prve i druge petlje mreže na slici.

Student response:	<b>Percent Value</b>	<b>Correct Response</b>	<b>Student Response</b>	<b>Answer Choices</b>
	100.0%			a. a)
	-50.0%			b. b)
	-50.0%			c. c)





-50.0%			d.	d)
--------	--	--	----	----

Score: 10 / 10

**Total score:** 45 / 50 = 90.0%

Korištenjem KZS u rješavanju neke mreže tražimo struju u jednoj od grana te mreže. Kako utječe promjena smjera konturnih struja (koje obilaze granu tražene struje) na iznos i smjer tražene struje?

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. iznos ostaje isti, a smjer se mijenja
100.0%			b. iznos i smjer ostaju isti
-50.0%			c. iznos postaje negativan, a smjer ostaje isti
-50.0%			d. iznos postaje negativan, a smjer suprotan onom prije
-50.0%			e. ne možemo odrediti bez poznavanja ostalih parametara mreže

Score: -5 / 10

### Question 2 (10 points)

Koliko iznosi najveći broj linearno nezavisnih jednažbi KZS za mrežu od  $N_b$  grana i  $N_v$  čvorova?

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. $N_b - (N_v + 1)$

-50.0%			b. $N_b - N_v$
100.0%	▶	▶	c. $N_v - 1$
-50.0%			d. $N_b - (N_v - 1)$
-50.0%			e. $N_v - (N_b - 1)$

Score: 10 / 10

### Question 3 (10 points)

Koje su od navedenih tvrdnji istinite ?

Student response:




Percent Value	Correct Response	Student Response	Answer Choices
-50.0%		▶	a. Prilikom rješavanja mreža KZN moramo sve izvore pretvoriti u naponske
-50.0%		▶	b. Prilikom rješavanja mreža KZS moramo sve izvore pretvoriti u strujne
100.0%	▶		c. Ako postoje i strujni i naponski izvori u mreži ne moramo ih pretvarati jer se ona može riješiti i KZN i KZS
-50.0%			d. Ako pretvaramo izvore u el. mreži svi moraju biti istog tipa, dakle svi naponski ili svi strujni

Score: -10 / 10

### Question 4 (10 points)

Iz slike slijedi...

Student response:

 

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. $i_4 = (u_2 - u_3)/R_4$
-50.0%			b. $i_1 = (u_g + u_1)/R_1$
-50.0%			c. $i_1 = (u_g - u_1)/R_1$
-50.0%			d. $i_5 = C_5 du_5/dt$
100.0%			e. svi odgovori su točni

Score: -10 / 10

### Question 5 (10 points)

Postavi jednažbu prve i druge petlje mreže na slici u Laplace-ovoj domeni.

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
100.0%			a. a)
-50.0%			b. b)
-50.0%			c. c)
-50.0%			d. d)

Score: 10 / 10

---

**Total score:** -5 / 50 = -10.0%

---

**View Results**

**Jednažbe mreža.**

User ID: eplecko

Attempt: 1 / 1

Out of: 50



Started: April 8, 2004 12:14 Finished: April 8, 2004 12:20 Time spent: 6 min. 7 sec.

Student finished 3 min. 53 sec. ahead of the 10 min. time limit.

### Question 1 (10 points)

Pretpostavimo li da rješavamo mrežu od Nb grana i Nv čvorova. Za točno rješenje mreže dobili bi :

Student response:



Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. Nv napona grana i Nb struja grana
100.0%			b. Nb napona grana i Nb struja grana
-50.0%			c. Nv napona grana i Nv struja grana
-50.0%			d. Nb napona grana i Nv struja grana
-50.0%			e. ništa od navedenog

Score: 10 / 10

### Question 2 (10 points)

Koliko iznosi najveći broj linearno nezavisnih jednadžbi KZS za mrežu od Nb grana i Nv čvorova?



Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. $Nb - (Nv + 1)$
-50.0%			b. $Nb - Nv$
100.0%			c. $Nv - 1$
-50.0%			d. $Nb - (Nv - 1)$
-50.0%			e. $Nv - (Nb - 1)$

Score: 10 / 10

### Question 3 (10 points)


Jednadžbe stanja koristimo u analizi nekih električnih mreža da bi:

Student response:	Percent Value	Correct Response	Student Response	Answer Choices
	-50.0%			a. odredili izraze za struje i napone
	100.0%			b. odredili izraze za početne uvjete
	-50.0%			c. odredili iznose početnih struja i napona na L i C
	-50.0%			d. odredili linearnost odnosno nelinearnost mreže

Score: 10 / 10

### Question 4 (10 points)

Za mrežu na slici vrijedi

Student response:	Percent Value	Correct Response	Student Response	Answer Choices
	-50.0%			a. $(uv4(s)-uv1(s))/R3 + iL3(0)/s + sC5(uv4(s)-uv3(s)) - C5(uv4(0)-uv3(0)) + (uv4(s)-uv3(s))/R6 = 0$
	-50.0%			b. $(uv4(s)-uv1(s))/R3 + C5(uv4(s)-uv3(s)) - sC5(uv4(0)-uv3(0)) + (uv4(s)-uv3(s))/R6 = 0$
	100.0%			c. $uv3(s)/R4 - sC5(uv4(s)-uv3(s)) +$

$$C5(uv4(0)-uv3(0)) - (uv4(s)-uv3(s))/R6 = 0$$


-50.0%

d. niti jedna od navedenih jednađžbi

Score: 0 / 10 (Question not answered.)

### Question 5 (10 points)

Za mrežu zadanu slikom vrijedi:

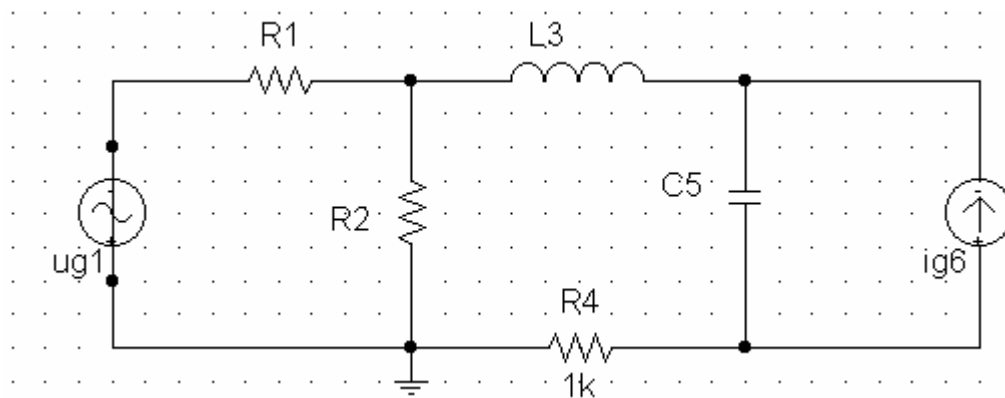

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. $-(uv1(s)+ug1(s))/R1 + uv2(s)/R2 - 1/sL3 (uv4(s)-uv1(s)) - iL3(0)/s = 0$
-50.0%			b. $uv3(s)/R4 - sC5 (uv4(o)-uv3(0)) + C5 (uv4(s)-uv3(s)) + ig6 = 0$
-50.0%			c. $1/sL3 (uv4(s)-uv1(s)) + iL3(0)/s - C5 (uv4(s)-uv3(s)) + sC5 (uv4(0)-uv3(0) - ig6 = 0$
-50.0%			d. sve navedeno
100.0%	▶	▶	e. nista od navedenog



Score: 10 / 10

---

**Total score:** 40 / 50 = 80.0%

---

 

Pretpostavimo li da rješavamo mrežu od Nb grana i Nv čvorova. Za točno rješenje mreže dobili bi :

Student response:	Percent Value	Correct Response	Student Response	Answer Choices
	-50.0%			a. Nv napona grana i Nb struja grana
	100.0%			b. Nb napona grana i Nb struja grana
	-50.0%			c. Nv napona grana i Nv struja grana
	-50.0%			d. Nb napona grana i Nv struja grana
	-50.0%			e. ništa od navedenog

Score: 10 / 10

### Question 2 (10 points)

O čemu ovisi broj linearno nezavisnih jednačbi KZS ?





Student response:	Percent Value	Correct Response	Student Response	Answer Choices
	-50.0%			a. o broju elemenata u granama
	-50.0%			b. o broju grana
	100.0%			c. o broju čvorova
	-50.0%			d. o broju čvorova i grana
	-50.0%			e. ništa od navedenog

Score: 10 / 10

**Question 3** (10 points)

Koje su od navedenih tvrdnji istinite?

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
50.0%			a. Konturne struje su zamišljene struje koje prolaze kroz petlje te njihovim zbrajanjem i oduzimanjem dobijamo prave iznose i smjerove struja u granama
-50.0%			b. Rješavanje mreža pomoću KZN je nešto lakse od rješavanja pomoću KZS
-50.0%			c. Smjerove svih konturnih struja odabiremo uvijek u istom smjeru, tako je najmanja mogućnost pogreške.
-50.0%			d. u mreži sa samo strujnim izvorima isključivo koristimo KZS
50.0%			e. početni uvjeti ponašaju se kao strujni ili naponski izvori u analizi mreže, ovisno o elementu na kojem postoje

Score: 10 / 10



#### Question 4 (10 points)

Koja je matrična jednačba ispravna ?


Student response:

Percent Value	Correct Response	Student Response	Answer Choices
50.0%	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	a. $I_g = Y_v U_v$
50.0%	<input checked="" type="checkbox"/>	<input type="checkbox"/>	b. $Y_v(\text{invertirano}) I_g = U_v$
-50.0%	<input type="checkbox"/>	<input type="checkbox"/>	c. $I_g Y_v(\text{invertirano}) = U_v$
-50.0%	<input type="checkbox"/>	<input type="checkbox"/>	d. $I_g = U_v Y_v$

Score: 5 / 10
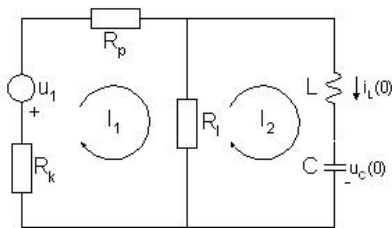
#### Question 5 (10 points)

Kako glase jednačbe petlji za mrežu na slici?



- a)  $I_1(R_p + R_L + R_k) - I_2 R_L = -u_1$   
 $-I_1 R_L + I_2(R_L + sL + \frac{1}{sC}) = -L i_L(0) - \frac{u_C(0)}{s}$
- b)  $I_1(R_p + R_L + R_k) - I_2 R_L = -u_1$   
 $-I_1 R_L + I_2(R_L + sL + \frac{1}{sC}) = -L i_L(0) + \frac{u_C(0)}{s}$
- c)  $I_1(R_p + R_L + R_k) - I_2 R_L = -u_1$   
 $-I_1 R_L + I_2(R_L + sL + \frac{1}{sC}) = L i_L(0) - \frac{u_C(0)}{s}$
- d)  $I_1(R_p + R_L + R_k) - I_2 R_L = -u_1$   
 $-I_1 R_L + I_2(R_L + sL + \frac{1}{sC}) = L i_L(0) + \frac{u_C(0)}{s}$

Student response:



Percent Value	Correct Response	Student Response	Answer Choices
-50.0%	<input type="checkbox"/>	<input type="checkbox"/>	a. a)

-50.0%			b.	b)
100.0%			c.	c)
-50.0%			d.	d)

Score: 10 / 10

Što se podrazumijeva pod pojmom "riješiti električnu mrežu" ?

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. postaviti sve jednadžbe KZN ili KZS
-50.0%			b. odrediti valne oblike svih napona u granama mreže
-50.0%			c. odrediti valne oblike svih konturnih struja i napona čvorova
100.0%			d. odrediti valne oblike svih struja i svih napona u granama mreže
-50.0%			e. odrediti valne oblike svih konturnih struja ili svih napona čvorova

Score: 10 / 10

## Question 2 (10 points)

O čemu ovisi broj linearno nezavisnih jednadžbi KZS ?

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. o broju elemenata u granama

-50.0%			b. o broju grana
100.0%			c. o broju čvorova
-50.0%			d. o broju čvorova i grana
-50.0%			e. ništa od navedenog

Score: 10 / 10

### Question 3 (10 points)

Ako u mreži postoje samo nezavisni i zavisni strujni izvor, što se dešava s potrebnim brojem jednažbi za rješavanje mreže korištenjem KZS?

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. povećava se za broj zavisnih izvora
100.0%			b. smanjuje se za broj nezavisnih izvora
-50.0%			c. povećava se za broj nezavisnih izvora
-50.0%			d. smanjuje se za broj zavisnih strujnih izvora
-50.0%			e. ostaje isti

Score: 0 / 10 (Question not answered.)

### Question 4 (10 points)

Koja je matrična jednažba ispravna ?

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
50.0%			a. $I_g = Y_v U_v$
50.0%			b. $Y_v(\text{invertirano}) I_g = U_v$
-50.0%			c. $I_g Y_v(\text{invertirano}) = U_v$


-50.0%

d.  $I_g = U_v Y_v$

Score: 10 / 10
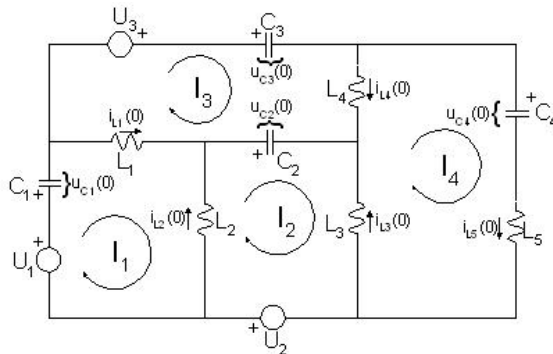
### Question 5 (10 points)

Postavi jednažbu prve petlje mreže na slici u Laplace-ovoj domeni.



- a)  $I_1(s) \left[ \frac{1}{sC_1} + sL_1 + sL_2 \right] - I_3(s)sL_1 - I_2(s)sL_2 = U_1(s) - \frac{U_{C1}(0)}{s} + L_1 i_{L1}(0) - L_2 i_{L2}(0)$
- b)  $I_1(s) \left[ \frac{1}{sC_1} + sL_1 + sL_2 \right] - I_3(s)sL_1 - I_2(s)sL_2 = U_1(s) + \frac{U_{C1}(0)}{s} + L_1 i_{L1}(0) - L_2 i_{L2}(0)$
- c)  $I_1(s) \left[ \frac{1}{sC_1} + sL_1 + sL_2 \right] - I_3(s)sL_1 - I_2(s)sL_2 = U_1(s) - \frac{U_{C1}(0)}{s} + L_1 i_{L1}(0) + L_2 i_{L2}(0)$
- d)  $I_1(s) \left[ \frac{1}{sC_1} + sL_1 + sL_2 \right] - I_3(s)sL_1 - I_2(s)sL_2 = U_1(s) - \frac{U_{C1}(0)}{s} - L_1 i_{L1}(0) - L_2 i_{L2}(0)$
- e)  $I_1(s) \left[ \frac{1}{sC_1} + sL_1 + sL_2 \right] - I_3(s)sL_1 - I_2(s)sL_2 = -U_1(s) - \frac{U_{C1}(0)}{s} + L_1 i_{L1}(0) - L_2 i_{L2}(0)$

Student response:

Percent Value	Correct Response	Student Response	Answer Choices	
100.0%	▶	▶	a.	a)
-50.0%			b.	b)
-50.0%			c.	c)
-50.0%			d.	d)
-50.0%			e.	e)

Score: 10 / 10

Pretpostavimo da analiziramo mrežu koristeći tri konturne struje. Promjenimo li jednoj

od konturnih struja smjer, koliko će linearno nezavisnih jednadžbi promijeniti svoj izraz?

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. 1
-50.0%			b. 2
-50.0%			c. 3
100.0%			d. ne možemo odrediti bez poznavanja topološke strukture mreže i koja konturna struja mijenja smjer

Score: 10 / 10

### Question 2 (10 points)

O čemu ovisi broj linearno nezavisnih jednadžbi KZN ?

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. o broju elemenata u granama
-50.0%			b. o broju grana
100.0%			c. o broju čvorova i grana
-50.0%			d. o broju čvorova
-50.0%			e. ništa od navedenog

Score: -5 / 10

### Question 3 (10 points)

Koje su od navedenih tvrdnji istinite?

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
50.0%			a. Konturne struje su zamišljene struje

koje prolaze kroz  
petlje te njihovim  
zbrajanjem i  
oduzimanjem  
dobijamo prave  
iznose i smjerove  
struja u granama

-50.0%

b. Rješavanje mreža  
pomoću KZN je  
nešto lakše od  
rješavanja pomoću  
KZS

-50.0%

c. Smjerove svih  
konturnih struja  
odabiremo uvijek u  
istom smjeru, tako je  
najmanja mogućnost  
pogreške.

-50.0%

d. u mreži sa samo  
strujnim izvorima  
isključivo koristimo  
KZS

50.0%




e. početni uvjeti  
ponašaju se kao  
strujni ili naponski  
izvori u analizi  
mreže, ovisno o  
elementu na kojem  
postoje

Score: 10 / 10
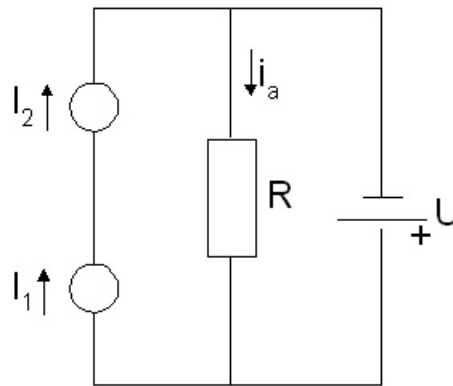
#### Question 4 (10 points)

Metodom jednadžbi petlji odredi struju  $I_a$ . Zadano:  $I_1=5\text{ A}$ ,  $I_2=5\text{ A}$ ,  $U=10\text{ V}$  i  $R=2\ \Omega$ .




Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. $I_a=5$ A
100.0%	▶	▶	b. $I_a=0$ A
-50.0%		Možda	c. $I_a=-5$ A
-50.0%			d. Nemoguće je odrediti, jer nije dozvoljen serijski spoj dva strujna izvora.

Score: 10 / 10
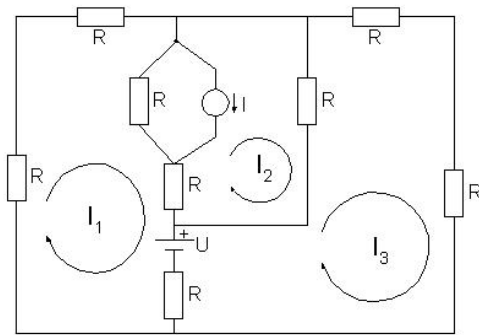
### Question 5 (10 points)

Postavi jednadžbu prve i treće petlje mreže na slici.



- a)  $5RI_1 - 2RI_2 = -U + IR$   
 $-I_1R - I_2R + 4RI_3 = U$
- b)  $5RI_1 - 2RI_2 = U + IR$   
 $-I_1R - I_2R + 4RI_3 = U$
- c)  $5RI_1 - 2RI_2 = -U - IR$   
 $-I_1R - I_2R + 4RI_3 = U$
- d)  $5RI_1 + 2RI_2 = -U + IR$   
 $-I_1R - I_2R + 4RI_3 = U$

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. a)
-50.0%			b. b)
-50.0%			c. c)
-50.0%			d. d)
100.0%			e. nijedno od navedenog

Score: 10 / 10

Opća jednađba petlji u matričnom obliku glasi:

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. $Z_m(s) * I_m(s) = -B * U_g(s) - B * (1/s) * u_c(0)$
100.0%			b. $Z_m(s) * I_m(s) = -B * U_g(s) - B * (1/s) * u_c(0) + B * L_b * i_b(0)$



-50.0%

c.  $Z_m(s) * I_m(s) = -B * U_g(s)$

-50.0%

d.  $Z_m(s) * I_m(s) = 0$

Score: 10 / 10

### Question 2 (10 points)

Usmjerenost je čvrsto svojstvo grafa, a vrh strelice smatra se:

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
100.0%			a. smjerom strujne referencije
-50.0%			b. plusom naponske referencije

Score: 10 / 10

### Question 3 (10 points)

Koje od navedenih naziva nije ime za matrice mreža?


Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. matrica incidencije
-50.0%			b. spojna matrica
100.0%			c. matrica dedukcije
-50.0%			d. rastavna matrica

Score: 10 / 10

### Question 4 (10 points)

Koliko ima spona u zadanom grafu?

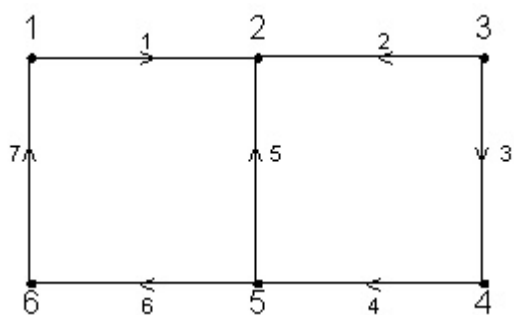


Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. 1
100.0%	▶	▶	b. 2
-50.0%			c. 3
-50.0%			d. 5
-50.0%			e. 7

Score: 10 / 10

### Question 5 (10 points)

Koliko ima temeljnih petlji u grafu?

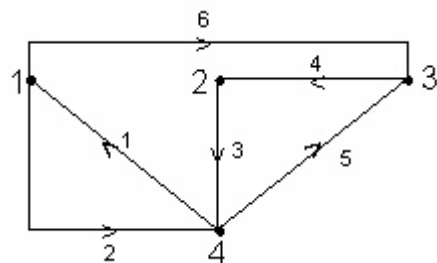

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. 1
-50.0%			b. 2
100.0%	▶	▶	c. 3
-50.0%			d. 4
-50.0%			e. 5

Score: 10 / 10

**Question 1** (10 points)

KZN u matričnoj normi glasi:

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
100.0%			a. $U_b(s) = U_g(s) + Z_b(s) * I_b(s) + u_c(0)/s - L_b * i_b(0)$
-50.0%			b. $U_b(s) = U_g(s) + Z_b(s) * I_b(s)$
-50.0%			c. $U_b(s) = U_g(s) + Z_b(s) * I_b(s) + u_c(0)/s$
-50.0%			d. $0 = U_g(s) + Z_b(s) * I_b(s) + u_c(0)/s - L_b * i_b(0)$

Score: -10 / 10

**Question 2** (10 points)

Ako je  $N_v$  broj čvorova, koliko ima temeljnih rezova?

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
100.0%			a. $N_v - 1$
-50.0%			b. $N_v$
-50.0%			c. $N_v + 1$

Score: 10 / 10

**Question 3** (10 points)

Što od slijedećeg ne može biti KZS za čvor?

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
---------------	------------------	------------------	----------------

-50.0%			a. $i1 + i2 - i3 + 0 + 0 = 0$
-50.0%			b. $-i1 + 0 + 0 + i4 + 0 = 0$
-50.0%			c. $0 - i2 + 0 - i4 - i5 = 0$
100.0%	▶	▶	d. $1 + 0 + 2*i3 + 0 + i5 = 0$

Score: 10 / 10

#### Question 4 (10 points)

Koliko graf ima spona?




Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. 0
100.0%	▶	▶	b. 1
-50.0%			c. 2
-50.0%			d. 3
-50.0%			e. 4

Score: 10 / 10
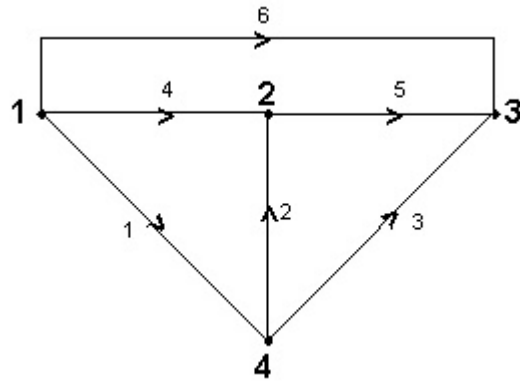
#### Question 5 (10 points)

Koliko ima temeljnih petlji u zadanom grafu?



Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. 1
-50.0%			b. 2
100.0%	▶	▶	c. 3
-50.0%			d. 4
-50.0%			e. 5

Score: 10 / 10

Kako glasi matricna impedancija petlji?

Student response:



Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. $Z_m(s) = Z_b(s) * B^T$
-50.0%			b. $Z_m(s) = A * Z_b(s) * A^T$
100.0%	▶	▶	c. $Z_m(s) = B * Z_b(s) * B^T$
-50.0%			d. $Z_m(s) = A * Z_b(s)$

Score: 10 / 10

Question 2 (10 points)

Može li čvor bez grane biti smatran grafom?

Student response:



Percent Value	Correct Response	Student Response	Answer Choices
100.0%			a. može
-50.0%			b. ne može

Score: 10 / 10

### Question 3 (10 points)

Matrična jednačba KZS glasi:


Student response:

Percent Value	Correct Response	Student Response	Answer Choices
100.0%			a. $A * ib(t) = 0$
-50.0%			b. $B * ub(t) = 0$
-50.0%			c. $A * ub(t) = 0$
-50.0%			d. $B * ib(t) = 0$



Score: 10 / 10

### Question 4 (10 points)

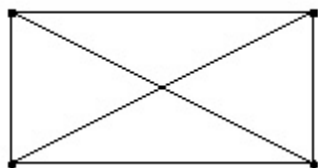Da li je graf planaran?




Student response:

Percent Value	Correct Response	Student Response	Answer Choices
100.0%			a. Da
-50.0%			b. Ne

Score: 10 / 10

**Question 5** (10 points)

Koliko ima spona u zadanom grafu?

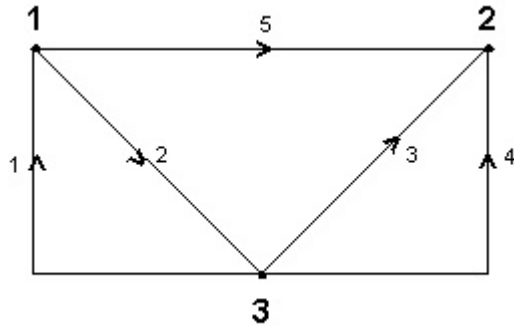

Student response:

Percent Value	Correct Response	Student Response	Answer Choices	
-50.0%			a.	1
-50.0%			b.	2
100.0%	▶	▶	c.	3
-50.0%			d.	4
-50.0%			e.	5

Score: 10 / 10

[View Results](#)

Jednadžbe mreža.

User ID: lalalica Attempt: 1 / 1 Out of: 50

Started: April 6, 2004 23:07 Finished: April 6, 2004 23:17 Time spent: 9 min. 44 sec.

Student finished 0 min. 16 sec. ahead of the 10 min. time limit.

Question 1 (10 points)

Što se podrazumijeva pod pojmom "riješiti elektricnu mrežu" ?

Student response: Percent

Value Correct

Response Student

Response Answer Choices

-50.0% a. postaviti sve jednadžbe KZN ili KZS

-50.0% b. odrediti valne oblike svih napona u granama mreže

-50.0% c. odrediti valne oblike svih konturnih struja i napona cvorova

100.0% d. odrediti valne oblike svih struja i svih napona u granama mreže

-50.0% e. odrediti valne oblike svih konturnih struja ili svih napona cvorova

---

Score: 10 / 10

Question 2 (10 points)

Koliko iznosi najmanji broj linearno nezavisnih jednadžbi KZN za mrežu od Nb grana i Nv cvorova?

Student response: Percent

Value Correct

Response Student

Response Answer Choices

-50.0% a.  $N_b - (N_v + 1)$

-50.0% b.  $N_b - N_v$

-50.0% c.  $N_v - 1$

100.0% d.  $N_b - (N_v - 1)$

-50.0% e.  $N_v - (N_b - 1)$

Score: 10 / 10

Question 3 (10 points)

Koje su od navedenih tvrdnji istinite?

Student response: Percent

Value Correct

Response Student

Response Answer Choices

50.0% a. Konturne struje su zamišljene struje koje prolaze kroz petlje te njihovim zbrajanjem i oduzimanjem dobijamo prave iznose i smjerove struja u granama

-50.0% b. Rješavanje mreža pomoću KZN je nešto lakše od rješavanja pomoću KZS

-50.0% c. Smjerove svih konturnih struja odabiremo uvijek u istom smjeru, tako je najmanja mogućnost pogreške.

-50.0% d. u mreži sa samo strujnim izvorima isključivo koristimo KZS

50.0% e. početni uvjeti ponašaju se kao strujni ili naponski izvori u analizi mreže, ovisno o elementu na kojem postoje

Score: 10 / 10

Question 4 (10 points)

Kako glasi vektor strujnih izvora?

Student response: Percent

Value Correct

Response Student

Response Answer Choices

100.0% a.  $[-i_a \ i_b \ 0 \ -i_b \ i_a]$

-50.0% b.  $[0 \ i_b \ i_a \ -i_b \ -i_a]$

-50.0% c.  $[-i_a \ -i_b \ 0 \ -i_b \ i_a]$

-50.0% d.  $[i_a \ -i_b \ i_b \ i_b \ -i_a]$

Score: 10 / 10

Question 5 (10 points)

Za mrežu sa slike vrijedi:

Student response: Percent

Value Correct

Response Student

Response Answer Choices

-50.0% a. napon grane 2 = -napon grane 1 = -napon cvora 1

50.0% b. napon grane 2 = -napon grane 1 = napon cvora 1

-50.0% c. napon grane 4 = napon grane 5 = -napon cvora 2

50.0% d. napon grane 3 = napon cvora 2 - napon cvora 1



---

Score: -5 / 10

Total score: 35 / 50 = 70.0%

Zadana je mreža koja se sastoji od izvora i tri otpora spojena u paralelu te su postavljene tri linearno nezavisne jednačbe KZS. Promjenom smjera jedne (bilo koje) konturne struje, koliko linearno nezavisnih jednačbi mijenja svoj izraz ?

Student response: Percent

Value Correct

Response Student

Response Answer Choices

-50.0% a. 1

50.0% b. 2

50.0% c. 3

-50.0% d. nijedna

Score: 5 / 10

Question 2 (10 points)

O čemu ovisi broj linearno nezavisnih jednačbi KZN ?

Student response: Percent

Value Correct

Response Student

Response Answer Choices

-50.0% a. o broju elemenata u granama

-50.0% b. o broju grana

100.0% c. o broju cvorova i grana

-50.0% d. o broju cvorova

-50.0% e. ništa od navedenog

Score: 10 / 10

Question 3 (10 points)

Otpor  $R$  u grani neke mreže priključen je na čvorove  $A$  i  $B$ . Čvor  $B$  je na većem potencijalu od čvora  $A$ , a pretpostavljeni smjer struje kroz granu je od čvora  $A$  prema čvoru  $B$ . Izraz za opis struje  $I_r$  je:

Student response: Percent

Value Correct

Response Student

Response Answer Choices

-50.0% a.  $I_r = (U_b - U_a)/R$

-50.0% b.  $I_r = -(U_b + U_a)/R$

100.0% c.  $I_r = (U_a - U_b)/R$

-50.0% d.  $I_r = (U_b + U_a)/R$

Score: 10 / 10

Question 4 (10 points)

Odredi struju  $i(t)$  za  $t < 0$  ako je:  $R = C = 2$   $U_o(t) = 2 \sin(2t)$  za  $t < 0$   $U_o(t) = 2$  za  $t > 0$

Student response: Percent

Value Correct

Response Student

Response Answer Choices

-50.0% a.  $2t - e^{2t}$

-50.0% b.  $0.64 \cos 2t$

-50.0% c.  $t^2 - 2t$

100.0% d.  $0.98 \sin(2t - 7^\circ)$

Score: -5 / 10

Question 5 (10 points)

Postavi jednađbu treće petlje mreže na slici u Laplace-ovoj domeni.

Student response: Percent

Value Correct

Response Student

Response Answer Choices

100.0% a. a)

-50.0% b. b)

-50.0% c. c)

-50.0% d. d)

-50.0% e. e)

Score: -5 / 10

Total score: 15 / 50 = 30.0%

Opća jednađba cvorova u matricnom obliku glasi:

Student response: Percent

Value Correct

Response Student

Response Answer Choices

100.0% a.  $Y_n(s) * U_n(s) = A * Z_b(s)^{-1} * U_g(s) - A * Z_b(s)^{-1} * L_b * i_b(0) + (1/s) * A * Z_b(s)^{-1} * u_c(0)$

-50.0% b.  $Y_n(s) * U_n(s) = A * Z_b(s)^{-1} * U_g(s) - A * Z_b(s)^{-1} * L_b * i_b(0)$

-50.0% c.  $Y_n(s) * U_n(s) = A * Z_b(s)^{-1} * U_g(s)$

-50.0% d.  $0 = A * Z_b(s)^{-1} * U_g(s) - A * Z_b(s)^{-1} * L_b * i_b(0) + (1/s) * A * Z_b(s)^{-1} * u_c(0)$

Score: 10 / 10

Question 2 (10 points)

[View Results](#)

### Jednađbe mreža.

User ID: mboskovic

Attempt: 1 / 1

Out of: 50

Started: April 13, 2004  
13:50

Finished: April 13, 2004  
13:54

Time spent: 4 min. 53  
sec.

Student finished 5 min. 7 sec. ahead of the 10 min. time limit.

### Question 1 (10 points)

U mreži sa 6 grana i 4 čvora broj linearno nezavisnih jednađbi struja(KZS) i napona(KZN) je:

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
---------------	------------------	------------------	----------------

-50.0%			a. KZS=5, KZN=5
-50.0%			b. KZN=5, KZS=3
100.0%	▶	▶	c. KZS=3, KZN=3
-50.0%			d. KZN=3, KZS=5
-50.0%			e. ne može se odrediti bez poznavanja topološke strukture mreže

Score: 10 / 10

### Question 2 (10 points)

O čemu ovisi broj lineararno nezavisnih jednađbi KZN ?

Student response:	Percent Value	Correct Response	Student Response	Answer Choices
	-50.0%			a. o broju elemenata u granama
	-50.0%			b. o broju grana
	100.0%	▶	▶	c. o broju čvorova i grana
	-50.0%			d. o broju čvorova
	-50.0%			e. ništa od navedenog

Score: 10 / 10

### Question 3 (10 points)

Otpor R u grani neke mreže priključen je na čvorove A i B. Čvor B je na većem potencijalu od čvora A, a pretpostavljeni smjer struje kroz granu je od čvora A prema čvoru B. Izraz za opis struje  $I_r$  je:

Student response:	Percent Value	Correct Response	Student Response	Answer Choices
	-50.0%			a. $I_r = (U_b - U_a)/R$
	-50.0%			b. $I_r = -(U_b + U_a)/R$
	100.0%	▶	▶	c. $I_r = (U_a - U_b)/R$
	-50.0%			d. $I_r = (U_b + U_a)/R$

Score: 10 / 10

**Question 4** (10 points)

Kako glase jednađžbe petlji za mrežu na slici?

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
100.0%			a. $I_1 (R_1+R_2) - I_2 * R_2 = u_g(t)$ $-I_1 * R_2 + I_2 (R_2+R_3+R_4+1/j\omega C) -$ $I_3 (R_4+1/j\omega C) = -ig(t) * R_3$ $I_3 (R_4+R_5+j\omega L+1/j\omega C) - I_2 (R_4+1/j\omega C) = 0$
-50.0%			b. $I_1 (R_1+R_2) - I_2 * R_2 = u_g(t)$ $-I_1 * R_2 + I_2 (R_2+R_3+R_4+1/j\omega C) -$ $I_3 (R_4+1/j\omega C) = ig(t) * R_3$ $I_3 (R_4+R_5+j\omega L+1/j\omega C) - I_2 (R_4+1/j\omega C) = 0$
-50.0%			c. $I_1 (R_1+R_2) - I_2 * R_2 = u_g(t)$ $-$ $I_1 * R_2 + I_2 (R_2+R_3+R_4+1/j\omega C) + I_3 (R_4+1/j\omega C) =$ $ig(t) * R_3$ $I_3 (R_4+R_5+j\omega L+1/j\omega C) - I_2 (R_4+1/j\omega C) = 0$
-50.0%			d. $I_1 (R_1+R_2) - I_2 * R_2 = u_g(t)$ $-I_1 * R_2 + I_2 (R_2+R_3+R_4+1/j\omega C) -$ $I_3 (R_4+1/j\omega C) = -ig(t) * R_3$ $I_3 (R_4+R_5+j\omega L+1/j\omega C) = -I_2 (R_4+1/j\omega C)$
-50.0%			e. $-I_1 (R_1+R_2) + I_2 * R_2 = u_g(t)$ $-I_1 * R_2 + I_2 (R_2+R_3+R_4+1/j\omega C) -$ $I_3 (R_4+1/j\omega C) = -ig(t) * R_3$ $I_3 (R_4+R_5+j\omega L+1/j\omega C) - I_2 (R_4+1/j\omega C) = 0$

Score: 10 / 10

**Question 5** (10 points)

Postavi jednađžbu četvrte petlje mreže na slici.

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
100.0%			a. a)
-50.0%			b. b)

-50.0%			c.	c)
-50.0%			d.	d)

Score: 10 / 10

---

**Total score: 50 / 50 = 100.0%**

---

Grafovi koji imaju svojstvo da se mogu separirati u dva nedegenerirana subgrafa, a koji imaju samo jedan zajednicki cvor zovu se:

Student response: Percent  
 Value Correct  
 Response Student  
 Response Answer Choices  
 -50.0% a. komplementarni grafovi  
 100.0% b. rasklopivi grafovi  
 -50.0% c. topološki grafovi

Score: 10 / 10

Question 3 (10 points)  
 Osnovni tip algebarskih jednađbi mreža u matricnoj formi je:

Student response: Percent  
 Value Correct  
 Response Student  
 Response Answer Choices  
 -50.0% a. samo opce jednađbe petlji  
 -50.0% b. samo opce jednađbe cvorova  
 100.0% c. opce jednađbe petlji i cvorova  
 -50.0% d. ne postoji osnovni tip

Score: 10 / 10

Question 4 (10 points)  
 Koliko graf ima stablenih grana?

Student response: Percent  
 Value Correct  
 Response Student  
 Response Answer Choices  
 -50.0% a. 0  
 -50.0% b. 1  
 -50.0% c. 2  
 100.0% d. 3  
 -50.0% e. 4

Score: -5 / 10

Question 5 (10 points)  
 Zadana je reducirana matrica incidencije grafa.

---

1	1	0	0	0	0	1
-1	-1	1	0	0	0	0
0	0	-1	0	1	0	0
0	0	0	-1	-1	-1	0

Da li grane 1,2,4,5 sacinjavaju stablo?

Student response: Percent

Value Correct

Response Student

Response Answer Choices

- 50.0% a. Da, jer je njihova determinanta submatrice jednaka -1  
-50.0% b. Da, jer je njihova determinanta submatrice jednaka 1  
-50.0% c. Da, jer je njihova determinanta submatrice jednaka 0  
100.0% d. Ne, jer je njihova determinanta submatrice jednaka 0  
-50.0% e. Ne, jer je njihova determinanta submatrice jednaka 1

Score: 10 / 10

Total score: 35 / 50 = 70.0%

[View Results](#)

Osnovi topološke analize elektricnih mreža.

User ID: irajsl Attempt: 1 / 1 Out of: 50

Started: April 6, 2004 23:56 Finished: April 7, 2004 00:06 Time spent: 9 min. 54 sec.

Student finished 0 min. 6 sec. ahead of the 10 min. time limit.

Question 1 (10 points)

KZN u matricnoj normi glasi:

Student response: Percent

Value Correct

Response Student

Response Answer Choices

- 100.0% a.  $U_b(s) = U_g(s) + Z_b(s) * I_b(s) + u_c(0)/s - L_b * i_b(0)$   
-50.0% b.  $U_b(s) = U_g(s) + Z_b(s) * I_b(s)$   
-50.0% c.  $U_b(s) = U_g(s) + Z_b(s) * I_b(s) + u_c(0)/s$   
-50.0% d.  $0 = U_g(s) + Z_b(s) * I_b(s) + u_c(0)/s - L_b * i_b(0)$

Score: 10 / 10

Question 2 (10 points)

Prvi korak u prikazivanju mreže je:

Student response: Percent

Value Correct

Response Student

Response Answer Choices

- 50.0% a. pisanje jednađžbi cvorova  
-50.0% b. pisanje jednađžbi petlji  
100.0% c. reduciranje mreže na tzv. graf

Score: 10 / 10

Question 3 (10 points)

Što od slijedeceg ne može biti KZS za cvor?

Student response: Percent

---

Value Correct

Response Student

Response Answer Choices

-50.0% a.  $i1 + i2 - i3 + 0 + 0 = 0$   
-50.0% b.  $-i1 + 0 + 0 + i4 + 0 = 0$   
-50.0% c.  $0 - i2 + 0 - i4 - i5 = 0$   
100.0% d.  $1 + 0 + 2i3 + 0 + i5 = 0$

Score: 10 / 10

Question 4 (10 points)

Kako glasi matrica incidencije za zadani graf ako su 1,2,3,4,6 stablene grane?

Student response: Percent

Value Correct

Response Student

Response Answer Choices

-50.0% a.  $\begin{bmatrix} 1 & 0 & 0 & 0 & 0 & 0 & -1 \\ 1 & 1 & 0 & 0 & 1 & 0 & 0 \\ 0 & 1 & 1 & 0 & 0 & 0 & 0 \\ 0 & 0 & 1 & 1 & 0 & 0 & 0 \\ 0 & 0 & 0 & -1 & -1 & -1 & 0 \\ 0 & 0 & 0 & 0 & 0 & -1 & -1 \end{bmatrix}$

-50.0% b.  $\begin{bmatrix} -1 & 0 & 0 & 0 & 0 & 0 & -1 \\ -1 & -1 & 0 & 0 & -1 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 1 & 0 & 1 & 0 & 1 & 0 \\ 1 & 1 & 0 & 0 & -1 & -1 & 1 \\ 1 & 0 & 0 & 0 & -1 & -1 & 1 \end{bmatrix}$

100.0% c.  $\begin{bmatrix} 1 & 0 & 0 & 0 & 0 & 0 & -1 \\ -1 & -1 & 0 & 0 & -1 & 0 & 0 \\ 0 & 1 & 1 & 0 & 0 & 0 & 0 \\ 0 & 0 & -1 & 1 & 0 & 0 & 0 \\ 0 & 0 & 0 & -1 & 1 & 1 & 0 \\ 0 & 0 & 0 & 0 & 0 & -1 & 1 \end{bmatrix}$

Score: 10 / 10

Question 5 (10 points)

Koliko ima stablenih grana u zadanom grafu?

Student response: Percent

Value Correct

Response Student

Response Answer Choices

-50.0% a. 2  
100.0% b. 3  
-50.0% c. 4  
-50.0% d. 5  
-50.0% e. 6

Score: -5 / 10

Total score: 35 / 50 = 70.0%

View Results

### Osnovi topološke analize električnih mreža.

User ID: mboskovic

Attempt: 1 / 1

Out of: 50

Started: April 13, 2004  
13:56

Finished: April 13, 2004  
14:00

Time spent: 3 min. 24  
sec.

Student finished 6 min. 36 sec. ahead of the 10 min. time limit.

#### Question 1 (10 points)

$I_b(0)$  je vektor početnih struja u induktivitetima s elementom  $I_j(0)$ .

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
33.0%			a. u j-tom redu, ako j-ta grana u mrezi ima induktivitet s početnom stujom $i_j(0)$
33.0%			b. pozitivnim, ako je u istom smjeru s orijentacijom j-te grane u grafu
33.0%			c. negativnim, ako je u suprotnom smjeru s orijentacijom j-te grane u grafu
-50.0%			d. nista od navedenog

Score: 9.9 / 10

#### Question 2 (10 points)

Linearni graf je suvisao ili povezan, ako se svakom paru čvorišta grafa koja nisu identična, može pridružiti otvoren put tako da je jedno čvorište toga para početno, a drugo završno čvorište puta.

Da li je definicija točna?

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
---------------	------------------	------------------	----------------



100.0%			a.	da
-50.0%			b.	ne

Score: 10 / 10

### Question 3 (10 points)

Ako je broj čvorova 4, a broj grana 5, koliko jednađbi KZN nam je potrebno?

Student response:

Percent Value	Correct Response	Student Response	Answer Choices	
100.0%			a.	2 od 3
-50.0%			b.	3 od 4
-50.0%			c.	4 od 5
-50.0%			d.	3 od 3

Score: 10 / 10

### Question 4 (10 points)

Koliko ima spona u zadanom grafu?


Student response:

Percent Value	Correct Response	Student Response	Answer Choices	
-50.0%			a.	1
100.0%			b.	2
-50.0%			c.	3
-50.0%			d.	5
-50.0%			e.	7

Score: 10 / 10

### Question 5 (10 points)

Koliko ima spona u zadanom grafu?

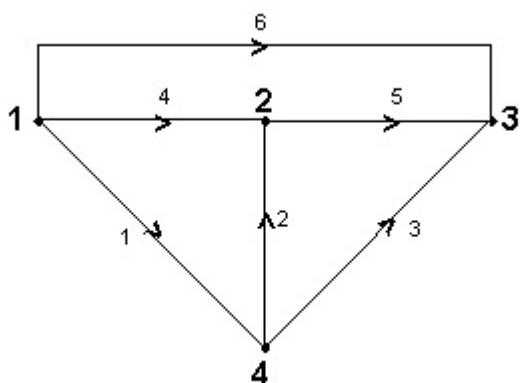

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. 0
-50.0%			b. 1
-50.0%			c. 2
100.0%			d. 3
-50.0%			e. 4

Score: 10 / 10

Total score: 49.9 / 50 = 99.8%

[View Results](#)

### Jednadžbe mreža.

User ID: mlesjak

Attempt: 1 / 1

Out of: 50

Started: April 13, 2004  
14:11

Finished: April 13, 2004  
14:16



Time spent: 5 min. 35  
sec.

Student finished 4 min. 25 sec. ahead of the 10 min. time limit.

Question 1 (10 points)

U mreži sa 6 grana i 4 čvora broj linearno nezavisnih jednažbi struja(KZS) i napona(KZN) je:

Student response:



Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. KZS=5, KZN=5
-50.0%			b. KZN=5, KZS=3
100.0%			c. KZS=3, KZN=3
-50.0%			d. KZN=3, KZS=5
-50.0%			e. ne može se odrediti bez poznavanja topološke strukture mreže

Score: 10 / 10

## Question 2 (10 points)

Ako nije zadano, kako određujemo smjer konturnih struja korištenjem KZS?

Student response:



Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. smjer konturnih struja je uvijek u smjeru kazaljke na satu
-50.0%			b. sve konturne struje moraju biti istog smjera
-50.0%			c. barem dvije konturne struje moraju biti različitih smjerova
-50.0%			d. ako nije zadano, ne možemo riješiti mrežu pomoću KZS
100.0%			e. smjer sami određujemo onako kako nam najviše odgovara

Score: 10 / 10

**Question 3** (10 points)

Od koliko čvorova se sastoji mreža sa 6 grana ako smo analizom mreže dobili 3 linearno nezavisne jednačbe KZS ?

Student response:



Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. 5
100.0%			b. 4
-50.0%			c. 3
-50.0%			d. 8
-50.0%			e. ne možemo odrediti

Score: 10 / 10

**Question 4** (10 points)

Odredi struju  $i(t)$  za  $t < 0$  ako je:  $R=L=1$   $U_o(t) = 2\sin(4t)$  za  $t < 0$

Student response:



Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. $t^2 + t + 1$
-50.0%			b. $0.23 \cos(4t)$
100.0%			c. $0.9 \sin(4t - 76^\circ)$
-50.0%			d. $0.5 \sin(2t - 56^\circ)$

Score: -5 / 10

**Question 5** (10 points)

Postavi jednačbu prve i druge petlje mreže na slici u Laplace-ovoj domeni.

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
100.0%			a. a)
-50.0%			b. b)

-50.0%			c.	c)
-50.0%			d.	d)

Score: 10 / 10

**Total score:** 35 / 50 = 70.0%

[View Results](#)

### Osnovi topološke analize električnih mreža.

**User ID:** mlesjak

**Attempt:** 1 / 1

**Out of:** 50

**Started:** April 13, 2004  
14:19

**Finished:** April 13, 2004  
14:22

**Time spent:** 2 min. 52  
sec.

Student finished 7 min. 8 sec. ahead of the 10 min. time limit.

### Question 1 (10 points)

Matrična admitancija čvorova glasi:

Student response:



Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. $Y_n(s) = A * Z_b(s)$
100.0%			b. $Y_n(s) = A * [Z_b(s)]^{(-1)*A^T}$
-50.0%			c. $Y_n(s) = A^{(-1)} * [Z_b(s)]^{(-1)}$
-50.0%			d. $Y_n(s) = A^T * [Z_b(s)]^{(-1)}$

Score: 10 / 10

### Question 2 (10 points)

Grana bez čvorova može biti graf.

Student response:



Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a.   točno
100.0%			b.   netočno

Score: 10 / 10

### Question 3 (10 points)

Ako je broj čvorova 4, a broj grana 5, koliki rang ima matrica incidencije Aa?

Student response:



Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a.   4
-50.0%			b.   1
-50.0%			c.   5
100.0%			d.   3

Score: -5 / 10

### Question 4 (10 points)

Koliko graf ima stablenih grana?


Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a.   0
-50.0%			b.   1
-50.0%			c.   2
100.0%			d.   3
-50.0%			e.   4

Score: 10 / 10

### Question 5 (10 points)

Koliko ima spona u zadanom grafu?

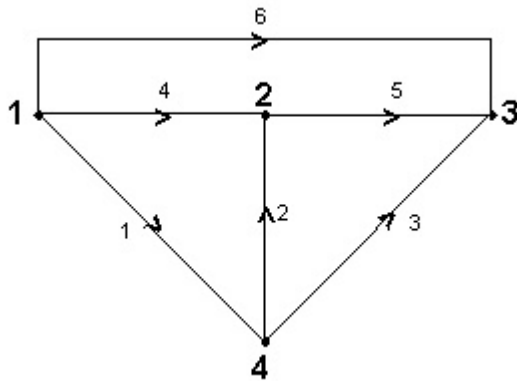

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. 0
-50.0%			b. 1
-50.0%			c. 2
100.0%			d. 3
-50.0%			e. 4

Score: 10 / 10

Total score: 35 / 50 = 70.0%

[View Results](#)

### Jednadžbe mreža.

User ID: hdemoli

Attempt: 1 / 1

Out of: 50



Started: April 13, 2004 14:23 Finished: April 13, 2004 14:32 Time spent: 9 min. 0 sec.

Student finished 1 min. 0 sec. ahead of the 10 min. time limit.

### Question 1 (10 points)

Vektor stanja  $x(t)$  definiran je kao :

Student response:



Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. $[i_c(t); u_L(t)]$
-50.0%			b. $[i_L(t); i_c(t)]$
-50.0%			c. $[U_c(t); U_L(t)]$
-50.0%			d. $[U_L(t); i_L(t)]$
100.0%			e. $[i_L(t); U_c(t)]$

Score: 10 / 10

### Question 2 (10 points)

Ako u mreži postoji zavisni strujni izvor, što se dešava sa potrebnim brojem jednažbi za rješavanje mreže pomoću KZS?

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. povećava za broj zavisnih strujnih izvora
100.0%			b. ostaje isti
-50.0%			c. smanjuje za broj zavisnih strujnih izvora
-50.0%			d. u tom slučaju mreža se ne može riješiti pomoću KZS
-50.0%			e. smanjuje ili povećava, ovisno o mjestu spoja zavisnog strujnog izvora

Score: 10 / 10

### Question 3 (10 points)

Koje su od navedenih tvrdnji istinite?

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
---------------	------------------	------------------	----------------



-50.0%

a. Ako postoji više čvorova u nekoj el. mreži, odabirom dva referentna na suprotnim stranama mreže postupak rješavanja KZN se pojednostavljuje.

-50.0%

b. Ako tražimo samo struju jedne grane u el. mreži možemo koristiti samo one linearno nezavisne jednačbe u kojima se pojavljuju konturne struje koja prolaze određenom granom.

100.0%



c. Ako u nekoj grani mreže postoji nezavisni izvor koji daje struju  $I_a$ , iznos konturne struje koja obilazi i tu granu je  $I_a$ .

-50.0%

d. Da bi odredili napon grane neke el. mreže uvijek oduzimamo napon čvora na većem potencijalu od napona čvora na manjem potencijalu.


Score: 10 / 10

#### Question 4 (10 points)

Za mrežu na slici ( $u_{g1} > 0$ ) vrijedi:

Student response:



Percent Value	Correct Response	Student Response	Answer Choices
100.0%			a. $u_{v3}/R_4 - C_5 d(u_{v4} - u_{v3})/dt - (u_{v4} -$

			$uv3)/R6 = 0$
-50.0%			b. $-(uv1-ug1)/R1 + uv1/R2 - (uv4-uv1)/R3 = 0$
-50.0%			c. $uv3/R4 - C5 (uv4-uv3) + (uv4-uv3)/R6 = 0$
-50.0%			d. $uv3/R4 - C5 d(uv4-uv3)/dt + (uv4-uv3)/R6 = 0$

Score: -5 / 10

### Question 5 (10 points)

Za mrežu sa slike vrijedi

Student response:	Percent Value	Correct Response	Student Response	Answer Choices
	-50.0%			a. $-(uv1(s)+ug(s))/R1 - uv1(s)/R2 - 1/sL3 (uv4(s)-uv1(s)) + iL3(0)/s = 0$
	-50.0%			b. $-(uv1(s)+ug(s))/R1 - uv1(s)/R2 + 1/sL3 (uv4(s)-uv1(s)) + iL2(0)/s = 0$
	-50.0%			c. $-(uv1(s)+ug(s))/R1 + uv1(s)/R2 + 1/sL3 (uv4(s)-uv1(s)) - iL2(0)/s = 0$
	100.0%			d. $-(uv1(s)+ug(s))/R1 - uv1(s)/R2 - 1/sL3 (uv4(s)-uv1(s)) - iL2(0)/s = 0$

Score: 10 / 10

Total score: 35 / 50 = 70.0%

[View Results](#)

Osnovi topološke analize električnih mreža.

User ID: hdemoli

Attempt: 1 / 1

Out of: 50

Started: April 13, 2004  
14:34

Finished: April 13, 2004  
14:35

Time spent: 1 min. 24  
sec.

Student finished 8 min. 36 sec. ahead of the 10 min. time limit.

Question 1 (10 points)

Kako glasi jednadžba za matričnu impedanciju grana?

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
100.0%			a. $Z_b(s) = R_b + s \cdot L_b + (1/s)D_b$
-50.0%			b. $Z_b(s) = R_b + 1/(sL_b) + s \cdot D_b$
-50.0%			c. $Z_b(s) = 1/r_b + 1/(s \cdot L_b) + s/D_b$
-50.0%			d. $Z_b(s) = 1/(r_b + s \cdot L_b + D_b/s)$

Score: 10 / 10

Question 2 (10 points)

Suvisao subgraf odabran u suvislom grafu tako da sadrži sva čvorišta grafa, ali ne sadrži petlje, naziva se:

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
100.0%			a. stablo grafa
-50.0%			b. sustav nezavisnih grana

-50.0%

c. temeljna petlja

Score: 10 / 10

### Question 3 (10 points)

Pišući KZS za neku mrežu, pišemo sistem linearnih jednažbi za sve čvorove. Što su varijable, a što koeficijenti?

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
100.0%			a. varijable su struje u granama, koeficijenti 1, -1, 0
-50.0%			b. varijable su samo struje u sponama, koeficijenti mogu biti bilo koji brojevi
-50.0%			c. varijable su naponi u čvorovima, koeficijenti mogu biti bilo koji brojevi
-50.0%			d. varijable su struje u granama, koeficijenti mogu biti bilo koji brojevi

Score: 10 / 10

### Question 4 (10 points)

Da li je graf planaran?

Student response:



Percent Value	Correct Response	Student Response	Answer Choices
100.0%			a. Da
-50.0%			b. Ne

Score: 10 / 10

**Question 5** (10 points)

Koliko ima stablenih grana u zadanom grafu?

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. 2
100.0%			b. 3
-50.0%			c. 4
-50.0%			d. 5
-50.0%			e. 6

Score: 10 / 10

---

**Total score:** 50 / 50 = 100.0%

[View Results](#)

**Jednadžbe mreža.**

User ID: mkajganic

Attempt: 1 / 1

Out of: 50

Started: April 13, 2004  
14:36

Finished: April 13, 2004  
14:45

Time spent: 8 min. 46  
sec.

Student finished 1 min. 14 sec. ahead of the 10 min. time limit.

**Question 1** (10 points)

Zadana je mreža koja se sastoji od izvora i tri otpora spojena u paralelu te su postavljene tri linearno nezavisne jednadžbe KZS. Promjenom smjera jedne (bilo koje) konturne struje, koliko linearno nezavisnih jednadžbi mijenja svoj izraz ?

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
---------------	------------------	------------------	----------------

-50.0%			a.	1
50.0%	▶	▶	b.	2
50.0%	▶	▶	c.	3
-50.0%			d.	nijedna

Score: 10 / 10

### Question 2 (10 points)

Da li prilikom rješavanja mreže uzimamo u obzir zavisne izvore?

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. ne, njih naknadno uvrštavamo
-50.0%			b. ako postoje zavisni strujni izvori, tada mrežu ne možemo riješiti pomoću KZN ili KZS
-50.0%			c. samo ako mrežu rješavamo korištenjem KZN
-50.0%			d. samo ako mrežu rješavamo korištenjem KZS
100.0%	▶	▶	e. da, opisujemo ih pomoću parametara o kojima ovise

Score: 10 / 10

### Question 3 (10 points)

Od koliko se grana sastoji mreža od 4 čvora, ako smo analizirajući mrežu dobili 3 linearno nezavisne jednačbe napona ?

Student response:



Percent Value	Correct Response	Student Response	Answer Choices
100.0%	▶	▶	a. 6
-50.0%			b. 4

-50.0%			c. 2
-50.0%			d. ne možemo odrediti bez poznavanja broja linearno nezavisnih jednažbi napona

Score: 10 / 10

#### Question 4 (10 points)

Koja od jednažbi odgovara uvjetima sa slike?

Student response:	Percent Value	Correct Response	Student Response	Answer Choices
	-50.0%			a. $(u_1+u_{g1})/R_1 + u_1/R_2 - 1/L_3(u_2-u_1) - i_3(0) = 0$
	-50.0%			b. $(u_1-u_{g1})/R_1 + u_1/R_2 - 1/L_3(u_2+u_1) - i_3(0) = 0$
	-50.0%			c. $(u_1+u_{g1})/R_1 + u_1/R_2 - 1/L_3(u_2-u_1) - i_3(0) = 0$
	100.0%			d. niti jedna od navedenih !

Score: 10 / 10

#### Question 5 (10 points)

Za mrežu na slici vrijedi

Student response:	Percent Value	Correct Response	Student Response	Answer Choices
-------------------	---------------	------------------	------------------	----------------

-50.0%			a. $uv3/R4 - C5 \frac{d(uv4-uv3)}{dt} - (uv4-uv3)/R6 = 0$
-50.0%			b. $uv3/R4 - C5 \frac{d(uv4-uv3)}{dt} - ig6 = 0$
100.0%	▶	▶	c. $uv3/R4 - C5 \frac{d(uv4-uv3)}{dt} + ig6 = 0$
-50.0%			d. $uv3/R4 + C5 \frac{d(uv4-uv3)}{dt} - ig6 = 0$
-50.0%			e. ništa od navedenog

Score: 10 / 10

Total score: 50 / 50 = 100.0%

[View Results](#)

#### Jednadžbe mreža.

User ID: tvesic

Attempt: 1 / 1

Out of: 50

Started: April 13, 2004  
14:50

Finished: April 13, 2004  
14:52

Time spent: 1 min. 46  
sec.

Student finished 8 min. 14 sec. ahead of the 10 min. time limit.

#### Question 1 (10 points)

Zadana je mreža koja se sastoji od izvora i tri otpora spojena u paralelu te su postavljene tri linearno nezavisne jednadžbe KZS. Promjenom smjera jedne (bilo koje) konturne struje, koliko linearno nezavisnih jednadžbi mijenja svoj izraz ?

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. 1
50.0%	▶	▶	b. 2
50.0%	▶	▶	c. 3
-50.0%			d. nijedna





Score: 10 / 10

### Question 2 (10 points)

Koliko iznosi najmanji broj linearno nezavisnih jednažbi KZN za mrežu od  $N_b$  grana i  $N_v$  čvorova?

Student response:



Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. $N_b - (N_v + 1)$
-50.0%			b. $N_b - N_v$
-50.0%			c. $N_v - 1$
100.0%			d. $N_b - (N_v - 1)$
-50.0%			e. $N_v - (N_b - 1)$

Score: 10 / 10

### Question 3 (10 points)

Što je  $w(t)$  u jednažbama stanja ?

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. vektor stanja
100.0%			b. vektor pobudnih funkcija
-50.0%			c. vektor odzivnih funkcija
-50.0%			d. ništa od navedenog

Score: 10 / 10

### Question 4 (10 points)

Za shemu na slici matrica

$\frac{1}{R_1} + \frac{1}{R_3} + \frac{1}{sL_2}$        $-\frac{1}{sL_2}$        $-\frac{1}{R_3}$

$-\frac{1}{sL_2}$        $-\frac{1}{sL_2} + sC_5 + \frac{1}{R_4}$        $-\frac{1}{R_4}$

$$-1/R_3 \qquad -1/R_4 \qquad 1/R_3 + 1/R_4 + 1/R_6$$

je...

Student response:	Percent Value	Correct Response	Student Response	Answer Choices
	100.0%			a. matrica impedancije čvorova
	-50.0%			b. matrica admitancija čvorova
	0.0%			c. niti jedno od navedenih

Score: 10 / 10

### Question 5 (10 points)

Kako glase jednađbe petlji za mrežu na slici?

Student response:	Percent Value	Correct Response	Student Response	Answer Choices
	-50.0%			a. a)
	-50.0%			b. b)
	100.0%			c. c)
	-50.0%			d. d)

Score: 10 / 10

---

**Total score:** 50 / 50 = 100.0%

[View Results](#)



**Osnovi topološke analize električnih mreža.****User ID:** tvesic**Attempt:** 1 / 1**Out of:** 50**Started:** April 13, 2004  
14:54**Finished:** April 13, 2004  
14:55**Time spent:** 1 min. 31  
sec.

Student finished 8 min. 29 sec. ahead of the 10 min. time limit.

**Question 1** (10 points)

Kojom relacijom smo preslikali struje grana u struje petlji?

Student response:



Percent Value	Correct Response	Student Response	Answer Choices
100.0%			a. $ib(t) = B^T * im(t)$
-50.0%			b. $ub(t) = A^T * un(t)$
-50.0%			c. $B * ub(t) = 0$
-50.0%			d. $A * ib(t) = 0$

Score: 10 / 10

**Question 2** (10 points)

Graf je planaran ako se ne može prikazati u ravnini (tako da se izvan čvorišta ni jedna grana ne ukrštava s drugom). Da li je definicija ispravna?

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. da
100.0%			b. ne

Score: 10 / 10

**Question 3** (10 points)Ako je broj čvorova 4, a broj grana 5, koliki rang ima spojna matrica  $B_a$ ?

Student response:


Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. 4
-50.0%			b. 3

100.0%			c.	2
-50.0%			d.	1

Score: 10 / 10
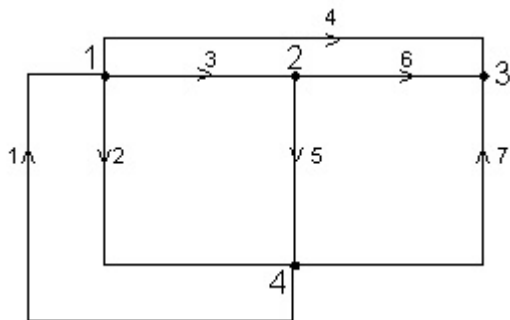
#### Question 4 (10 points)

Kako glasi rastavna matrica grafa ako su grane 1,3,7 stabilne?



Student response:	Percent Value	Correct Response	Student Response	Answer Choices
	-50.0%			a. $\begin{bmatrix} 1 & 1 & 0 & 1 & 1 & 1 & 0 \\ 0 & 0 & -1 & 0 & -1 & -1 & 0 \\ 0 & 0 & 0 & -1 & 0 & 1 & 1 \end{bmatrix}$
	100.0%			b. $\begin{bmatrix} 1 & -1 & 0 & -1 & -1 & -1 & 0 \\ 0 & 0 & 1 & 0 & -1 & -1 & 0 \\ 0 & 0 & 0 & 1 & 0 & 1 & 1 \end{bmatrix}$
	-50.0%			c. $\begin{bmatrix} 1 & -1 & 0 & -1 & -1 & -1 & 0 \\ 0 & 0 & -1 & 0 & 1 & 1 & 0 \\ 0 & 0 & 0 & 1 & 0 & 1 & 1 \end{bmatrix}$

Score: -5 / 10

#### Question 5 (10 points)

Zadana je reducirana matrica incidencije grafa.

1	1	0	0	0	0	1
-1	-1	1	0	0	0	0
0	0	-1	0	1	0	0
0	0	0	-1	-1	-1	0

Da li grane 1,3,5,6 sačinjavaju stablo?

Student response:	Percent Value	Correct Response	Student Response	Answer Choices
-------------------	---------------	------------------	------------------	----------------

50.0%	▶	▶	a. Da
-50.0%			b. Ne
50.0%	▶	▶	c. Da, jer je njihova determinanta submatrice razlicita od nule
-50.0%			d. Ne, jer je njihova determinanta submatrice jednaka nuli

Score: 10 / 10

Total score: 35 / 50 = 70.0%

[View Results](#)

#### Jednadžbe mreža.

User ID: dcvetek

Attempt: 1 / 1

Out of: 50

Started: April 13, 2004  
14:57

Finished: April 13, 2004  
15:00

Time spent: 2 min. 56  
sec.

Student finished 7 min. 4 sec. ahead of the 10 min. time limit.

#### Question 1 (10 points)

Da bi riješili mrežu, koji od navedenih uvjeta nam nije potreban ?

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
100.0%	▶	▶	a. poznavanje KZN
-50.0%			b. topološka konfiguracija mreže
-50.0%			c. eventualno postojanje ili nepostojanje početnih stanja mreže
-50.0%			d. izvori

-50.0%



e. vrsta i parametri  
elemenata u mreži

Score: 10 / 10

### Question 2 (10 points)

Ako nije zadano, kako određujemo smjer konturnih struja korištenjem KZS?

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. smjer konturnih struja je uvijek u smjeru kazaljke na satu
-50.0%			b. sve konturne struje moraju biti istog smjera
-50.0%			c. barem dvije konturne struje moraju biti različitih smjerova
-50.0%			d. ako nije zadano, ne možemo riješiti mrežu pomoću KZS
100.0%			e. smjer sami određujemo onako kako nam najviše odgovara

Score: 10 / 10

### Question 3 (10 points)

Koje su od navedenih tvrdnji istinite?

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. Ako postoji više čvorova u nekoj el. mreži, odabirom dva referentna na suprotnim stranama mreže postupak

-50.0%			rješavanja KZN se pojednostavljuje.
100.0%	▶	▶	b. Ako tražimo samo struju jedne grane u el. mreži možemo koristiti samo one linearno nezavisne jednačbe u kojima se pojavljuju konturne struje koja prolaze određenom granom.
-50.0%			c. Ako u nekoj grani mreže postoji nezavisni izvor koji daje struju $I_a$ , iznos konturne struje koja obilazi i tu granu je $I_a$ .
-50.0%			d. Da bi odredili napon grane neke el. mreže uvijek oduzimamo napon čvora na većem potencijalu od napona čvora na manjem potencijalu.

Score: 10 / 10

#### Question 4 (10 points)

Za mrežu na slici ( $u_{g1} > 0$ ) vrijedi:

Student response:	Percent Value	Correct Response	Student Response	Answer Choices
	100.0%	▶	▶	a. $u_{v3}/R_4 - C_5 d(u_{v4} - u_{v3})/dt - (u_{v4} - u_{v3})/R_6 = 0$
	-50.0%			b. $-(u_{v1} - u_{g1})/R_1 + u_{v1}/R_2 - (u_{v4} - u_{v1})/R_3 = 0$
	-50.0%			c. $u_{v3}/R_4 - C_5 (u_{v4} -$

$$uv3) + (uv4-uv3)/R6 = 0$$

-50.0%			d. $uv3/R4 - C5 \frac{d(uv4-uv3)}{dt} + (uv4-uv3)/R6 = 0$
--------	--	--	---

Score: 10 / 10

### Question 5 (10 points)

Postavi jednadžbu treće petlje mreže na slici.

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
100.0%			a. a)
-50.0%			b. b)
-50.0%			c. c)
-50.0%			d. d)

Score: 10 / 10

Total score: 50 / 50 = 100.0%

[View Results](#)

### Osnovi topološke analize električnih mreža.

User ID: dcvetek

Attempt: 1 / 1

Out of: 50

Started: April 13, 2004  
15:00

Finished: April 13, 2004  
15:02

Time spent: 1 min. 57  
sec.

Student finished 8 min. 3 sec. ahead of the 10 min. time limit.



**Question 1** (10 points)

je vektor pocetnih napona na kapacitetima s elementom :

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
33.0%			a. u j-tom redu, ako j-ta grana u mrezi ima kapacitet s pocetnim naponom ucj(0)
33.0%			b. pozitivnim, ako se njegov polaritet podudara sa polaritetom j-te grane u grafu
33.0%			c. negativnim, ako je njegov polaritet suprotan od polariteta j-te grane u grafu
-50.0%			d. niti jedan odgovor nije točan

Score: 9.9 / 10

**Question 2** (10 points)

Koje su tvrdnje ispravne?

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
50.0%			a. Čvorište i grana koja spaja to čvorište incidentni su jedan s drugim.
50.0%			b. Broj koji kaže koliko je grana incidentno s nekim čvorištem, naziva se red čvorišta.
-50.0%			c. Dvije su grane u seriji, ako su incidentne s istim parom čvorišta.
-50.0%			d. Dvije grane su paralelne, ako imaju točno jedno

			zajedničko čvorište, koje nije incidentno ni s jednom daljnjom granom.
-50.0%			e. Nijedna od navedenih.

Score: 10 / 10

### Question 3 (10 points)

Matrična jednadžba KZS glasi:

Student response:	Percent Value	Correct Response	Student Response	Answer Choices
	100.0%			a. $A * i_b(t) = 0$
	-50.0%			b. $B * u_b(t) = 0$
	-50.0%			c. $A * u_b(t) = 0$
	-50.0%			d. $B * i_b(t) = 0$

Score: 10 / 10

### Question 4 (10 points)

Kako glasi rastavna matrica grafa ako su grane 1,3,7 stabilne?


Student response:	Percent Value	Correct Response	Student Response	Answer Choices
	-50.0%			a. $\begin{bmatrix} 1 & 1 & 0 & 1 & 1 & 1 \\ 0 & 0 & -1 & 0 & -1 & -1 \\ 0 & 0 & 0 & -1 & 0 & 1 \\ 1 \end{bmatrix}$
	100.0%			b. $\begin{bmatrix} 1 & -1 & 0 & -1 & -1 & -1 \\ 0 & 0 & 1 & 0 & -1 & -1 \\ 0 & 0 & 0 & 1 & 0 & 1 \\ 1 \end{bmatrix}$
	-50.0%			c. $\begin{bmatrix} 1 & -1 & 0 & -1 & -1 & -1 \\ 0 \end{bmatrix}$

0	0	-1	0	1	1
0					
0	0	0	1	0	1
1					

Score: 10 / 10

Question 5 (10 points)

Koliko ima spona u zadanom grafu?

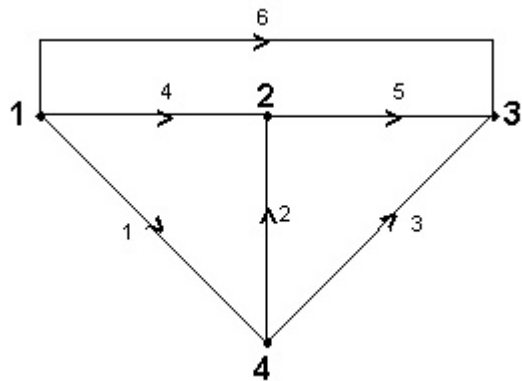

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. 0
-50.0%			b. 1
-50.0%			c. 2
100.0%			d. 3
-50.0%			e. 4



Score: 10 / 10

Total score: 49.9 / 50 = 99.8%

**Question 1** (10 points)

Koje su nepoznate varijable u jednažbama petlji?

Student response:



Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. naponi
100.0%			b. struje
-50.0%			c. početni uvjeti
-50.0%			d. izvori
-50.0%			e. naponi i struje

Score: 10 / 10

**Question 2** (10 points)

Ako u mreži postoji zavisni strujni izvor, što se dešava sa potrebnim brojem jednažbi za rješavanje mreže pomoću KZS?

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. povećava za broj zavisnih strujnih izvora
100.0%			b. ostaje isti
-50.0%			c. smanjuje za broj zavisnih strujnih izvora
-50.0%			d. u tom slučaju mreža se ne može riješiti pomoću KZS
-50.0%			e. smanjuje ili povećava, ovisno o

mjestu spoja  
zavisnog strujnog  
izvora

Score: 10 / 10

### Question 3 (10 points)

Ako kroz neku granu el. mreže prolaze dvije konturne struje  $I_a$  i  $I_b$  različitog smjera, a pretpostavljen smjer struje  $I_g$  grane koju tražimo je istog smjera kao  $I_a$ , koji izraz točno opisuje struju grane  $I_g$  ?


Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. $I_g = -I_a - I_b$
-50.0%			b. $I_g = I_a + I_b$
-50.0%			c. $I_g = -I_a + I_b$
100.0%			d. $I_g = I_a - I_b$
-50.0%			e. ništa od navedenog

Score: 10 / 10
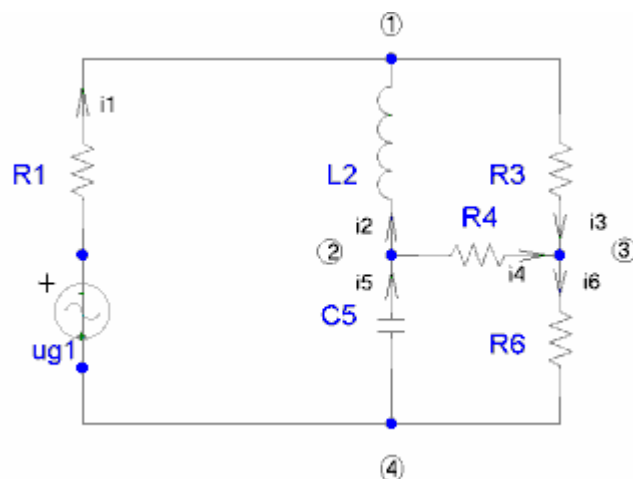
### Question 4 (10 points)

Koja matrica odgovara matrici struje za sliku ?



Student response:


Percent Value	Correct Response	Student Response	Answer Choices
---------------	------------------	------------------	----------------

-50.0%			a. $u_g/R1+iL2(0)/s$ $iL2(0)/s+C5uC5(0) 0$
-50.0%			b. $u_g/R1+iL2(0)/s$ $iL2(0)/s+C5uC5(0)$ $i1$
-50.0%			c. $u_g/R1+iL2(0)/s -$ $iL2(0)/s-C5uC5(0) i1$
100.0%			d. $u_g/R1+iL2(0)/s -$ $iL2(0)/s-C5uC5(0) 0$

Score: -5 / 10
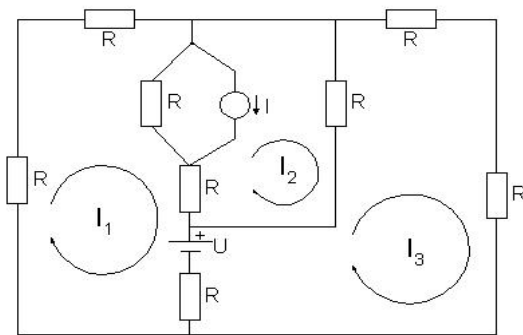
### Question 5 (10 points)

Postavi jednađžbu prve i druge petlje mreže na slici.



- a)  $5RI_1 - 2RI_2 - I_3R = -U + IR$   
 $-2RI_1 + 3RI_2 - I_3R = -IR$
- b)  $5RI_1 - 2RI_2 - I_3R = -U + IR$   
 $-2RI_1 + 3RI_2 - I_3R = IR$
- c)  $5RI_1 - 2RI_2 - I_3R = +U - IR$   
 $-2RI_1 + 3RI_2 - I_3R = -IR$
- d)  $5RI_1 - 2RI_2 - I_3R = -U + IR$   
 $2RI_1 - 3RI_2 - I_3R = IR$

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
100.0%			a. a)
-50.0%			b. b)
-50.0%			c. c)
-50.0%			d. d)



Score: -5 / 10

---

**Total score:** 20 / 50 = 40.0%

**Question 1** (10 points)



Matricna jednadzba KZS glasi:

Student response:	Percent Value	Correct Response	Student Response	Answer Choices
	100.0%			a. $A \cdot I_b(s) = 0$
	-50.0%			b. $B \cdot U_b(s) = 0$
	-50.0%			c. $A \cdot U_b(s) = 0$
	-50.0%			d. $B \cdot I_b(s) = 0$

Score: 10 / 10

**Question 2** (10 points)

Što je temeljni rez?

Student response:	Percent Value	Correct Response	Student Response	Answer Choices
	-50.0%			a. Petlja koju u suvislom grafu tvori jedna spojnica s granama stabla.
	-50.0%			b. Sve temeljne petlje u suvislom grafu stvorene na bazi jednog stabla.
	100.0%			c. Skup grana od kojih jedna pripada stablu, a druge sustavu spona, a odabrane su tako da se odstranjenjem toga skupa grana, graf raspada u 2 međusobna nesuvislata grafa.

Score: 10 / 10

### Question 3 (10 points)

Ako je broj čvorova 4, a broj grana 5, koliki rang ima spojna matrica Ba?

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. 4
-50.0%			b. 3
100.0%			c. 2
-50.0%			d. 1

Score: 10 / 10

### Question 4 (10 points)

Kako glasi matrica incidencije za zadani graf ako su 1,2,3,4,6 stablene grane?

Student response:









Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. $\begin{bmatrix} 1 & 0 & 0 & 0 & 0 & 0 & -1 \\ 1 & 1 & 0 & 0 & 1 & 0 & 0 \\ 0 & 1 & 1 & 0 & 0 & 0 & 0 \\ 0 & 0 & 1 & 1 & 0 & 0 & 0 \\ 0 & 0 & 0 & -1 & -1 & -1 & 0 \\ 0 & 0 & 0 & 0 & 0 & -1 & -1 \end{bmatrix}$
-50.0%			b. $\begin{bmatrix} -1 & 0 & 0 & 0 & 0 & 0 & -1 \\ -1 & -1 & 0 & 0 & -1 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 1 & 0 & 1 & 0 & 1 & 0 \\ 1 & 1 & 0 & 0 & -1 & -1 & 1 \\ 1 & 0 & 0 & 0 & -1 & -1 & 1 \end{bmatrix}$
100.0%			c. $\begin{bmatrix} 1 & 0 & 0 & 0 & 0 & 0 & -1 \\ -1 & -1 & 0 & 0 & -1 & 0 & 0 \\ 0 & 1 & 1 & 0 & 0 & 0 & 0 \\ 0 & 0 & -1 & 1 & 0 & 0 & 0 \\ 0 & 0 & 0 & -1 & 1 & 1 & 0 \\ 0 & 0 & 0 & 0 & 0 & -1 & 1 \end{bmatrix}$



Score: 10 / 10

**Question 5** (10 points)



Kako glasi spojna matrica za zadani graf? (2,5,6 su spone)

Student response:	Percent Value	Correct Response	Student Response	Answer Choices
	25.0%			a. $\begin{bmatrix} 1 & 1 & 0 & -1 & 0 & 0 \\ -1 & 0 & -1 & 1 & 1 & 0 \\ -1 & 0 & -1 & 0 & 0 & 1 \end{bmatrix}$
	25.0%			b. $\begin{bmatrix} -1 & -1 & 0 & 1 & 0 & 0 \\ -1 & 0 & -1 & 1 & 1 & 0 \\ -1 & 0 & -1 & 0 & 0 & 1 \end{bmatrix}$
	25.0%			c. $\begin{bmatrix} 1 & 1 & 0 & -1 & 0 & 0 \\ 1 & 0 & 1 & -1 & -1 & 0 \\ 1 & 0 & 1 & 0 & 0 & -1 \end{bmatrix}$
	25.0%			d. $\begin{bmatrix} 1 & 1 & 0 & -1 & 0 & 0 \\ -1 & 0 & -1 & 1 & 1 & 0 \\ 1 & 0 & 1 & 0 & 0 & -1 \end{bmatrix}$
	-50.0%			e. $\begin{bmatrix} -1 & -1 & 0 & 1 & 0 & 0 \\ 1 & 0 & 1 & 1 & -1 & 0 \\ -1 & 0 & 1 & 0 & 0 & -1 \end{bmatrix}$

Score: 10 / 10

**Question 1** (10 points)



Koliko ima linearno nezavisnih jednađbi KZS u mreži sa 4 grane?

Student response:	Percent Value	Correct Response	Student Response	Answer Choices
	-50.0%			a. 4
	-50.0%			b. 3
	-50.0%			c. 2
	100.0%			d. ništa od navedenog

Score: 10 / 10

**Question 2** (10 points)



O čemu ovisi broj linearno nezavisnih jednažbi KZS ?

Student response:	Percent Value	Correct Response	Student Response	Answer Choices
	-50.0%			a. o broju elemenata u granama
	-50.0%			b. o broju grana
	100.0%			c. o broju čvorova
	-50.0%			d. o broju čvorova i grana
	-50.0%			e. ništa od navedenog

Score: 10 / 10

**Question 3** (10 points)

Od koliko se grana sastoji mreža od 4 čvora, ako smo analizirajući mrežu dobili 3 linearno nezavisne jednažbe napona ?



Student response:	Percent Value	Correct Response	Student Response	Answer Choices
	100.0%			a. 6
	-50.0%			b. 4
	-50.0%			c. 2
	-50.0%			d. ne možemo odrediti bez poznavanja broja linearno nezavisnih jednažbi napona

Score: 10 / 10

**Question 4** (10 points)

Iz slike slijedi...

Student response:



Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. $i_4 = (u_{v2}-u_{v3})/R_4$
-50.0%			b. $i_1 = (u_g+u_1)/R_1$
-50.0%			c. $i_1 = (u_g-u_{v1})/R_1$
-50.0%			d. $i_5 = C_5 \, du_5/dt$
100.0%			e. svi odgovori su točni

Score: 10 / 10

#### Question 5 (10 points)

Kako glase jednađbe petlji za mrežu na slici?

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. a)
-50.0%			b. b)
100.0%			c. c)
-50.0%			d. d)

Score: 10 / 10



---

**Total score:** 50 / 50 = 100.0%

#### Question 1 (10 points)

Kojom relacijom smo preslikali struje grana u struje petlji?

Student response:



Percent Value	Correct Response	Student Response	Answer Choices
100.0%			a. $i_b(t) = B^T \cdot i_m(t)$

-50.0%			b. $ub(t) = A^T * un(t)$
-50.0%			c. $B * ub(t) = 0$
-50.0%			d. $A * ib(t) = 0$

Score: 10 / 10

### Question 2 (10 points)



Grafovi koji imaju svojstvo da se mogu separirati u dva nedegenerirana subgrafa, a koji imaju samo jedan zajednički čvor zovu se:

Student response:	Percent Value	Correct Response	Student Response	Answer Choices
	-50.0%			a. komplementarni grafovi
	100.0%			b. rasklopivi grafovi
	-50.0%			c. topološki grafovi

Score: 10 / 10

### Question 3 (10 points)

Pišući KZS za neku mrežu, pišemo sistem linearnih jednažbi za sve čvorove. Što su varijable, a što koeficijenti?

Student response:	Percent Value	Correct Response	Student Response	Answer Choices
	100.0%			a. varijable su struje u granama, koeficijenti 1, -1, 0
	-50.0%			b. varijable su samo struje u sponama, koeficijenti mogu biti bilo koji brojevi
	-50.0%			c. varijable su naponi u čvorovima, koeficijenti mogu biti bilo koji brojevi
	-50.0%			d. varijable su struje u granama, koeficijenti mogu biti bilo koji

			brojevi

Score: 10 / 10

**Question 4** (10 points)

Da li je graf planaran?

Student response:	Percent Value	Correct Response	Student Response	Answer Choices
	100.0%			a. Da
	-50.0%			b. Ne

Score: 10 / 10

**Question 5** (10 points)

Koliko ima stablenih grana u zadanom grafu?



Student response:	Percent Value	Correct Response	Student Response	Answer Choices
	-50.0%			a. 2
	100.0%			b. 3
	-50.0%			c. 4
	-50.0%			d. 5
	-50.0%			e. 6

Score: 10 / 10

**Total score:** 50 / 50 = 100.0%

**Question 1** (10 points)



Kojom relacijom smo preslikali napone grana u napone čvorova?

Student response:	Percent Value	Correct Response	Student Response	Answer Choices
	-50.0%			a. $ib(t) = B^T * im(t)$
	100.0%			b. $ub(t) = A^T * un(t)$
	-50.0%			c. $B * ub(t) = 0$
	-50.0%			d. $A * ib(t) = 0$

Score: -5 / 10

### Question 2 (10 points)

Što je temeljni rez?

Student response:	Percent Value	Correct Response	Student Response	Answer Choices
	-50.0%			a. Petlja koju u suvislom grafu tvori jedna spojnica s granama stabla.
	-50.0%			b. Sve temeljne petlje u suvislom grafu stvorene na bazi jednog stabla.
	100.0%			c. Skup grana od kojih jedna pripada stablu, a druge sustavu spona, a odabrane su tako da se odstranjenjem toga skupa grana, graf raspada u 2 međusobna nesuvisla grafa.

Score: 10 / 10

### Question 3 (10 points)

Broj čvorova, referentni smjerovi za struje i referentni polariteti za napone, mogu biti

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
100.0%			a. proizvoljno postavljani
-50.0%			b. samo je jedan odabir ispravan
-50.0%			c. čvorovi su jedinstveno postavljani, dok se ostalo može mijenjati
-50.0%			d. možemo mijenjati samo referentni smjer struje

Score: -5 / 10

#### Question 4 (10 points)

Koliko graf ima stablenih grana?

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. 0
-50.0%			b. 1
-50.0%			c. 2
100.0%			d. 3
-50.0%			e. 4

Score: 10 / 10

#### Question 5 (10 points)

Koliko ima temeljnih petlji u zadanom grafu?

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
---------------	------------------	------------------	----------------

-50.0%			a.	1
-50.0%			b.	2
100.0%			c.	3
-50.0%			d.	4
-50.0%			e.	5

Score: 10 / 10

**Total score:** 20 / 50 = 40.0%

[View Results](#)

### Jednadžbe mreža.

User ID: mprstec

Attempt: 1 / 1

Out of: 50

Started: April 13, 2004 17:28 Finished: April 13, 2004 17:32 Time spent: 4 min. 4 sec.

Student finished 5 min. 56 sec. ahead of the 10 min. time limit.

### Question 1 (10 points)

Što se podrazumijeva pod pojmom "riješiti električnu mrežu" ?

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. postaviti sve jednadžbe KZN ili KZS
-50.0%			b. odrediti valne oblike svih napona u granama mreže
-50.0%			c. odrediti valne oblike svih konturnih struja i napona čvorova
100.0%			d. odrediti valne oblike svih struja i svih napona u granama mreže



-50.0%



e. odrediti valne oblike svih konturnih struja ili svih napona čvorova

Score: 10 / 10

### Question 2 (10 points)

Koliko iznosi najmanji broj linearno nezavisnih jednažbi KZN za mrežu od  $N_b$  grana i  $N_v$  čvorova?

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. $N_b - (N_v + 1)$
-50.0%			b. $N_b - N_v$
-50.0%			c. $N_v - 1$
100.0%			d. $N_b - (N_v - 1)$
-50.0%			e. $N_v - (N_b - 1)$

Score: 10 / 10

### Question 3 (10 points)

Koje su od navedenih tvrdnji istinite?

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. Ako postoji više čvorova u nekoj el. mreži, odabirom dva referentna na suprotnim stranama mreže postupak rješavanja KZN se pojednostavljuje.
-50.0%			b. Ako tražimo samo struju jedne grane u el. mreži možemo koristiti samo one linearno nezavisne jednažbe u kojima se

			pojavljuju konturne struje koja prolaze određenom granom.
100.0%	▶	▶	c. Ako u nekoj grani mreže postoji nezavisni izvor koji daje struju $I_a$ , iznos konturne struje koja obilazi i tu granu je $I_a$ .
-50.0%			d. Da bi odredili napon grane neke el. mreže uvijek oduzimamo napon čvora na većem potencijalu od napona čvora na manjem potencijalu.

Score: 10 / 10

#### Question 4 (10 points)

Za mrežu zadanu slikom vrijedi:

Student response:	Percent Value	Correct Response	Student Response	Answer Choices
	50.0%	▶	▶	a. $-(u_{v1}(s)-u_{v3}(s))/R_3 - (u_{v2}(s)-u_{v3}(s))/R_4 + u_{v3}(s)/R_6 = 0$
	-50.0%			b. $-(u_{v1}(s)-u_{v3}(s))/R_3 - (u_{v2}(s)-u_{v3}(s))/R_4 - u_{v3}(s)/R_6 = 0$
	-50.0%			c. $(u_{v1}(s)-u_{v3}(s))/R_3 - (u_{v2}(s)-u_{v3}(s))/R_4 - u_{v3}(s)/R_6 = 0$
	50.0%	▶	▶	d. $-(u_{v1}-u_{v3})/R_3 - (u_{v2}-u_{v3})/R_4 + u_{v3}/R_6 = 0$

Score: 10 / 10

**Question 5** (10 points)

Za mrežu sa slike vrijedi:

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. napon grane 2 = - napon grane 1 = - napon čvora 1
50.0%			b. napon grane 2 = - napon grane 1 = napon čvora 1
-50.0%			c. napon grane 4 = napon grane 5 = - napon čvora 2
50.0%			d. napon grane 3 = napon čvora 2 - napon čvora 1

Score: 10 / 10

Total score: 50 / 50 = 100.0%

[View Results](#)

**Osnovi topološke analize električnih mreža.**

User ID: mprstec

Attempt: 1 / 1

Out of: 50



Started: April 13, 2004 17:33 Finished: April 13, 2004 17:34 Time spent: 1 min. 5 sec.

Student finished 8 min. 55 sec. ahead of the 10 min. time limit.

**Question 1** (10 points)

Kako glasi jednačba za matričnu impedanciju grana?

Student response:



Percent Value	Correct Response	Student Response	Answer Choices
100.0%			a. $Z_b(s) = R_b + s \cdot L_b + (1/s)D_b$
-50.0%			b. $Z_b(s) = R_b + 1/(sL_b) + s \cdot D_b$
-50.0%			c. $Z_b(s) = 1/r_b + 1/(s \cdot L_b) + s/D_b$
-50.0%			d. $Z_b(s) = 1/(r_b + s \cdot L_b + D_b/s)$

Score: 10 / 10

### Question 2 (10 points)

Graf je planaran ako se ne može prikazati u ravnini (tako da se izvan čvorišta ni jedna grana ne ukrštava s drugom). Da li je definicija ispravna?

Student response:



Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. da
100.0%			b. ne

Score: 10 / 10

### Question 3 (10 points)

Ako je broj čvorova 4, a broj grana 5, koliki rang ima spojna matrica  $B_a$ ?

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. 4
-50.0%			b. 3
100.0%			c. 2
-50.0%			d. 1

Score: 10 / 10

**Question 4** (10 points)

Koliko ima spona u zadanom grafu?

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. 1
100.0%			b. 2
-50.0%			c. 3
-50.0%			d. 5
-50.0%			e. 7

Score: 10 / 10

**Question 5** (10 points)

Zadana je reducirana matrica incidencije grafa.

```

1  1  0  0  0  0  1
-1 -1  1  0  0  0  0
0  0 -1  0  1  0  0
0  0  0 -1 -1 -1  0

```

Da li grane 1,3,5,6 sacinjavaju stablo?

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
50.0%			a. Da
-50.0%			b. Ne
50.0%			c. Da, jer je njihova determinanta submatrice razlicita od nule
-50.0%			d. Ne, jer je njihova determinanta submatrice jednaka nuli

Score: 10 / 10

Total score: 50 / 50 = 100.0%

[View Results](#)

### Jednadžbe mreža.

User ID: aloncarek

Attempt: 1 / 1

Out of: 50

Started: April 13, 2004  
17:36

Finished: April 13, 2004  
17:42



Time spent: 6 min. 44  
sec.

Student finished 3 min. 16 sec. ahead of the 10 min. time limit.

### Question 1 (10 points)

Pretpostavimo li da rješavamo mrežu od Nb grana i Nv čvorova. Za točno rješenje mreže dobili bi :

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. Nv napona grana i Nb struja grana
100.0%			b. Nb napona grana i Nb struja grana
-50.0%			c. Nv napona grana i Nv struja grana
-50.0%			d. Nb napona grana i Nv struja grana
-50.0%			e. ništa od navedenog

Score: 10 / 10

### Question 2 (10 points)

Koliko iznosi najveći broj linearno nezavisnih jednadžbi KZS za mrežu od Nb grana i Nv čvorova?

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. Nb - (Nv + 1)
-50.0%			b. Nb - Nv

100.0%			c. $N_v - 1$
-50.0%			d. $N_b - (N_v - 1)$
-50.0%			e. $N_v - (N_b - 1)$

Score: 10 / 10

### Question 3 (10 points)


Jednadžbe stanja koristimo u analizi nekih električnih mreža da bi:

Student response:	Percent Value	Correct Response	Student Response	Answer Choices
	-50.0%			a. odredili izraze za struje i napone
	100.0%			b. odredili izraze za početne uvjete
	-50.0%			c. odredili iznose početnih struja i napona na L i C
	-50.0%			d. odredili linearnost odnosno nelinearnost mreže

Score: 10 / 10

### Question 4 (10 points)

Kako glasi vektor strujnih izvora?

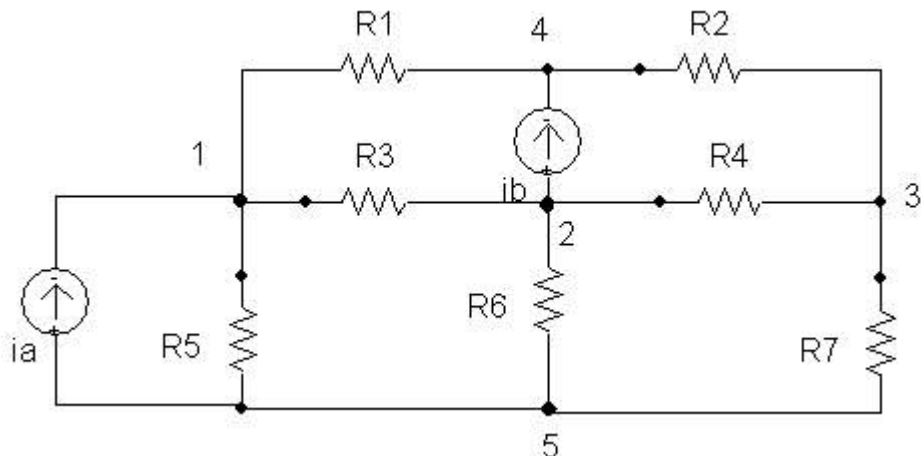

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
100.0%			a. [ -ia ib 0 -ib ia ]
-50.0%			b. [ 0 ib ia -ib -ia ]
-50.0%			c. [ -ia -ib 0 -ib ia ]
-50.0%			d. [ ia -ib ib ib -ia ]

Score: 10 / 10

### Question 5 (10 points)

Postavi jednadžbu prve i treće petlje mreže na slici.

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. a)
-50.0%			b. b)
-50.0%			c. c)
-50.0%			d. d)
100.0%			e. nijedno od navedenog

Score: 10 / 10

Total score: 50 / 50 = 100.0%

[View Results](#)

### Osnovi topološke analize električnih mreža.

User ID: aloncarek

Attempt: 1 / 1

Out of: 50

Started: April 13, 2004 17:43 Finished: April 13, 2004 17:46 Time spent: 3 min. 0 sec.

Student finished 7 min. 0 sec. ahead of the 10 min. time limit.



**Question 1** (10 points)

Kako glasi matricna impedancija petlji?

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. $Z_m(s) = Z_b(s) * B^T$
-50.0%			b. $Z_m(s) = A * Z_b(s) * A^T$
100.0%			c. $Z_m(s) = B * Z_b(s) * B^T$
-50.0%			d. $Z_m(s) = A * Z_b(s)$

Score: 10 / 10

**Question 2** (10 points)

Grana bez čvorova može biti graf.

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. točno
100.0%			b. netočno

Score: 10 / 10

**Question 3** (10 points)

Što od slijedećeg ne može biti KZS za čvor?

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. $i_1 + i_2 - i_3 + 0 + 0 = 0$
-50.0%			b. $-i_1 + 0 + 0 + i_4 + 0 = 0$
-50.0%			c. $0 - i_2 + 0 - i_4 - i_5 = 0$
100.0%			d. $1 + 0 + 2*i_3 + 0 + i_5 = 0$

Score: 10 / 10

**Question 4** (10 points)

Da li je graf planaran?


Student response:

Percent Value	Correct Response	Student Response	Answer Choices
100.0%	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	a. Da
-50.0%	<input type="checkbox"/>	<input type="checkbox"/>	b. Ne

Score: 10 / 10

**Question 5** (10 points)

Koliko ima spona u zadanom grafu?

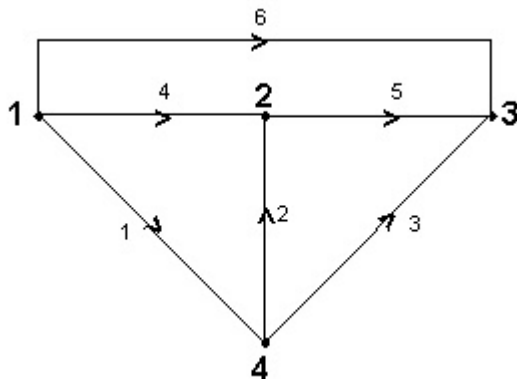

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%	<input type="checkbox"/>	<input type="checkbox"/>	a. 1
-50.0%	<input type="checkbox"/>	<input type="checkbox"/>	b. 2
100.0%	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	c. 3
-50.0%	<input type="checkbox"/>	<input type="checkbox"/>	d. 4
-50.0%	<input type="checkbox"/>	<input type="checkbox"/>	e. 5

Score: 10 / 10

**Total score:**     **50 / 50 = 100.0%**

[View Results](#)

### Jednadžbe mreža.

**User ID:** llazic

**Attempt:** 1 / 1

**Out of:** 50

**Started:** April 13, 2004  
17:47

**Finished:** April 13, 2004  
17:52

**Time spent:** 4 min. 40  
sec.

Student finished 5 min. 20 sec. ahead of the 10 min. time limit.

### Question 1 (10 points)

Koje su nepoznate varijable u jednadžbama stanja?

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. naponi
-50.0%			b. struje
100.0%	▶	▶	c. početni uvjeti
-50.0%			d. izvori
-50.0%			e. naponi i struje

**Score:**     10 / 10

### Question 2 (10 points)

Koliko iznosi najveći broj linearno nezavisnih jednadžbi KZS za mrežu od Nb grana i Nv čvorova?

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. $Nb - (Nv + 1)$
-50.0%			b. $Nb - Nv$
100.0%	▶	▶	c. $Nv - 1$
-50.0%			d. $Nb - (Nv - 1)$
-50.0%			e. $Nv - (Nb - 1)$

Score: 10 / 10

**Question 3** (10 points)

Koje su od navedenih tvrdnji istinite ?

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. Prilikom rješavanja mreža KZN moramo sve izvore pretvoriti u naponske
-50.0%			b. Prilikom rješavanja mreža KZS moramo sve izvore pretvoriti u strujne
100.0%			c. Ako postoje i strujni i naponski izvori u mreži ne mormo ih pretvarati jer se ona može riješiti i KZN i KZS
-50.0%			d. Ako pretvaramo izvore u el. mreži svi moraju biti istog tipa, dakle svi naponski ili svi strujni

Score: 10 / 10

**Question 4** (10 points)

Kako glasi vektor strujnih izvora?

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
100.0%			a. [ -ia ib 0 -ib ia ]
-50.0%			b. [ 0 ib ia -ib -ia ]

-50.0%

c. [ -ia -ib 0 -ib ia ]

-50.0%



d. [ ia -ib ib ib -ia ]

Score: 10 / 10

### Question 5 (10 points)

Postavi jednažbu druge i treće petlje mreže na slici u Laplace-ovoj domeni.

Student response:

Percent Value	Correct Response	Student Response	Answer Choices	
100.0%			a.	a)
-50.0%			b.	b)
-50.0%			c.	c)
-50.0%			d.	d)

Score: 10 / 10

---

**Total score:** 50 / 50 = 100.0%

[View Results](#)

### Osnovi topološke analize električnih mreža.

User ID: llazic

Attempt: 1 / 1

Out of: 50



Started: April 13, 2004  
17:53

Finished: April 13, 2004  
17:54

Time spent: 1 min. 22  
sec.

Student finished 8 min. 38 sec. ahead of the 10 min. time limit.

### Question 1 (10 points)

 je vektor početnih napona na kapacitetima s elementom .

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
33.4%			a. u j-tom redu, ako j-ta grana u mrezi ima kapacitet s pocetnim naponom ucj(0)
33.3%			b. pozitivnim, ako se njegov polaritet podudara sa polaritetom j-te grane u grafu
33.3%			c. negativnim, ako je njegov polaritet suprotan od polariteta j-te grane u grafu
-50.0%			d. niti jedan odgovor nije točan

Score: 10 / 10

## Question 2 (10 points)

Topologija je posebna grana jedne znanstvene discipline. Koje?

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. primjenjene fizike
100.0%			b. primjenjene matematike
-50.0%			c. elektrotehnike

Score: 10 / 10

## Question 3 (10 points)

Ako je broj čvorova 4, a broj grana 5, koliki rang ima spojna matrica Ba?

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. 4
-50.0%			b. 3

100.0%			c.	2
-50.0%			d.	1

Score: 10 / 10

#### Question 4 (10 points)

Koliko ima spona u zadanom grafu?

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. 1
100.0%			b. 2
-50.0%			c. 3
-50.0%			d. 5
-50.0%			e. 7

Score: 10 / 10

#### Question 5 (10 points)

Kako glasi spojna matrica za zadani graf? (2,5,6 su spona)

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
25.0%			a. $\begin{bmatrix} 1 & 1 & 0 & -1 & 0 & 0 \\ -1 & 0 & -1 & 1 & 1 & 0 \\ -1 & 0 & -1 & 0 & 0 & 1 \end{bmatrix}$
25.0%			b. $\begin{bmatrix} -1 & -1 & 0 & 1 & 0 & 0 \\ -1 & 0 & -1 & 1 & 1 & 0 \\ -1 & 0 & -1 & 0 & 0 & 1 \end{bmatrix}$
25.0%			c. $\begin{bmatrix} 1 & 1 & 0 & -1 & 0 & 0 \\ 1 & 0 & 1 & -1 & -1 & 0 \\ 1 & 0 & 1 & 0 & 0 & -1 \end{bmatrix}$
25.0%			d. $\begin{bmatrix} 1 & 1 & 0 & -1 & 0 & 0 \\ -1 & 0 & -1 & 1 & 1 & 0 \\ 1 & 0 & 1 & 0 & 0 & -1 \end{bmatrix}$

-50.0%

e.  $\begin{bmatrix} -1 & -1 & 0 & 1 & 0 & 0 \\ 1 & 0 & 1 & 1 & -1 & 0 \\ -1 & 0 & 1 & 0 & 0 & -1 \end{bmatrix}$

Score: 10 / 10

Total score: 50 / 50 = 100.0%

[View Results](#)

### Jednadžbe mreža.

User ID: mvavrous

Attempt: 1 / 1

Out of: 50



Started: April 13, 2004 17:55 Finished: April 13, 2004 18:00 Time spent: 5 min. 2 sec.

Student finished 4 min. 58 sec. ahead of the 10 min. time limit.

### Question 1 (10 points)

Koje su nepoznate varijable u jednadžbama stanja?

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. naponi
-50.0%			b. struje
100.0%			c. početni uvjeti
-50.0%			d. izvori
-50.0%			e. naponi i struje

Score: 10 / 10

### Question 2 (10 points)

Koliko iznosi najveći broj linearno nezavisnih jednadžbi KZS za mrežu od  $N_b$  grana i  $N_v$  čvorova?

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
---------------	------------------	------------------	----------------



-50.0%			a. $N_b - (N_v + 1)$
-50.0%			b. $N_b - N_v$
100.0%	▶	▶	c. $N_v - 1$
-50.0%			d. $N_b - (N_v - 1)$
-50.0%			e. $N_v - (N_b - 1)$

Score: 10 / 10

### Question 3 (10 points)

Što je  $w(t)$  u jednažbama stanja ?

Student response:	Percent Value	Correct Response	Student Response	Answer Choices
	-50.0%			a. vektor stanja
	100.0%	▶	▶	b. vektor pobudnih funkcija
	-50.0%			c. vektor odzivnih funkcija
	-50.0%			d. ništa od navedenog

Score: 10 / 10

### Question 4 (10 points)



Kako glasi vektor strujnih izvora?

Student response:	Percent Value	Correct Response	Student Response	Answer Choices
	-50.0%			a. $\begin{bmatrix} i_a & i_b & -i_a \\ i_c & -i_b & -i_c \end{bmatrix}$
	-50.0%			b. $\begin{bmatrix} -i_a & i_a & i_b & - \\ i_b & i_c & -i_c \end{bmatrix}$
	100.0%	▶	▶	c. $\begin{bmatrix} -i_a & i_a & -i_b \\ i_b & i_c & -i_c \end{bmatrix}$
	-50.0%			d. $\begin{bmatrix} i_a & i_a & i_b & i_b & i_c & i_c \end{bmatrix}$

Score: 10 / 10

### Question 5 (10 points)

Za mrežu zadanu slikom vrijedi:



Student response:	Percent Value	Correct Response	Student Response	Answer Choices
	-50.0%			a. $-(uv1(s)+ug1(s))/R1 + uv2(s)/R2 - 1/sL3 (uv4(s)-uv1(s)) - iL3(0)/s = 0$
	-50.0%			b. $uv3(s)/R4 - sC5 (uv4(o)-uv3(0)) + C5 (uv4(s)-uv3(s)) + ig6 = 0$
	-50.0%			c. $1/sL3 (uv4(s)-uv1(s)) + iL3(0)/s - C5 (uv4(s)-uv3(s)) + sC5 (uv4(0)-uv3(0)) - ig6 = 0$
	-50.0%			d. sve navedeno
	100.0%			e. nista od navedenog

Score: 10 / 10

Total score: 50 / 50 = 100.0%

### Question 1 (10 points)

Matricna jednadzba KZN glasi:


 
Student response:	Percent Value	Correct Response	Student Response	Answer Choices
	-50.0%			a. $A*Ib(s)=0$
	100.0%			b. $B*Ub(s)=0$
	-50.0%			c. $A*Ub(s)=0$
	-50.0%			d. $B*Ib(s)=0$

Score: 10 / 10

**Question 2** (10 points)

Što je singularno čvorište?

Student response:



Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. početno čvorište
-50.0%			b. završno čvorište
100.0%			c. čvorište koje nije povezano s nijednom granom

Score: 10 / 10

**Question 3** (10 points)

Što od slijedećeg ne može biti KZN?

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. $-u_1 + u_2 + 0 - u_4 + 0 = 0$
-50.0%			b. $0 - u_2 - u_3 + 0 + u_5 = 0$
-50.0%			c. $-u_1 + 0 - u_3 - u_4 + u_5 = 0$
100.0%			d. $1 + 0 + u_3 + 1 - u_5 = 0$

Score: 10 / 10

**Question 4** (10 points)

Koliko graf ima stablenih grana?

Student response:


Percent	Correct	Student	Answer Choices
---------	---------	---------	----------------

Value	Response	Response	
-50.0%			a. 0
-50.0%			b. 1
-50.0%			c. 2
100.0%			d. 3
-50.0%			e. 4

Score: 10 / 10

### Question 5 (10 points)

Koliko ima spona u zadanom grafu?

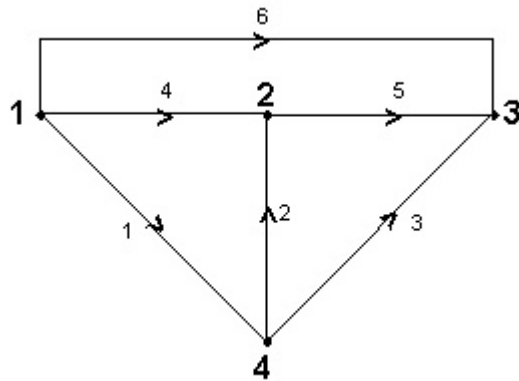

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. 0
-50.0%			b. 1
-50.0%			c. 2
100.0%			d. 3
-50.0%			e. 4

Score: 10 / 10

**Total score: 50 / 50 = 100.0%**

**Question 1** (10 points)

Koliko najmanje linearno nezavisnih jednađbi ćemo koristiti prilikom rješavanja mreže s 5 čvorova koristeći KZS ?

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. 5
100.0%			b. 4
-50.0%			c. 6
-50.0%			d. ne možemo odrediti bez poznavanja broja grana mreže
-50.0%			e. ne možemo odrediti bez poznavanja topološke strukture mreže

Score: 10 / 10

**Question 2** (10 points)

Koje su nepoznate varijable u jednađbama čvorova?

Student response:



Percent Value	Correct Response	Student Response	Answer Choices
100.0%			a. naponi
-50.0%			b. struje
-50.0%			c. početni uvjeti
-50.0%			d. izvori
-50.0%			e. naponi i struje

Score: 10 / 10

**Question 3** (10 points)

Od koliko čvorova se sastoji mreža sa 6 grana ako smo analizom mreže dobili 3 linearno nezavisne jednađbe KZS ?


Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. 5
100.0%			b. 4
-50.0%			c. 3
-50.0%			d. 8
-50.0%			e. ne možemo odrediti


Score: 10 / 10

#### Question 4 (10 points)

Za mrežu na slici vrijedi:

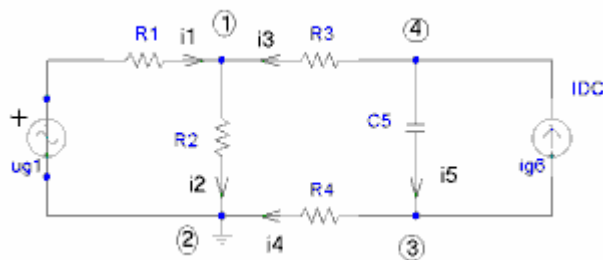

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. $(u_{v4}(s)-u_{v1}(s))/R3 + iL3(0)/s + sC5(u_{v4}(s)-u_{v3}(s)) - C5(u_{v4}(0)-u_{v3}(0)) + (u_{v4}(s)-u_{v3}(s))/R6 = 0$
-50.0%			b. $(u_{v4}(s)-u_{v1}(s))/R3 + C5(u_{v4}(s)-u_{v3}(s)) - sC5(u_{v4}(0)-u_{v3}(0)) + (u_{v4}(s)-u_{v3}(s))/R6 = 0$
100.0%			c. $u_{v3}(s)/R4 - sC5(u_{v4}(s)-u_{v3}(s)) + C5(u_{v4}(0)-u_{v3}(0)) - i_{g6} = 0$
-50.0%			d. $u_{v3}(s)/R4 -$

			$sC5(uv4(s)-uv3(s)) + C5(uv4(0)-uv3(0)) - ig6(0) = 0$
--	--	--	---

-50.0%




e. niti jedna od navedenih jednađžbi

Score: -5 / 10

**Question 5** (10 points)

Za mrežu sa slike vrijedi

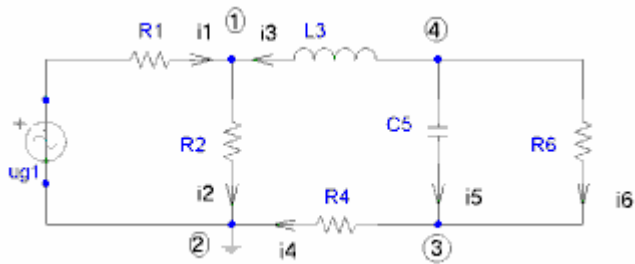



Student response:	Percent Value	Correct Response	Student Response	Answer Choices
-50.0%				a. $-(uv1(s)+ug(s))/R1 - uv1(s)/R2 - 1/sL3 (uv4(s)-uv1(s)) + iL3(0)/s = 0$
-50.0%				b. $-(uv1(s)+ug(s))/R1 - uv1(s)/R2 + 1/sL3 (uv4(s)-uv1(s)) + iL2(0)/s = 0$
-50.0%				c. $-(uv1(s)+ug(s))/R1 + uv1(s)/R2 + 1/sL3 (uv4(s)-uv1(s)) - iL2(0)/s = 0$
100.0%				d. $-(uv1(s)+ug(s))/R1 - uv1(s)/R2 - 1/sL3 (uv4(s)-uv1(s)) - iL2(0)/s = 0$

Score: 10 / 10

**Question 1** (10 points)

Koliko iznosi broj linearno nezavisnih jednažbi napona u mreži sa 5 čvorova?

Student response:



Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. 4
-50.0%			b. 5
100.0%			c. ne može se odrediti bez poznavanja broja grana u mreži
-50.0%			d. 3
-50.0%			e. ne može se odrediti bez poznavanja topološke strukture mreže

Score: -5 / 10

**Question 2** (10 points)

Koliko iznosi najmanji broj linearno nezavisnih jednažbi KZN za mrežu od  $N_b$  grana i  $N_v$  čvorova?

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. $N_b - (N_v + 1)$
-50.0%			b. $N_b - N_v$
-50.0%			c. $N_v - 1$
100.0%			d. $N_b - (N_v - 1)$
-50.0%			e. $N_v - (N_b - 1)$



Score: 10 / 10

**Question 3** (10 points)



Ako kroz neku granu el. mreže prolaze dvije konturne struje  $I_a$  i  $I_b$  različitog smjera, a pretpostavljen smjer struje  $I_g$  grane koju tražimo je istog smjera kao  $I_a$ , koji izraz točno opisuje struju grane  $I_g$  ?

Student response:



Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. $I_g = -I_a - I_b$
-50.0%			b. $I_g = I_a + I_b$
-50.0%			c. $I_g = -I_a + I_b$
100.0%			d. $I_g = I_a - I_b$
-50.0%			e. ništa od navedenog

Score: 10 / 10

### Question 1 (10 points)

Koliko ima linearno nezavisnih jednadžbi KZS u mreži sa 4 grane?

Student response:



Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. 4
-50.0%			b. 3
-50.0%			c. 2
100.0%			d. ništa od navedenog

Score: 10 / 10

### Question 2 (10 points)

Koje su nepoznate varijable u jednadžbama čvorova?

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
100.0%			a. naponi
-50.0%			b. struje
-50.0%			c. početni uvjeti
-50.0%			d. izvori
-50.0%			e. naponi i struje

Score: 10 / 10

### Question 3 (10 points)

Jednadžbe stanja koristimo u analizi nekih električnih mreža da bi:


Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. odredili izraze za struje i napone
100.0%	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	b. odredili izraze za početne uvjete
-50.0%			c. odredili iznose početnih struja i napona na L i C
-50.0%			d. odredili linearnost odnosno nelinearnost mreže

Score: 10 / 10

### Question 4 (10 points)

Za mrežu na slici vrijedi

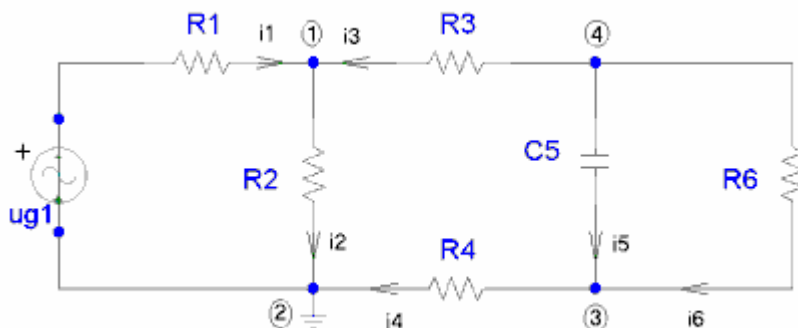

Student response:


Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. $(u_{v4}(s)-u_{v1}(s))/R3 +$

-50.0%			$iL3(0)/s + sC5(uv4(s)-uv3(s)) - C5(uv4(0)-uv3(0)) + (uv4(s)-uv3(s))/R6 = 0$
100.0%	▶	▶	b. $(uv4(s)-uv1(s))/R3 + C5(uv4(s)-uv3(s)) - sC5(uv4(0)-uv3(0)) + (uv4(s)-uv3(s))/R6 = 0$ c. $uv3(s)/R4 - sC5(uv4(s)-uv3(s)) + C5(uv4(0)-uv3(0)) - (uv4(s)-uv3(s))/R6 = 0$
-50.0%			d. niti jedna od navedenih jednađžbi

Score: 10 / 10

Question 5 (10 points)

Za mrežu na slici vrijedi

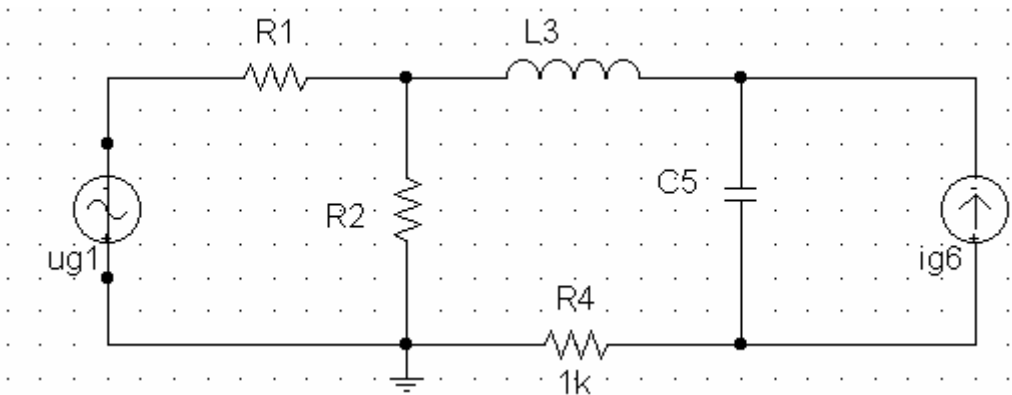

Student response:	Percent Value	Correct Response	Student Response	Answer Choices
	-50.0%			a. $uv3/R4 - C5 \, d(uv4-uv3)/dt - (uv4-uv3)/R6 = 0$
	-50.0%			b. $uv3/R4 - C5 \, d(uv4-uv3)/dt - ig6 = 0$

100.0%			c. $uv3/R4 - C5 \frac{d(uv4-uv3)}{dt} + ig6 = 0$
-50.0%			d. $uv3/R4 + C5 \frac{d(uv4-uv3)}{dt} - ig6 = 0$
-50.0%			e. ništa od navedenog

Score: 10 / 10

Matriča admitancija čvorova glasi:

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. $Y_n(s) = A * Z_b(s)$
100.0%			b. $Y_n(s) = A * [Z_b(s)]^{-1} * A^T$
-50.0%			c. $Y_n(s) = A^{(-1)} * [Z_b(s)]^{(-1)}$
-50.0%			d. $Y_n(s) = A^T * [Z_b(s)]^{(-1)}$

Score: 10 / 10

### Question 2 (10 points)

Može li čvor bez grane biti smatran grafom?

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
100.0%			a. može
-50.0%			b. ne može

Score: 10 / 10

### Question 3 (10 points)

Koje od navedenih naziva nije ime za matrice mreža?


Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. matrica incidencije
-50.0%			b. spojna matrica
100.0%	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	c. matrica dedukcije
-50.0%			d. rastavna matrica

Score: 10 / 10
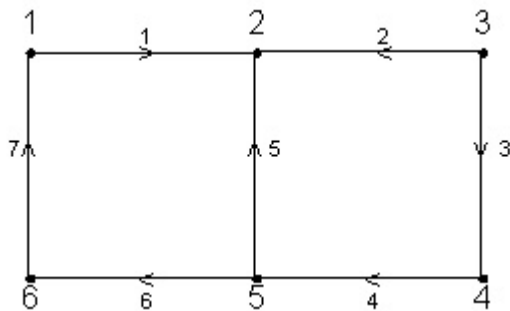
#### Question 4 (10 points)

Koliko ima stablenih grana u zadanom grafu?




Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. 1
-50.0%			b. 2
-50.0%			c. 3
100.0%	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	d. 5
-50.0%			e. 7

Score: 10 / 10

#### Question 5 (10 points)

Koliko ima spona u zadanom grafu?

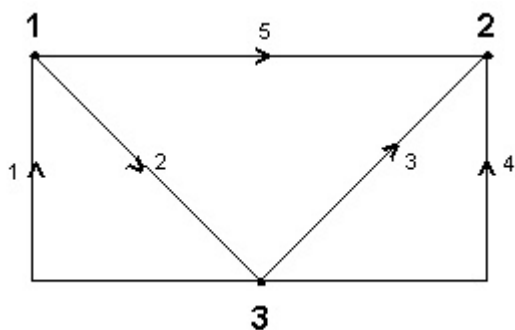

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. 1
-50.0%			b. 2
100.0%	▶	▶	c. 3
-50.0%			d. 4
-50.0%			e. 5

Score: 10 / 10

### Question 1 (10 points)

U mreži sa 6 grana i 4 čvora broj linearno nezavisnih jednađbi struja(KZS) i napona(KZN) je:

Student response:

 

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. KZS=5, KZN=5
-50.0%			b. KZN=5, KZS=3
100.0%	▶	▶	c. KZS=3, KZN=3
-50.0%			d. KZN=3, KZS=5
-50.0%			e. ne može se odrediti bez poznavanja topološke strukture mreže

Score: 10 / 10

**Question 2** (10 points)

O čemu ovisi broj linearno nezavisnih jednažbi KZS ?

Student response:



Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. o broju elemenata u granama
-50.0%			b. o broju grana
100.0%			c. o broju čvorova
-50.0%			d. o broju čvorova i grana
-50.0%			e. ništa od navedenog

Score: 10 / 10

**Question 3** (10 points)

Otpor  $R$  u grani neke mreže priključen je na čvorove  $A$  i  $B$ . Čvor  $B$  je na većem potencijalu od čvora  $A$ , a pretpostavljeni smjer struje kroz granu je od čvora  $A$  prema čvoru  $B$ . Izraz za opis struje  $I_r$  je:

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. $I_r = (U_b - U_a)/R$
-50.0%			b. $I_r = -(U_b + U_a)/R$
100.0%			c. $I_r = (U_a - U_b)/R$
-50.0%			d. $I_r = (U_b + U_a)/R$

Score: 10 / 10

**Question 4** (10 points)

Matrica impedancije bit će simetrična ako je mreža

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
50.0%			a. sastavljena od kapaciteta, induktiviteta, otpora i neovisnih izvora
50.0%			b. recipročna
0.0%			c. bez induktiviteta i kapaciteta

Score: 5 / 10

### Question 5 (10 points)

Postavi jednadžbu prve i druge petlje mreže na slici u Laplace-ovoj domeni.

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
100.0%			a. a)
-50.0%			b. b)
-50.0%			c. c)
-50.0%			d. d)

Score: 10 / 10

---

**Total score:** 45 / 50 = 90.0%

### Question 1 (10 points)

Kako glasi matricna impedancija petlji?

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. $Z_m(s) = Z_b(s) * B^T$



-50.0%			b. $Z_m(s) = A * Z_b(s) * A^T$
100.0%	▶	▶	c. $Z_m(s) = B * Z_b(s) * B^T$
-50.0%			d. $Z_m(s) = A * Z_b(s)$

Score: 10 / 10

### Question 2 (10 points)

Koje su tvrdnje ispravne?

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
50.0%	▶	▶	a. Čvorište i grana koja spaja to čvorište incidentni su jedan s drugim.
50.0%	▶	▶	b. Broj koji kaže koliko je grana incidentno s nekim čvorištem, naziva se red čvorišta.
-50.0%			c. Dvije su grane u seriji, ako su incidentne s istim parom čvorišta.
-50.0%			d. Dvije grane su paralelne, ako imaju točno jedno zajedničko čvorište, koje nije incidentno ni s jednom daljnjom granom.
-50.0%			e. Nijedna od navedenih.

Score: 10 / 10

**Question 3** (10 points)

Ako je broj čvorova 4, a broj grana 5, koliko jednađbi KZS nam je potrebno?

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
100.0%			a. 3 od 4
-50.0%			b. 3 od 5
-50.0%			c. 4 od 5
-50.0%			d. 4 od 4

Score: 10 / 10

**Question 4** (10 points)

Koliko graf ima stablenih grana?


Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. 0
-50.0%			b. 1
-50.0%			c. 2
100.0%			d. 3
-50.0%			e. 4

Score: 10 / 10

**Question 5** (10 points)

Koliko ima spona u zadanom grafu?

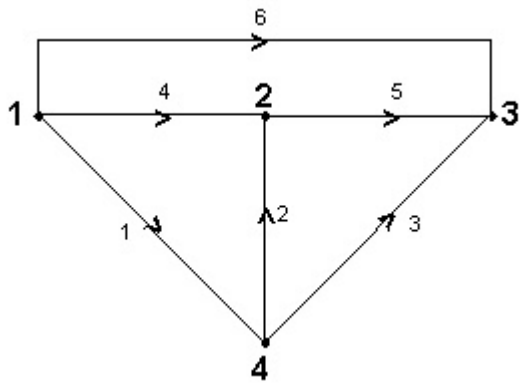

Student response:

Percent Value	Correct Response	Student Response	Answer Choices	
-50.0%			a.	1
-50.0%			b.	2
100.0%	▶	▶	c.	3
-50.0%			d.	4
-50.0%			e.	6

Score: 10 / 10



---

**Total score:** 50 / 50 = 100.0%

**Question 1** (10 points)

Pretpostavimo li da rješavamo mrežu od  $N_b$  grana i  $N_v$  čvorova. Za točno rješenje mreže dobili bi :

Student response:



Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. $N_v$ napona grana i $N_b$ struja grana
100.0%			b. $N_b$ napona grana i $N_b$ struja grana
-50.0%			c. $N_v$ napona grana i $N_v$ struja grana
-50.0%			d. $N_b$ napona grana i $N_v$ struja grana
-50.0%			e. ništa od navedenog

Score: -5 / 10

**Question 2** (10 points)

Ako nije zadan, kako se odabire referentni čvor korištenjem KZN?

Student response:

 

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. na čvoru na kojem je spojena negativna stezaljka naponskog ili strujnog izvora
-50.0%			b. na čvoru u koji ulazi najviše struja
100.0%			c. proizvoljno
-50.0%			d. na čvoru iz kojeg izlazi najviše struja
-50.0%			e. ništa od navedenog

Score: 10 / 10

**Question 3** (10 points)

Koje su od navedenih tvrdnji istinite?

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. Ako postoji više čvorova u nekoj el. mreži, odabirom dva referentna na suprotnim stranama mreže postupak rješavanja KZN se pojednostavljuje.
-50.0%			b. Ako tražimo samo struju jedne grane u el. mreži možemo koristiti samo one linearno nezavisne jednačbe u kojima se pojavljuju konturne struje koja prolaze određenom granom.
100.0%			c. Ako u nekoj grani mreže postoji nezavisni izvor koji daje struju $I_a$ , iznos konturne struje koja obilazi i tu granu je $I_a$ .
-50.0%			d. Da bi odredili napon grane neke el. mreže uvijek oduzimamo napon čvora na većem potencijalu od napona čvora na manjem potencijalu.

Score: 10 / 10

**Question 4** (10 points)

Za mrežu na slici odredi jednačbe petlji.

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
100.0%			a. $I_1 (R_g + 1/j\omega C) = U_0$ $I_2 (R_k + R_p + R_l) = -U_g$
-50.0%			b. $I_1 (R_g + 1/j\omega C) = U_0 + U_z$ $I_2 (R_k + R_p + R_l) = -U_g$
-50.0%			c. $I_1 (R_g + 1/j\omega C) = U_0$ $I_2 (R_k + R_p + R_l) = -U_g + U_z$
-50.0%			d. $I_1 (R_g + 1/j\omega C) = U_0 + U_z$ $I_2 (R_k + R_p + R_l) = -U_g + U_z$
-50.0%			e. Točan odgovor nije ponuđen.

Score: 10 / 10

### Question 5 (10 points)

Postavi jednažbu treće petlje mreže na slici u Laplace-ovoj domeni.



Student response:

Percent Value	Correct Response	Student Response	Answer Choices
100.0%			a. a)
-50.0%			b. b)
-50.0%			c. c)
-50.0%			d. d)
-50.0%			e. e)

Score: 10 / 10

Total score: 35 / 50 = 70.0%

KZN u matricnoj normi glasi:



Student response:	Percent Value	Correct Response	Student Response	Answer Choices
	100.0%			a. $U_b(s) = U_g(s) + Z_b(s) * I_b(s) + u_c(0)/s - L_b * i_b(0)$
	-50.0%			b. $U_b(s) = U_g(s) + Z_b(s) * I_b(s)$
	-50.0%			c. $U_b(s) = U_g(s) + Z_b(s) * I_b(s) + u_c(0)/s$
	-50.0%			d. $0 = U_g(s) + Z_b(s) * I_b(s) + u_c(0)/s - L_b * i_b(0)$

Score: -5 / 10

### Question 2 (10 points)

Da li je slijedeća definicija ispravna?



Pod grafom smatramo skup čvorova zajedno sa skupom grana sa takovim svojstvima,  
da svaka grana završava na svakom kraju sa čvorom.

Student response:	Percent Value	Correct Response	Student Response	Answer Choices
	100.0%			a. točno
	-50.0%			b. netočno

Score: 10 / 10

### Question 3 (10 points)

Pišući KZS za neku mrežu, pišemo sistem linearnih jednačbi za sve čvorove. Što su varijable, a što koeficijenti?

Student response:	Percent Value	Correct Response	Student Response	Answer Choices
	100.0%			a. varijable su struje u



			granama, koeficijenti 1, -1, 0
-50.0%			b. varijable su samo struje u sponama, koeficijenti mogu biti bilo koji brojevi
-50.0%			c. varijable su naponi u čvorovima, koeficijenti mogu biti bilo koji brojevi
-50.0%			d. varijable su struje u granama, koeficijenti mogu biti bilo koji brojevi

Score: 10 / 10

#### Question 4 (10 points)

Koliko graf ima spona?

Student response:


Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. 0
100.0%			b. 1
-50.0%			c. 2
-50.0%			d. 3
-50.0%			e. 4

Score: 10 / 10

#### Question 5 (10 points)

Koliko ima spona u zadanom grafu?



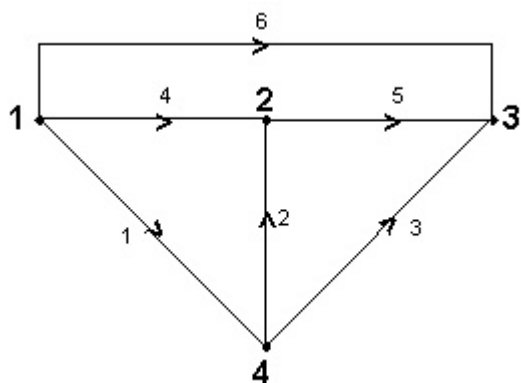

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. 1
-50.0%			b. 2
100.0%	▶	▶	c. 3
-50.0%			d. 4
-50.0%			e. 6

Score: 10 / 10

### Question 1 (10 points)

Koje su nepoznate varijable u jednađbama stanja?

Student response:



Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. naponi
-50.0%			b. struje
100.0%	▶	▶	c. početni uvjeti
-50.0%			d. izvori
-50.0%			e. naponi i struje

Score: 10 / 10

**Question 2** (10 points)

Da li prilikom rješavanja mreže uzimamo u obzir zavisne izvore?

Student response:



Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. ne, njih naknadno uvrštavamo
-50.0%			b. ako postoje zavisni strujni izvori, tada mrežu ne možemo riješiti pomoću KZN ili KZS
-50.0%			c. samo ako mrežu rješavamo korištenjem KZN
-50.0%			d. samo ako mrežu rješavamo korištenjem KZS
100.0%			e. da, opisujemo ih pomoću parametara o kojima ovise

Score: 10 / 10

**Question 3** (10 points)

Od koliko se grana sastoji mreža od 4 čvora, ako smo analizirajući mrežu dobili 3 linearno nezavisne jednačbe napona ?

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
100.0%			a. 6
-50.0%			b. 4
-50.0%			c. 2
-50.0%			d. ne možemo odrediti bez poznavanja broja linearno nezavisnih jednačbi napona

Score: 10 / 10

**Question 4** (10 points)

Odredi struju  $i(t)$  za  $t < 0$  ako je:  $R=C=2$   $U_o(t) = 2 \sin(2t)$  za  $t < 0$   $U_o(t) = 2$  za  $t > 0$

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. $2t - e^{2t}$
-50.0%			b. $0.64 \cos 2t$
-50.0%			c. $t^2 - 2t$
100.0%			d. $0.98 \sin(2t - 7^\circ)$

Score: 0 / 10 (Question not answered.)

**Question 5** (10 points)

Postavi jednađbu četvrte petlje mreže na slici.

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
100.0%			a. a)
-50.0%			b. b)
-50.0%			c. c)
-50.0%			d. d)

Score: 10 / 10



---

**Total score:** 40 / 50 = 80.0%

**Question 1** (10 points)

Kojom relacijom smo preslikali napone grana u napone čvorova?

Student response:



Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. $ib(t) = B^T * im(t)$
100.0%			b. $ub(t) = A^T * un(t)$
-50.0%			c. $B * ub(t) = 0$
-50.0%			d. $A * ib(t) = 0$

Score: 10 / 10

### Question 2 (10 points)

Koliki je broj temeljnih petlji, ako je Nb ukupni broj grana, a Nv broj čvorova?

Student response:



Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. $Nb - (Nv + 1)$
100.0%			b. $Nb - (Nv - 1)$
-50.0%			c. $Nb + (Nv + 1)$

Score: 10 / 10

### Question 3 (10 points)

Osnovni tip algebarskih jednažbi mreža u matricnoj formi je:

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. samo opće jednažbe petlji
-50.0%			b. samo opće jednažbe čvorova
100.0%			c. opće jednažbe petlji i čvorova
-50.0%			d. ne postoji osnovni tip

Score: 10 / 10

**Question 4** (10 points)

Koliko ima stabilnih grana u zadanom grafu?

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. 1
-50.0%			b. 2
-50.0%			c. 3
100.0%			d. 5
-50.0%			e. 7

Score: 10 / 10

**Question 5** (10 points)

Kako glasi spojna matrica za zadani graf? (2,5,6 su spone)

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
25.0%			a. $\begin{bmatrix} 1 & 1 & 0 & -1 & 0 & 0 \\ -1 & 0 & -1 & 1 & 1 & 0 \\ -1 & 0 & -1 & 0 & 0 & 1 \end{bmatrix}$
25.0%			b. $\begin{bmatrix} -1 & -1 & 0 & 1 & 0 & 0 \\ -1 & 0 & -1 & 1 & 1 & 0 \\ -1 & 0 & -1 & 0 & 0 & 1 \end{bmatrix}$
25.0%			c. $\begin{bmatrix} 1 & 1 & 0 & -1 & 0 & 0 \\ 1 & 0 & 1 & -1 & -1 & 0 \\ 1 & 0 & 1 & 0 & 0 & -1 \end{bmatrix}$
25.0%			d. $\begin{bmatrix} 1 & 1 & 0 & -1 & 0 & 0 \\ -1 & 0 & -1 & 1 & 1 & 0 \\ 1 & 0 & 1 & 0 & 0 & -1 \end{bmatrix}$
-50.0%			e. $\begin{bmatrix} -1 & -1 & 0 & 1 & 0 & 0 \\ 1 & 0 & 1 & 1 & -1 & 0 \\ -1 & 0 & 1 & 0 & 0 & -1 \end{bmatrix}$

Score: 2.5 / 10

Total score: 42.5 / 50 = 85.0%

**Question 1** (10 points)

Da bi riješili mrežu, koji od navedenih uvjeta nam nije potreban ?

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
100.0%			a. poznavanje KZN
-50.0%			b. topološka konfiguracija mreže
-50.0%			c. eventualno postojanje ili nepostojanje početnih stanja mreže
-50.0%			d. izvori
-50.0%			e. vrsta i parametri elemenata u mreži

Score: -5 / 10

**Question 2** (10 points)

Koje su nepoznate varijable u jednadžbama čvorova?

Student response:

 

Percent Value	Correct Response	Student Response	Answer Choices
100.0%			a. naponi
-50.0%			b. struje
-50.0%			c. početni uvjeti
-50.0%			d. izvori
-50.0%			e. naponi i struje

Score: 10 / 10

**Question 3** (10 points)

Koje su od navedenih tvrdnji istinite?

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. Ako postoji više čvorova u nekoj el. mreži, odabirom dva referentna na suprotnim stranama mreže postupak rješavanja KZN se pojednostavljuje.
-50.0%			b. Ako tražimo samo struju jedne grane u el. mreži možemo koristiti samo one linearno nezavisne jednadžbe u kojima se pojavljuju konturne struje koja prolaze određenom granom.
100.0%			c. Ako u nekoj grani mreže postoji nezavisni izvor koji daje struju $I_a$ , iznos konturne struje koja obilazi i tu granu je $I_a$ .
-50.0%			d. Da bi odredili napon grane neke el. mreže uvijek oduzimamo napon čvora na većem potencijalu od napona čvora na manjem potencijalu.

Score: 10 / 10

**Question 4** (10 points)

Iz slike slijedi ...

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
50.0%			a. napon grane 1 = - napon čvora 1
-50.0%			b. napon grane 2 = napon čvora 1 + napon čvora 3
50.0%			c. napon grane 4 = napon čvora 2 - napon čvora 3
-50.0%			d. svi odgovori su točni !

Score: 5 / 10

### Question 5 (10 points)

Za mrežu na slici vrijedi

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. $uv3/R4 - C5 \frac{d(uv4-uv3)}{dt} - (uv3-uv4)/R6 = 0$
100.0%			b. $uv3/R4 - C5 \frac{d(uv4-uv3)}{dt} - (uv4-uv3)/R6 = 0$
-50.0%			c. $uv3/R4 - C5 \frac{d(uv3-uv4)}{dt} - (uv4-uv3)/R6 = 0$
-50.0%			d. $uv3/R4 - C5 \frac{d(uv3-uv4)}{dt} - (uv3-uv4)/R6 = 0$



Score: 10 / 10

Total score: 30 / 50 = 60.0%

[View Results](#)

### Osnovi topološke analize električnih mreža.

User ID: iflis

Attempt: 1 / 1

Out of: 50

Started: April 8, 2004 11:26 Finished: April 8, 2004 11:30 Time spent: 3 min. 49 sec.

Student finished 6 min. 11 sec. ahead of the 10 min. time limit.

#### Question 1 (10 points)

Matrična jednadžba KZN glasi:

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. $A \cdot i_b(t) = 0$
100.0%			b. $B \cdot u_b(t) = 0$
-50.0%			c. $A \cdot u_b(t) = 0$
-50.0%			d. $B \cdot i_b(t) = 0$

Score: 10 / 10

#### Question 2 (10 points)

Usmjerenost je čvrsto svojstvo grafa, a vrh strelice smatra se:

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
100.0%			a. smjerom strujne referencije
-50.0%			b. plusom naponske referencije

Score: 10 / 10

### Question 3 (10 points)

Matrična jednačba KZS glasi:

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
100.0%			a. $A * ib(t) = 0$
-50.0%			b. $B * ub(t) = 0$
-50.0%			c. $A * ub(t) = 0$
-50.0%			d. $B * ib(t) = 0$

Score: 10 / 10

### Question 4 (10 points)

Koliko graf ima stablenih grana?

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. 0
-50.0%			b. 1
-50.0%			c. 2
100.0%			d. 3
-50.0%			e. 4

Score: 10 / 10

### Question 5 (10 points)

Zadana je reducirana matrica incidencije grafa.

```
1 1 0 0 0 0 1
-1 -1 1 0 0 0 0
0 0 -1 0 1 0 0
0 0 0 -1 -1 -1 0
```

Da li grane 1,3,5,6 sacinjavaju stablo?

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
50.0%			a. Da
-50.0%			b. Ne
50.0%			c. Da, jer je njihova determinanta submatrice razlicita od nule
-50.0%			d. Ne, jer je njihova determinanta submatrice jednaka nuli

Score: -5 / 10

---

**Total score:** 35 / 50 = 70.0%

**View Results**

#### Jednadžbe mreža.

**User ID:** mlojina

**Attempt:** 1 / 1

**Out of:** 50

**Started:** April 8, 2004 11:45

**Finished:** April 8, 2004 11:53

**Time spent:** 8 min. 48 sec.



Student finished 1 min. 12 sec. ahead of the 10 min. time limit.

#### Question 1 (10 points)

Koliko iznosi broj linearno nezavisnih jednadžbi napona u mreži sa 5 čvorova?

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. 4
-50.0%			b. 5



100.0%			c. ne može se odrediti bez poznavanja broja grana u mreži
-50.0%			d. 3
-50.0%			e. ne može se odrediti bez poznavanja topološke strukture mreže

Score: 10 / 10

### Question 2 (10 points)

Koliko iznosi najveći broj linearno nezavisnih jednažbi KZS za mrežu od  $N_b$  grana i  $N_v$  čvorova?

Student response:



Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. $N_b - (N_v + 1)$
-50.0%			b. $N_b - N_v$
100.0%			c. $N_v - 1$
-50.0%			d. $N_b - (N_v - 1)$
-50.0%			e. $N_v - (N_b - 1)$

Score: 10 / 10

### Question 3 (10 points)

Jednažbe stanja koristimo u analizi nekih električnih mreža da bi:

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. odredili izraze za struje i napone
100.0%			b. odredili izraze za početne uvjete
-50.0%			c. odredili iznose početnih struja i napona na L i C

-50.0%			d. odredili linearnost odnosno nelinearnost mreže
--------	--	--	---

Score: 10 / 10

#### Question 4 (10 points)

Za mrežu zadanu slikom vrijedi:

Student response:	Percent Value	Correct Response	Student Response	Answer Choices
	50.0%			a. $-(uv1(s)-uv3(s))/R3 - (uv2(s)-uv3(s))/R4 + uv3(s)/R6 = 0$
	-50.0%			b. $-(uv1(s)-uv3(s))/R3 - (uv2(s)-uv3(s))/R4 - uv3(s)/R6 = 0$
	-50.0%			c. $(uv1(s)-uv3(s))/R3 - (uv2(s)-uv3(s))/R4 - uv3(s)/R6 = 0$
	50.0%			d. $-(uv1-uv3)/R3 - (uv2-uv3)/R4 + uv3/R6 = 0$

Score: 5 / 10

#### Question 5 (10 points)

Postavi jednadžbu prve i druge petlje mreže na slici.

Student response:	Percent Value	Correct Response	Student Response	Answer Choices
	100.0%			a. a)
	-50.0%			b. b)



-50.0%			c.	c)
-50.0%			d.	d)

Score: 10 / 10

**Total score:** 45 / 50 = 90.0%

Korištenjem KZS u rješavanju neke mreže tražimo struju u jednoj od grana te mreže. Kako utječe promjena smjera konturnih struja (koje obilaze granu tražene struje) na iznos i smjer tražene struje?

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. iznos ostaje isti, a smjer se mijenja
100.0%			b. iznos i smjer ostaju isti
-50.0%			c. iznos postaje negativan, a smjer ostaje isti
-50.0%			d. iznos postaje negativan, a smjer suprotan onom prije
-50.0%			e. ne možemo odrediti bez poznavanja ostalih parametara mreže

Score: -5 / 10

## Question 2 (10 points)

Koliko iznosi najveći broj linearno nezavisnih jednažbi KZS za mrežu od  $N_b$  grana i  $N_v$  čvorova?

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
---------------	------------------	------------------	----------------

-50.0%			a. $N_b - (N_v + 1)$
-50.0%			b. $N_b - N_v$
100.0%			c. $N_v - 1$
-50.0%			d. $N_b - (N_v - 1)$
-50.0%			e. $N_v - (N_b - 1)$

Score: 10 / 10

### Question 3 (10 points)

Koje su od navedenih tvrdnji istinite ?

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. Prilikom rješavanja mreža KZN moramo sve izvore pretvoriti u naponske
-50.0%			b. Prilikom rješavanja mreža KZS moramo sve izvore pretvoriti u strujne
100.0%			c. Ako postoje i strujni i naponski izvori u mreži ne mormo ih pretvarati jer se ona može riješiti i KZN i KZS
-50.0%			d. Ako pretvaramo izvore u el. mreži svi moraju biti istog tipa, dakle svi naponski ili svi strujni

Score: -10 / 10

### Question 4 (10 points)

Iz slike slijedi...

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%		<input type="radio"/>	a. $i_4 = (u_{v2}-u_{v3})/R_4$
-50.0%		<input type="radio"/>	b. $i_1 = (u_g+u_1)/R_1$
-50.0%		<input type="radio"/>	c. $i_1 = (u_g-u_{v1})/R_1$
-50.0%		<input type="radio"/>	d. $i_5 = C_5 \, du_5/dt$
100.0%	<input checked="" type="radio"/>	<input type="radio"/>	e. svi odgovori su točni

Score: -10 / 10

#### Question 5 (10 points)

Postavi jednadžbu prve i druge petlje mreže na slici u Laplace-ovoj domeni.

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
100.0%	<input checked="" type="radio"/>	<input checked="" type="radio"/>	a. a)
-50.0%		<input type="radio"/>	b. b)
-50.0%		<input type="radio"/>	c. c)
-50.0%		<input type="radio"/>	d. d)

Score: 10 / 10

---

Total score: -5 / 50 = -10.0%

---

[View Results](#)



**Jednadžbe mreža.**

User ID: eplecko

Attempt: 1 / 1

Out of: 50



Started: April 8, 2004 12:14 Finished: April 8, 2004 12:20 Time spent: 6 min. 7 sec.

Student finished 3 min. 53 sec. ahead of the 10 min. time limit.

**Question 1** (10 points)

Pretpostavimo li da rješavamo mrežu od Nb grana i Nv čvorova. Za točno rješenje mreže dobili bi :

Student response:



Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. Nv napona grana i Nb struja grana
100.0%			b. Nb napona grana i Nb struja grana
-50.0%			c. Nv napona grana i Nv struja grana
-50.0%			d. Nb napona grana i Nv struja grana
-50.0%			e. ništa od navedenog

Score: 10 / 10

**Question 2** (10 points)

Koliko iznosi najveći broj linearno nezavisnih jednažbi KZS za mrežu od Nb grana i Nv čvorova?

Student response:



Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. $Nb - (Nv + 1)$
-50.0%			b. $Nb - Nv$
100.0%			c. $Nv - 1$
-50.0%			d. $Nb - (Nv - 1)$
-50.0%			e. $Nv - (Nb - 1)$

Score: 10 / 10

### Question 3 (10 points)

Jednažbe stanja koristimo u analizi nekih električnih mreža da bi:

Student response:


Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. odredili izraze za struje i napone
100.0%			b. odredili izraze za početne uvjete
-50.0%			c. odredili iznose početnih struja i napona na L i C
-50.0%			d. odredili linearnost odnosno nelinearnost mreže

Score: 10 / 10

**Question 4** (10 points)

Za mrežu na slici vrijedi

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. $(uv4(s)-uv1(s))/R3 + iL3(0)/s + sC5(uv4(s)-uv3(s)) - C5(uv4(0)-uv3(0)) + (uv4(s)-uv3(s))/R6 = 0$
-50.0%			b. $(uv4(s)-uv1(s))/R3 + C5(uv4(s)-uv3(s)) - sC5(uv4(0)-uv3(0)) + (uv4(s)-uv3(s))/R6 = 0$
100.0%			c. $uv3(s)/R4 - sC5(uv4(s)-uv3(s)) + C5(uv4(0)-uv3(0)) - (uv4(s)-uv3(s))/R6 = 0$



-50.0%			d. niti jedna od navedenih jednađbi
--------	--	--	-------------------------------------

Score: 0 / 10 (Question not answered.)

### Question 5 (10 points)

Za mrežu zadanu slikom vrijedi:

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. - $(uv1(s)+ug1(s))/R1 + uv2(s)/R2 - 1/sL3 (uv4(s)-uv1(s)) - iL3(0)/s = 0$
-50.0%			b. $uv3(s)/R4 - sC5 (uv4(o)-uv3(0)) + C5 (uv4(s)-uv3(s)) + ig6 = 0$
-50.0%			c. $1/sL3 (uv4(s)-uv1(s)) + iL3(0)/s - C5 (uv4(s)-uv3(s)) + sC5 (uv4(0)-uv3(0)) - ig6 = 0$
-50.0%			d. sve navedeno
100.0%			e. nista od navedenog



Score: 10 / 10

---

Total score: 40 / 50 = 80.0%

### Question 1 (10 points)



Pretpostavimo li da rješavamo mrežu od Nb grana i Nv čvorova. Za točno rješenje mreže dobili bi :  
Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. Nv napona grana i Nb struja grana
100.0%			b. Nb napona grana i Nb struja grana
-50.0%			c. Nv napona grana i Nv struja grana
-50.0%			d. Nb napona grana i Nv struja grana
-50.0%			e. ništa od navedenog

Score: 10 / 10

## Question 2 (10 points)

Koliko iznosi najmanji broj linearno nezavisnih jednažbi KZN za mrežu od Nb grana i Nv čvorova?  
Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. $Nb - (Nv + 1)$
-50.0%			b. $Nb - Nv$
-50.0%			c. $Nv - 1$
100.0%			d. $Nb - (Nv - 1)$

-50.0%

e.  $N_v - (N_b - 1)$

Score:

10 / 10

### Question 3 (10 points)

Od koliko čvorova se sastoji mreža sa 6 grana ako smo analizom mreže dobili 3 linearno nezavisne jednačbe KZS ?

Student response:


Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. 5
100.0%	<input type="checkbox"/>		b. 4
-50.0%		<input checked="" type="checkbox"/>	c. 3
-50.0%			d. 8
-50.0%			e. ne možemo odrediti

Score:

-5 / 10
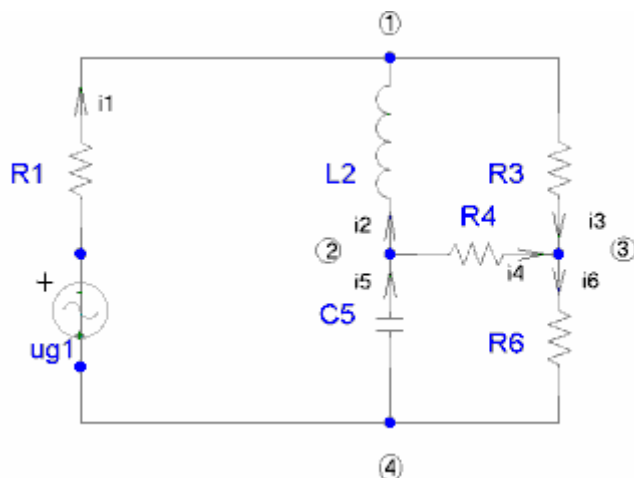
### Question 4 (10 points)

Koja matrica odgovara matrici struje za sliku ?



Student response:

Percent	Correct	Student	Answer Choices
---------	---------	---------	----------------


Value	Response	Response	
-50.0%			a. $u_g/R1+iL2(0)/s$ $iL2(0)/s+C5uC5(0)$ 0
-50.0%			b. $u_g/R1+iL2(0)/s$ $iL2(0)/s+C5uC5(0)$ i1
-50.0%		▶	c. $u_g/R1+iL2(0)/s -$ $iL2(0)/s-C5uC5(0)$ i1
100.0%	▶		d. $u_g/R1+iL2(0)/s -$ $iL2(0)/s-C5uC5(0)$ 0

Score:

-5 / 10
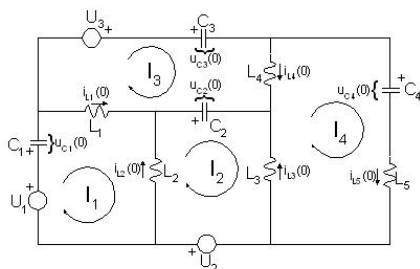
### Question 5 (10 points)

Postavi jednađžbu prve petlje mreže na slici u Laplace-ovoj domeni.



- a)  $I_1(s) \left[ \frac{1}{sC_1} + sL_1 + sL_2 \right] - I_3(s)sL_1 - I_2(s)sL_2 = U_1(s) - \frac{U_{C1}(0)}{s} + L_1 i_{L1}(0) - L_2 i_{L2}(0)$
- b)  $I_1(s) \left[ \frac{1}{sC_1} + sL_1 + sL_2 \right] - I_3(s)sL_1 - I_2(s)sL_2 = U_1(s) + \frac{U_{C1}(0)}{s} + L_1 i_{L1}(0) - L_2 i_{L2}(0)$
- c)  $I_1(s) \left[ \frac{1}{sC_1} + sL_1 + sL_2 \right] - I_3(s)sL_1 - I_2(s)sL_2 = U_1(s) - \frac{U_{C1}(0)}{s} + L_1 i_{L1}(0) + L_2 i_{L2}(0)$
- d)  $I_1(s) \left[ \frac{1}{sC_1} + sL_1 + sL_2 \right] - I_3(s)sL_1 - I_2(s)sL_2 = U_1(s) - \frac{U_{C1}(0)}{s} - L_1 i_{L1}(0) - L_2 i_{L2}(0)$
- e)  $I_1(s) \left[ \frac{1}{sC_1} + sL_1 + sL_2 \right] - I_3(s)sL_1 - I_2(s)sL_2 = -U_1(s) - \frac{U_{C1}(0)}{s} + L_1 i_{L1}(0) - L_2 i_{L2}(0)$

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
100.0%	▶	▶	a. a)
-50.0%			b. b)
-50.0%			c. c)
-50.0%			d. d)

-50.0%

e. e)



Score:

10 / 10

### Question 1 (10 points)

Koliko ima linearno nezavisnih jednađbi KZS u mreži sa 4 grane?

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. 4
-50.0%			b. 3
-50.0%			c. 2
100.0%			d. ništa od navedenog



Score:

-5 / 10

### Question 2 (10 points)

Koliko iznosi najmanji broj linearno nezavisnih jednađbi KZN za mrežu od Nb grana i Nv čvorova?

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. $Nb - (Nv + 1)$
-50.0%			b. $Nb - Nv$
-50.0%			c. $Nv - 1$
100.0%			d. $Nb - (Nv - 1)$
-50.0%			e. $Nv - (Nb - 1)$

Score:

10 / 10

### Question 3 (10 points)



Koje su od navedenih tvrdnji istinite?


Student response:

Percent Value	Correct Response	Student Response	Answer Choices
50.0%			a. Konturne struje su zamišljene struje koje prolaze kroz petlje te njihovim zbrajanjem i oduzimanjem dobijamo prave iznose i smjerove struja u granama
-50.0%			b. Rješavanje mreža pomoću KZN je nešto lakse od rješavanja pomoću KZS
-50.0%			c. Smjerove svih konturnih struja odabiremo uvijek u istom smjeru, tako je najmanja mogućnost pogreške.
-50.0%			d. u mreži sa samo strujnim izvorima isključivo koristimo KZS
50.0%			e. početni uvjeti ponašaju se kao strujni ili naponski izvori u analizi mreže, ovisno o elementu na kojem postoje

Score: 10 / 10
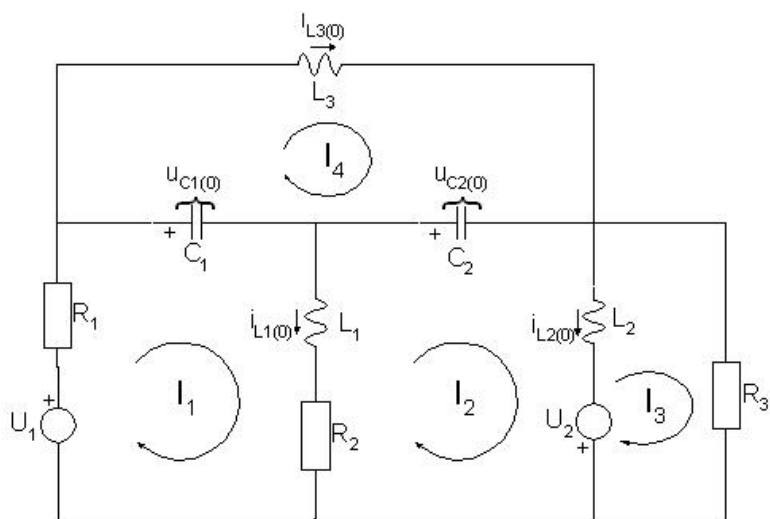
#### Question 4 (10 points)

Postavi jednadžbu prve petlje mreže na slici.



- a)  $i_1 R_1 + \frac{1}{C_1} \int_{-\infty}^t [i_1(\tau) - i_4(\tau)] d\tau + L_1 \frac{d}{dt} [i_1(\tau) - i_2(\tau)] + R_2 [i_1(t) - i_2(t)] = u_1(t)$
- b)  $i_1 R_1 + \frac{1}{C_1} \int_{-\infty}^t [i_1(\tau) - i_4(\tau)] d\tau - L_1 \frac{d}{dt} [i_1(\tau) - i_2(\tau)] + R_2 [i_1(t) - i_2(t)] = u_1(t)$
- c)  $i_1 R_1 + \frac{1}{C_1} \int_{-\infty}^t [i_1(\tau) - i_4(\tau)] d\tau - L_1 \frac{d}{dt} [i_1(\tau) - i_2(\tau)] - R_2 [i_1(t) - i_2(t)] = u_1(t)$
- d)  $i_1 R_1 + \frac{1}{C_1} \int_{-\infty}^t [i_1(\tau) - i_4(\tau)] d\tau - L_1 \frac{d}{dt} [i_1(\tau) - i_2(\tau)] + R_2 [i_1(t) - i_2(t)] = -u_1(t)$


Student response:

Percent Value	Correct Response	Student Response	Answer Choices
100.0%	▶	▶	a. a)
-50.0%			b. b)
-50.0%			c. c)
-50.0%			d. d)

Score: 10 / 10
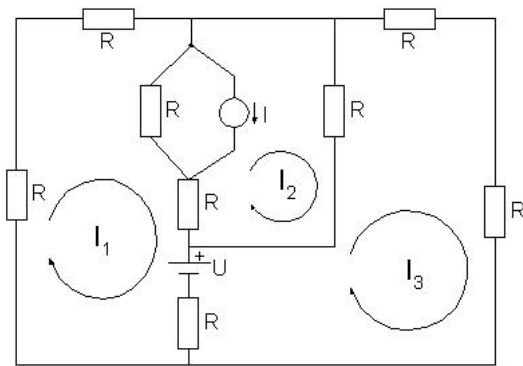
### Question 5 (10 points)

Postavi jednađbu prve i treće petlje mreže na slici.



- a)  $5RI_1 - 2RI_2 = -U + IR$   
 $-I_1R - I_2R + 4RI_3 = U$
- b)  $5RI_1 - 2RI_2 = U + IR$   
 $-I_1R - I_2R + 4RI_3 = U$
- c)  $5RI_1 - 2RI_2 = -U - IR$   
 $-I_1R - I_2R + 4RI_3 = U$
- d)  $5RI_1 + 2RI_2 = -U + IR$   
 $-I_1R - I_2R + 4RI_3 = U$

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%		<input type="radio"/>	a. a)
-50.0%		<input type="radio"/>	b. b)
-50.0%		<input type="radio"/>	c. c)
-50.0%		<input type="radio"/>	d. d)
100.0%		<input checked="" type="radio"/>	e. nijedno od navedenog

Score: -5 / 10

### Question 1 (10 points)

Da bi riješili mrežu, koji od navedenih uvjeta nam nije potreban ?

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
100.0%			a. poznavanje KZN
-50.0%			b. topološka konfiguracija mreže
-50.0%			c. eventualno postojanje ili nepostojanje početnih stanja mreže
-50.0%			d. izvori
-50.0%			e. vrsta i parametri elemenata u mreži

Score: 10 / 10

### Question 2 (10 points)

Ako nije zadano, kako određujemo smjer konturnih struja korištenjem KZS?

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. smjer konturnih struja je uvijek u smjeru kazaljke na satu
-50.0%			b. sve konturne struje moraju biti istog smjera
-50.0%			c. barem dvije konturne struje moraju biti različitih smjerova
-50.0%			d. ako nije zadano, ne možemo riješiti mrežu pomoću KZS
100.0%			e. smjer sami određujemo onako kako nam najviše odgovara

Score: 10 / 10

### Question 3 (10 points)

Od koliko se grana sastoji mreža od 4 čvora, ako smo analizirajući mrežu dobili 3 linearno nezavisne jednačbe napona ?

Student response:


Percent	Correct	Student	Answer Choices
---------	---------	---------	----------------

Value	Response	Response	
100.0%	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	a. 6
-50.0%	<input type="checkbox"/>	<input type="checkbox"/>	b. 4
-50.0%	<input type="checkbox"/>	<input type="checkbox"/>	c. 2
-50.0%	<input type="checkbox"/>	<input type="checkbox"/>	d. ne možemo odrediti bez poznavanja broja linearno nezavisnih jednažbi napona

Score: 10 / 10
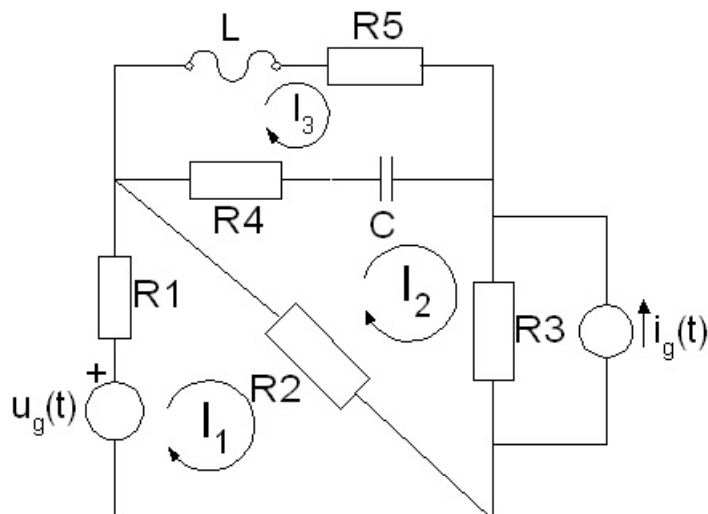
#### Question 4 (10 points)

Kako glase jednažbe petlji za mrežu na slici?



Student response:


Percent Value	Correct Response	Student Response	Answer Choices
100.0%	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	a. $I_1 (R_1 + R_2) - I_2 * R_2 = u_g(t)$ $-I_1 * R_2 + I_2 (R_2 + R_3 + R_4 + 1/j\omega C) - I_3 (R_4 + 1/j\omega C) = -i_g(t) * R_3$ $I_3 (R_4 + R_5 + j\omega L + 1/j\omega C) - I_2 (R_4 + 1/j\omega C) = 0$
-50.0%	<input type="checkbox"/>	<input type="checkbox"/>	b. $I_1 (R_1 + R_2) - I_2 * R_2 = u_g(t)$ $-I_1 * R_2 + I_2 (R_2 + R_3 + R_4 + 1/j\omega C) - I_3 (R_4 + 1/j\omega C) = i_g(t) * R_3$ $I_3 (R_4 + R_5 + j\omega L + 1/j\omega C) - I_2 (R_4 + 1/j\omega C) = 0$
-50.0%	<input type="checkbox"/>	<input type="checkbox"/>	c. $I_1 (R_1 + R_2) - I_2 * R_2 = u_g(t)$ $-I_1 * R_2 + I_2 (R_2 + R_3 + R_4 + 1/j\omega C) + I_3 (R_4 + 1/j\omega C) = i_g(t) * R_3$ $I_3 (R_4 + R_5 + j\omega L + 1/j\omega C) - I_2 (R_4 + 1/j\omega C) = 0$

-50.0%			d.	$I_1(R_1+R_2) - I_2 \cdot R_2 = u_g(t)$ $-I_1 \cdot R_2 + I_2(R_2+R_3+R_4+1/j\omega C) -$ $I_3(R_4+1/j\omega C) = -i_g(t) \cdot R_3$ $I_3(R_4+R_5+j\omega L+1/j\omega C) = -I_2(R_4+1/j\omega C)$
-50.0%			e.	$-I_1(R_1+R_2) + I_2 \cdot R_2 = u_g(t)$ $-I_1 \cdot R_2 + I_2(R_2+R_3+R_4+1/j\omega C) -$ $I_3(R_4+1/j\omega C) = -i_g(t) \cdot R_3$ $I_3(R_4+R_5+j\omega L+1/j\omega C) - I_2(R_4+1/j\omega C) = 0$

Score: 10 / 10
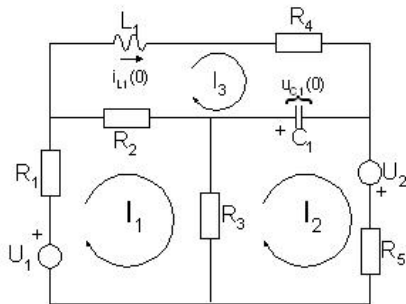
### Question 5 (10 points)

Postavi jednađzbu prve i druge petlje mreže na slici u Laplace-ovoj domeni.



- a)  $I_1(s)[R_1 + R_2 + R_3] - I_3(s)R_2 - I_2(s)R_3 = U_1(s)$   
 $I_2(s)[R_3 + \frac{1}{sC_1} + R_5] - I_1(s)R_3 - I_3(s)\frac{1}{sC_1} = U_2(s) - \frac{u_{C1}(0)}{s}$
- b)  $I_1(s)[R_1 + R_2 + R_3] - I_2(s)R_2 - I_3(s)R_3 = U_1(s)$   
 $I_2(s)[R_3 + \frac{1}{sC_1} + R_5] - I_1(s)R_3 - I_3(s)\frac{1}{sC_1} = U_2(s) + \frac{u_{C1}(0)}{s}$
- c)  $I_1(s)[R_1 + R_2 + R_3] - I_2(s)R_2 - I_3(s)R_3 = -U_1(s)$   
 $I_2(s)[R_3 + \frac{1}{sC_1} + R_5] - I_1(s)R_3 - I_3(s)\frac{1}{sC_1} = U_2(s) + \frac{u_{C1}(0)}{s}$
- d)  $I_1(s)[R_1 + R_2 + R_3] - I_2(s)R_2 - I_3(s)R_3 = U_1(s)$   
 $I_2(s)[R_3 + \frac{1}{sC_1} + R_5] - I_1(s)R_3 - I_3(s)\frac{1}{sC_1} = U_2(s) - \frac{u_{C1}(0)}{s}$

Student response:

Percent Value	Correct Response	Student Response	Answer Choices	
100.0%	▶	▶	a.	a)
-50.0%			b.	b)



-50.0%			c.	c)
-50.0%			d.	d)

Score: 10 / 10

### Question 1 (10 points)

Pretpostavimo da analiziramo mrežu koristeći tri konturne struje. Promijenimo li jednoj od konturnih struja smjer, koliko će linearno nezavisnih jednadžbi promijeniti svoj izraz?

Student response:



Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. 1
-50.0%			b. 2
-50.0%			c. 3
100.0%			d. ne možemo odrediti bez poznavanja topološke strukture mreže i koja konturna struja mijenja smjer

Score: 10 / 10

### Question 2 (10 points)

Ako nije zadan, kako se odabire referentni čvor korištenjem KZN?

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. na čvoru na kojem je spojena negativna stezaljka naponskog ili strujnog izvora
-50.0%			b. na čvoru u koji ulazi najviše struja
100.0%			c. proizvoljno



-50.0%			d. na čvoru iz kojeg izlazi najviše struja
-50.0%			e. ništa od navedenog

Score: 10 / 10

### Question 3 (10 points)

Koje su od navedenih tvrdnji istinite ?

Student response:


Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. Prilikom rješavanja mreža KZN moramo sve izvore pretvoriti u naponske
-50.0%			b. Prilikom rješavanja mreža KZS moramo sve izvore pretvoriti u strujne
100.0%			c. Ako postoje i strujni i naponski izvori u mreži ne mormo ih pretvarati jer se ona može riješiti i KZN i KZS
-50.0%			d. Ako pretvaramo izvore u el. mreži svi moraju biti istog tipa, dakle svi naponski ili svi strujni

Score: 10 / 10
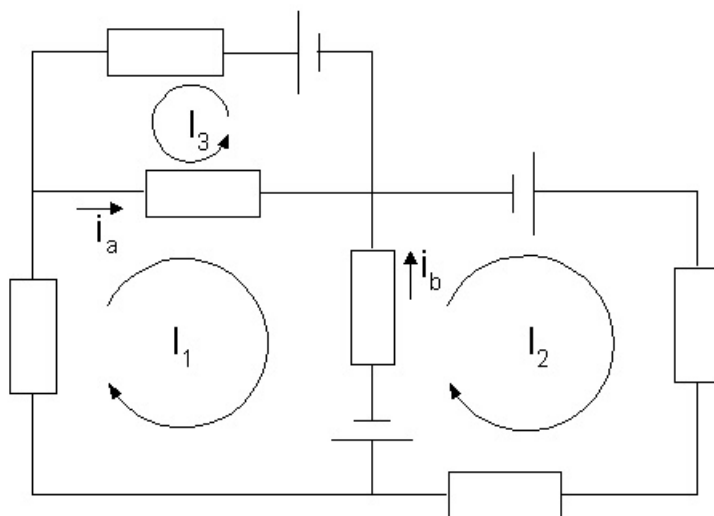
### Question 4 (10 points)

Ako konturne struje sa slike iznose  $I_1=0,1$  A,  $I_2=0,3$  A i  $I_3=-0,5$  A, kolike iznose struje  $I_a$  i  $I_b$ ?






Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. $i_a = -0,4$ A $i_b = -0,2$ A
-50.0%			b. $i_a = 0,4$ A $i_b = 0,2$ A
-50.0%			c. $i_a = 0,4$ A $i_b = 0,2$ A
-50.0%			d. $i_a = -0,6$ A $i_b = 0,2$ A
100.0%	►	►	e. $i_a = -0,4$ A $i_b = 0,2$ A

Score: 10 / 10
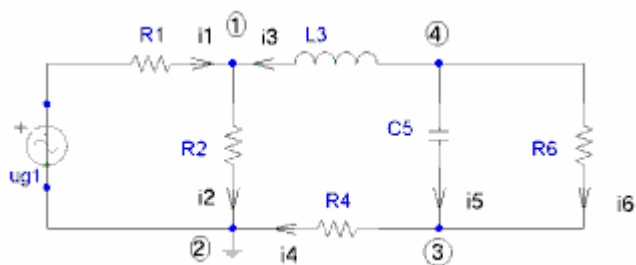
### Question 5 (10 points)

Za mrežu na slici ( $u_{g1}=0$ ) vrijedi:



Student response:

Percent Value	Correct Response	Student Response	Answer Choices
---------------	------------------	------------------	----------------

33.4%			a. napon grane 1 = - napon grane 2 = - napon čvora 1
-50.0%			b. napon grane 1 = - napon grane 2 = napon čvora 1
33.3%			c. napon grane 3 = napon čvora 4 - napon čvora 1
33.3%			d. napon grane 5 = napon čvora 4 - napon čvora 3 = napon grane 6

Score: 10 / 10

### Question 1 (10 points)

Pretpostavimo li da rješavamo mrežu od  $N_b$  grana i  $N_v$  čvorova. Za točno rješenje mreže dobili bi :

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. $N_v$ napona grana i $N_b$ struja grana
100.0%			b. $N_b$ napona grana i $N_b$ struja grana
-50.0%			c. $N_v$ napona grana i $N_v$ struja grana
-50.0%			d. $N_b$ napona grana i $N_v$ struja grana
-50.0%			e. ništa od navedenog

Score: 10 / 10

**Question 2** (10 points)

Koliko iznosi najveći broj linearno nezavisnih jednažbi KZS za mrežu od  $N_b$  grana i  $N_v$  čvorova?

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. $N_b - (N_v + 1)$
-50.0%			b. $N_b - N_v$
100.0%			c. $N_v - 1$
-50.0%			d. $N_b - (N_v - 1)$
-50.0%			e. $N_v - (N_b - 1)$

Score: -5 / 10

**Question 3** (10 points)

Koje su od navedenih tvrdnji istinite?

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
50.0%			a. Konturne struje su zamišljene struje koje prolaze kroz petlje te njihovim zbrajanjem i oduzimanjem dobijamo prave iznose i smjerove struja u granama
-50.0%			b. Rješavanje mreža pomoću KZN je nešto lakše od rješavanja pomoću KZS
-50.0%			c. Smjerove svih konturnih struja odabiremo uvijek u istom smjeru, tako je najmanja mogućnost pogreške.

-50.0%			d. u mreži sa samo strujnim izvorima isključivo koristimo KZS
--------	--	--	---

50.0%




e. početni uvjeti ponašaju se kao strujni ili naponski izvori u analizi mreže, ovisno o elementu na kojem postoje

Score: 10 / 10

#### Question 4 (10 points)

Da li su ove sheme dualne?

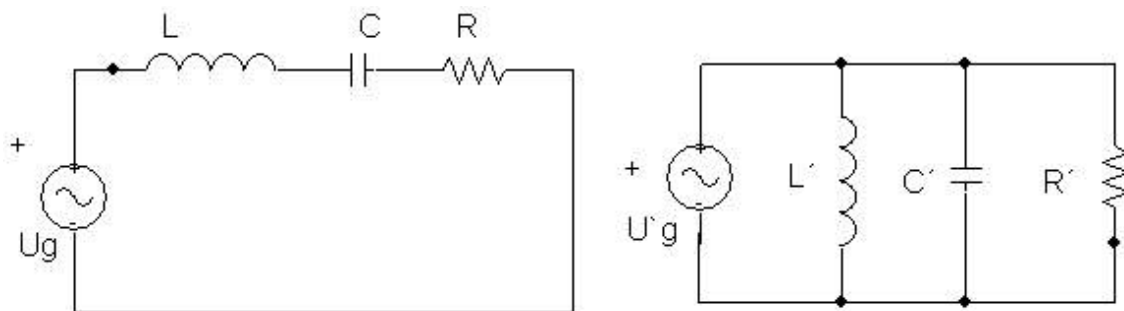


Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. Da
100.0%			b. Ne

Score: -5 / 10
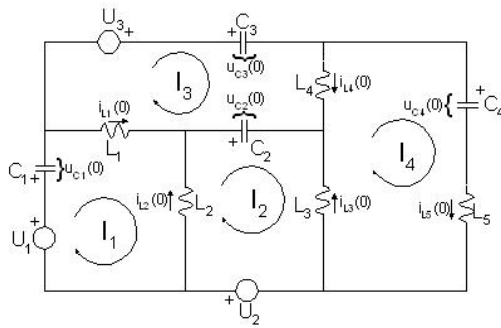
#### Question 5 (10 points)

Postavi jednadžbu druge petlje mreže na slici u Laplace-ovoj domeni.



- a)  $I_2(s)[sL_2 + \frac{1}{sC_2} + sL_3] - I_1(s)sL_2 - I_3(s)\frac{1}{sC_2} - I_4(s)sL_3 = U_2(s) + L_2 i_{L2}(0) - \frac{u_{C2}(0)}{s} - i_{L3}(0)L_3$
- b)  $I_2(s)[sL_2 + \frac{1}{sC_2} + sL_3] - I_1(s)sL_2 - I_3(s)\frac{1}{sC_2} - I_4(s)sL_3 = U_2(s) + L_2 i_{L2}(0) - \frac{u_{C2}(0)}{s} + i_{L3}(0)L_3$
- c)  $I_2(s)[sL_2 + \frac{1}{sC_2} + sL_3] - I_1(s)sL_2 - I_3(s)\frac{1}{sC_2} - I_4(s)sL_3 = U_2(s) - L_2 i_{L2}(0) - \frac{u_{C2}(0)}{s} + i_{L3}(0)L_3$
- d)  $I_2(s)[sL_2 + \frac{1}{sC_2} + sL_3] - I_1(s)sL_2 - I_3(s)\frac{1}{sC_2} - I_4(s)sL_3 = -U_2(s) + L_2 i_{L2}(0) + \frac{u_{C2}(0)}{s} - i_{L3}(0)L_3$
- e)  $I_2(s)[sL_2 + \frac{1}{sC_2} + sL_3] - I_1(s)sL_2 - I_3(s)\frac{1}{sC_2} - I_4(s)sL_3 = U_2(s) + L_2 i_{L2}(0) + \frac{u_{C2}(0)}{s} - i_{L3}(0)L_3$

Student response:

Percent Value	Correct Response	Student Response	Answer Choices	
100.0%			a.	a)
-50.0%			b.	b)
-50.0%			c.	c)
-50.0%			d.	d)
-50.0%			e.	e)

Score: 10 / 10

### Question 1 (10 points)

Opća jednačba čvorova u matričnom obliku glasi:

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
100.0%			a. $Y_n(s) * U_n(s) = A * Z_b(s)^{-1} * U_g(s) - A * Z_b(s)^{-1} * L_b * i_b(0) + (1/s) * A * Z_b(s)^{-1} * u_c(0)$
-50.0%			b. $Y_n(s) * U_n(s) = A *$

			$Zb(s)^{-1} * Ug(s) - A * Zb(s)^{-1} * Lb * ib(0)$
-50.0%			c. $Yn(s) * Un(s) = A * Zb(s)^{-1} * Ug(s)$
-50.0%			d. $0 = A * Zb(s)^{-1} * Ug(s) - A * Zb(s)^{-1} * Lb * ib(0) + (1/s) * A * Zb(s)^{-1} * uc(0)$

Score: 10 / 10

### Question 2 (10 points)

Subgraf nekog grafa naziva se petljom grafa ako je:

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
50.0%			a. taj subgraf povezan
50.0%			b. točno dvije grane od tog subgrafa su incidentne sa svakim čvorištem
-50.0%			c. grane ne moraju biti incidentne sa čvorištima
-50.0%			d. nijedno od navedenog

Score: 10 / 10

### Question 3 (10 points)

Ako je broj čvorova 4, a broj grana 5, koliko jednačbi KZS nam je potrebno?

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
100.0%			a. 3 od 4
-50.0%			b. 3 od 5

-50.0%			c.	4 od 5
-50.0%			d.	4 od 4

Score: 10 / 10

**Question 4** (10 points)

Koliko graf ima stablenih grana?




Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. 0
-50.0%		▶	b. 1
-50.0%			c. 2
100.0%	▶		d. 3
-50.0%			e. 4



Score: -5 / 10

**Question 5** (10 points)

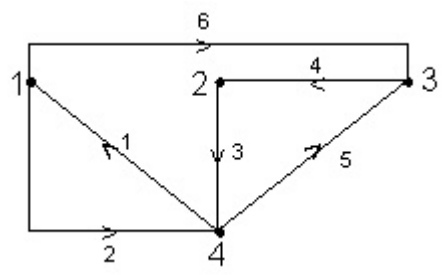Koliko ima stablenih grana u zadanom grafu?



Student response:



Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. 2
100.0%			b. 3
-50.0%			c. 4
-50.0%			d. 5
-50.0%			e. 6

Score: 10 / 10

---

Koliko najmanje linearno nezavisnih jednađbi ćemo koristiti prilikom rješavanja mreže s 5 čvorova koristeći KZS ?

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. 5
100.0%			b. 4
-50.0%			c. 6
-50.0%			d. ne možemo odrediti bez poznavanja broja grana mreže
-50.0%			e. ne možemo odrediti bez poznavanja topološke strukture mreže

Score: 10 / 10

## Question 2 (10 points)

O čemu ovisi broj linearno nezavisnih jednađbi KZS ?

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
---------------	------------------	------------------	----------------



-50.0%			a. o broju elemenata u granama
-50.0%			b. o broju grana
100.0%	▶	▶	c. o broju čvorova
-50.0%			d. o broju čvorova i grana
-50.0%			e. ništa od navedenog

Score: 10 / 10

### Question 3 (10 points)

Ako kroz neku granu el. mreže prolaze dvije konturne struje  $I_a$  i  $I_b$  različitog smjera, a pretpostavljen smjer struje  $I_g$  grane koju tražimo je istog smjera kao  $I_a$ , koji izraz točno opisuje struju grane  $I_g$  ?


Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. $I_g = -I_a - I_b$
-50.0%			b. $I_g = I_a + I_b$
-50.0%			c. $I_g = -I_a + I_b$
100.0%	▶	▶	d. $I_g = I_a - I_b$
-50.0%			e. ništa od navedenog

Score: 10 / 10

### Question 4 (10 points)

Za mrežu zadanu slikom vrijedi:

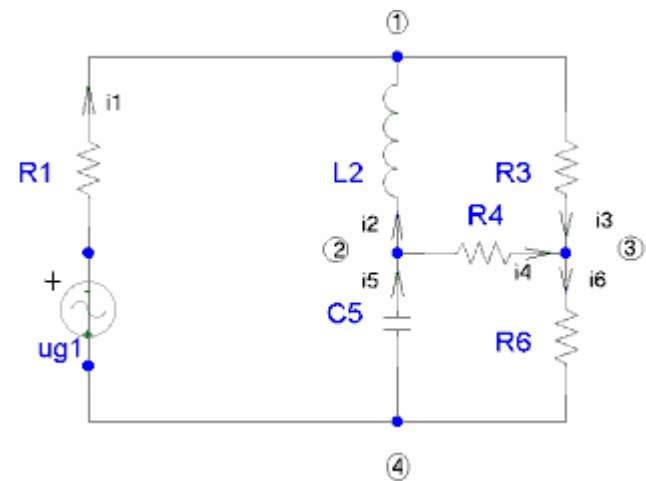

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
50.0%			a. $-(uv1(s)-uv3(s))/R3 - (uv2(s)-uv3(s))/R4 + uv3(s)/R6 = 0$
-50.0%			b. $-(uv1(s)-uv3(s))/R3 - (uv2(s)-uv3(s))/R4 - uv3(s)/R6 = 0$
-50.0%			c. $(uv1(s)-uv3(s))/R3 - (uv2(s)-uv3(s))/R4 - uv3(s)/R6 = 0$
50.0%			d. $-(uv1-uv3)/R3 - (uv2-uv3)/R4 + uv3/R6 = 0$

Score: 10 / 10

### Question 5 (10 points)

Postavi jednađbu druge petlje mreže na slici u Laplace-ovoj domeni.

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
---------------	------------------	------------------	----------------

100.0%			a.	a)
-50.0%			b.	b)
-50.0%			c.	c)
-50.0%			d.	d)
-50.0%			e.	e)

Score: 10 / 10

### Question 1 (10 points)

Matricna jednadzba KZS glasi:

Student response:	Percent Value	Correct Response	Student Response	Answer Choices
	100.0%			a. $A \cdot I_b(s) = 0$
	-50.0%			b. $B \cdot U_b(s) = 0$
	-50.0%			c. $A \cdot U_b(s) = 0$
	-50.0%			d. $B \cdot I_b(s) = 0$

Score: 10 / 10

### Question 2 (10 points)

Graf je planaran ako se ne može prikazati u ravnini (tako da se izvan čvorišta ni jedna grana ne ukrštava s drugom). Da li je definicija ispravna?



Student response:	Percent Value	Correct Response	Student Response	Answer Choices
	-50.0%			a. da
	100.0%			b. ne

Score: 10 / 10

### Question 3 (10 points)

Broj čvorova, referentni smjerovi za struje i referentni polariteti za napone, mogu biti


Student response:

Percent Value	Correct Response	Student Response	Answer Choices
100.0%			a. proizvoljno postavljani
-50.0%			b. samo je jedan odabir ispravan
-50.0%			c. čvorovi su jedinstveno postavljani, dok se ostalo može mijenjati
-50.0%			d. možemo mijenjati samo referentni smjer struje


Score: 10 / 10
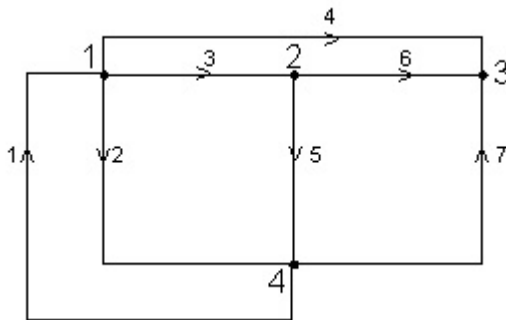
### Question 4 (10 points)

Kako glasi rastavna matrica grafa ako su grane 1,3,7 stablene?



Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. $\begin{bmatrix} 1 & 1 & 0 & 1 & 1 & 1 \\ 0 & 0 & -1 & 0 & -1 & -1 \\ 0 & 0 & 0 & -1 & 0 & 1 \\ 1 \end{bmatrix}$
100.0%			b. $\begin{bmatrix} 1 & -1 & 0 & -1 & -1 & -1 \\ 0 \end{bmatrix}$

				0	0	1	0	-1	-1
				0					
				0	0	0	1	0	1
				1					

-50.0%




c.  $\begin{pmatrix} 1 & -1 & 0 & -1 & -1 & -1 \\ 0 & 0 & -1 & 0 & 1 & 1 \\ 0 & 0 & 0 & 1 & 0 & 1 \\ 1 & & & & & \end{pmatrix}$

Score: -5 / 10

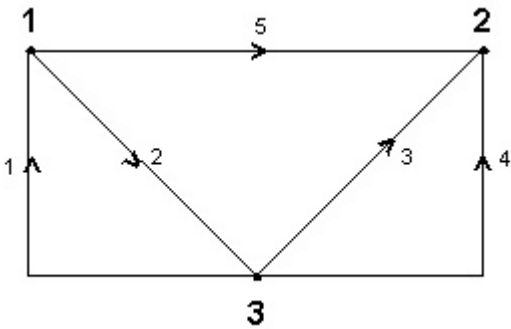**Question 5** (10 points)

Kako glasi spojna matrica? (1,4,5 su spone)



Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. $\begin{pmatrix} -1 & -1 & 0 & 0 & 0 \\ 0 & 0 & -1 & -1 & 0 \\ 0 & 1 & -1 & 0 & -1 \end{pmatrix}$
-50.0%			b. $\begin{pmatrix} 1 & 1 & 0 & 0 & 0 \\ 0 & 0 & 1 & 1 & 0 \\ 0 & -1 & 1 & 0 & 1 \end{pmatrix}$
-50.0%			c. $\begin{pmatrix} 0 & 0 & 1 & 1 & 1 \\ 1 & 1 & -1 & -1 & 1 \\ 1 & 0 & 1 & 0 & 1 \end{pmatrix}$
100.0%			d. $\begin{pmatrix} 1 & 1 & 0 & 0 & 0 \\ 0 & 0 & 1 & -1 & 0 \\ 0 & 1 & 1 & 0 & -1 \end{pmatrix}$

Score: 10 / 10

---

**Question 1** (10 points)

Matricna jednadzba KZN glasi:

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. $A \cdot I_b(s) = 0$
100.0%			b. $B \cdot U_b(s) = 0$
-50.0%			c. $A \cdot U_b(s) = 0$
-50.0%			d. $B \cdot I_b(s) = 0$

Score: 10 / 10

**Question 2** (10 points)

Što je singularno čvorište?

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. početno čvorište
-50.0%			b. završno čvorište
100.0%			c. čvorište koje nije povezano s nijednom granom

Score: 10 / 10

**Question 3** (10 points)

Pišući KZS za neku mrežu, pišemo sistem linearnih jednadžbi za sve čvorove. Što su varijable, a što koeficijenti?

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
100.0%			a. varijable su struje u granama, koeficijenti 1, -1, 0
-50.0%			b. varijable su samo

			struje u sponama, koeficijenti mogu biti bilo koji brojevi
-50.0%			c. varijable su naponi u čvorovima, koeficijenti mogu biti bilo koji brojevi
-50.0%			d. varijable su struje u granama, koeficijenti mogu biti bilo koji brojevi

Score: 10 / 10

Question 4 (10 points)

Koliko graf ima stablenih grana?




Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. 0
-50.0%			b. 1
-50.0%			c. 2
100.0%	▶	▶	d. 3
-50.0%			e. 4

Score: 10 / 10

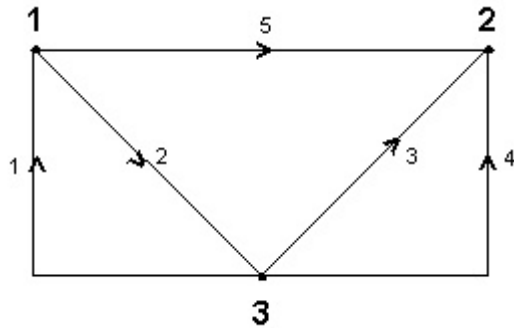Question 5 (10 points)

Kako glasi matrica incidencije za zadani graf? (2,3 grane stabla)



Student response:

Percent Value	Correct Response	Student Response	Answer Choices
100.0%			a. $\begin{bmatrix} -1 & 1 & 0 & 0 & 1 \\ 0 & 0 & 1 & -1 & -1 \\ 1 & -1 & -1 & 1 & 0 \end{bmatrix}$
-50.0%			b. $\begin{bmatrix} 1 & 1 & 0 & 0 & -1 \\ 0 & 0 & 1 & 1 & -1 \\ 0 & 0 & 1 & 1 & -1 \end{bmatrix}$
-50.0%			c. $\begin{bmatrix} 1 & -1 & 0 & 0 & -1 \\ 0 & 0 & -1 & 1 & 1 \\ -1 & 1 & 1 & -1 & 0 \end{bmatrix}$
-50.0%			d. $\begin{bmatrix} 1 & 0 & -1 & -1 & 0 \\ -1 & -1 & 0 & 1 & 1 \\ 0 & 1 & 1 & 0 & -1 \end{bmatrix}$

Score: -5 / 10

### Question 1 (10 points)

Matricna jednadzba KZN glasi:

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. $A \cdot I_b(s) = 0$
100.0%			b. $B \cdot U_b(s) = 0$
-50.0%			c. $A \cdot U_b(s) = 0$
-50.0%			d. $B \cdot I_b(s) = 0$



Score: 10 / 10



**Question 2** (10 points)

Grana bez čvorova može biti graf.

Student response:



Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. točno
100.0%			b. netočno

Score: 10 / 10

**Question 3** (10 points)

Osnovni tip algebarskih jednažbi mreža u matričnoj formi je:


Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. samo opće jednažbe petlji
-50.0%			b. samo opće jednažbe čvorova
100.0%			c. opće jednažbe petlji i čvorova
-50.0%			d. ne postoji osnovni tip

Score: 10 / 10

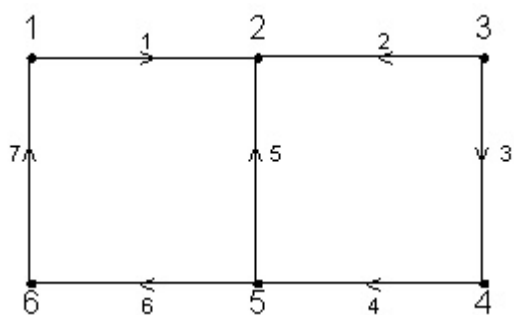**Question 4** (10 points)

Kako glasi spojna matrica grafa ako su 5 i 7 spone?




Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. $\begin{bmatrix} 1 & 1 & 1 & 1 & 0 & 1 \\ -1 & & & & & \\ 0 & -1 & 1 & 1 & 1 & 0 \\ -1 & & & & & \end{bmatrix}$
-50.0%			b. $\begin{bmatrix} -1 & -1 & 1 & 1 & 0 \\ 0 & 1 & & & \\ 0 & 1 & 1 & -1 & -1 \\ 0 & 1 & & & \end{bmatrix}$
-50.0%			c. $\begin{bmatrix} 1 & -1 & -1 & -1 & 0 & 1 \\ 1 & & & & & \\ 0 & -1 & 1 & 1 & 1 & 0 \\ 0 & & & & & \end{bmatrix}$
100.0%			d. $\begin{bmatrix} 1 & -1 & 1 & 1 & 0 & 1 \\ 1 & & & & & \\ 0 & -1 & 1 & 1 & 1 & 0 \\ 0 & & & & & \end{bmatrix}$

Score: 10 / 10
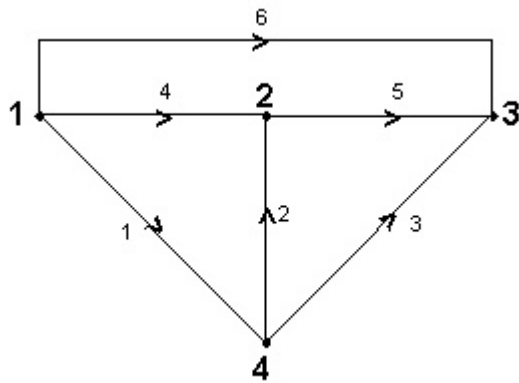
### Question 5 (10 points)

Kako glasi matrica incidencije za zadani graf?



Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. $\begin{bmatrix} 1 & 0 & 0 & 1 & 0 & - \\ 1 & & & & & \\ 0 & 1 & 0 & -1 & 1 & \\ 0 & & & & & \\ 0 & 0 & -1 & 0 & -1 & \\ 1 & & & & & \\ -1 & -1 & 1 & 0 & 0 & \\ 0 & & & & & \end{bmatrix}$
100.0%			b. $\begin{bmatrix} 1 & 0 & 0 & 1 & 0 & \\ 1 & & & & & \\ 0 & -1 & 0 & -1 & 1 & \\ 0 & & & & & \\ 0 & 0 & -1 & 0 & -1 & - \\ 1 & & & & & \\ -1 & 1 & 1 & 0 & 0 & \\ 0 & & & & & \end{bmatrix}$
-50.0%			c. $\begin{bmatrix} -1 & 0 & 0 & -1 & 0 & \\ 1 & & & & & \\ 0 & -1 & 0 & 1 & 1 & \\ 0 & & & & & \\ 0 & 0 & 1 & 0 & -1 & - \\ 1 & & & & & \\ -1 & 1 & 1 & 0 & 0 & \\ 1 & & & & & \end{bmatrix}$
-50.0%			d. $\begin{bmatrix} -1 & 0 & 0 & -1 & 0 & - \\ 1 & & & & & \\ 0 & 1 & 0 & 1 & -1 & \\ 1 & & & & & \\ 0 & 0 & 1 & 0 & 1 & \\ 1 & & & & & \\ -1 & -1 & -1 & 0 & 0 & \\ 0 & & & & & \end{bmatrix}$

Score:

10 / 10

**Question 1** (10 points)

Zadana je mreža koja se sastoji od izvora i tri otpora spojena u paralelu te su postavljene tri linearno nezavisne jednačbe KZS. Promjenom smjera jedne (bilo koje) konturne struje, koliko linearno nezavisnih jednačbi mijenja svoj izraz ?

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. 1
50.0%			b. 2
50.0%			c. 3
-50.0%			d. nijedna

Score: 10 / 10

**Question 2** (10 points)

Da li prilikom rješavanja mreže uzimamo u obzir zavisne izvore?

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. ne, njih naknadno uvrstavamo
-50.0%			b. ako postoje zavisni strujni izvori, tada mrežu ne možemo riješiti pomoću KZN ili KZS
-50.0%			c. samo ako mrežu rješavamo korištenjem KZN
-50.0%			d. samo ako mrežu rješavamo korištenjem KZS
100.0%			e. da, opisujemo ih pomoću parametara o kojima ovise

Score: 10 / 10

### Question 3 (10 points)

Od koliko čvorova se sastoji mreža sa 6 grana ako smo analizom mreže dobili 3 linearno nezavisne jednačbe KZS ?


Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. 5
100.0%	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	b. 4
-50.0%			c. 3
-50.0%			d. 8
-50.0%			e. ne možemo odrediti

Score: 10 / 10

### Question 4 (10 points)

Za mrežu na slici vrijedi

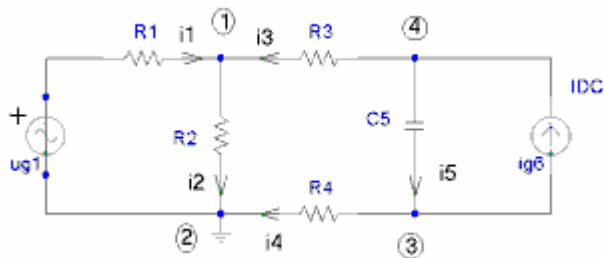


Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. $uv_3/R_4 - C_5 \frac{d(uv_4 - uv_3)}{dt} - ig_6 = 0$
100.0%	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	b. $-(uv_1 - ug_1)/R_1 + uv_1/R_2 - (uv_4 - uv_1)/R_3 = 0$
-50.0%			c. $uv_3/R_4 - C_5 (uv_4 - uv_3) + ig_6 = 0$
-50.0%		<input checked="" type="checkbox"/>	d. $uv_3/R_4 - C_5 \frac{d(uv_4 - uv_3)}{dt} + ig_6 = 0$

Score: -5 / 10
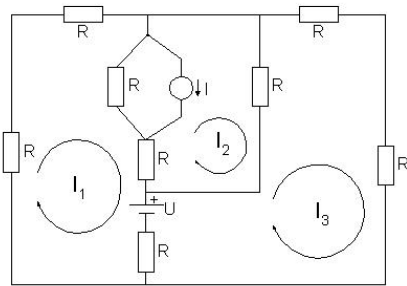
### Question 5 (10 points)

Postavi jednađzbu prve i druge petlje mreže na slici.



- a)  $5RI_1 - 2RI_2 - I_3R = -U + IR$   
 $-2RI_1 + 3RI_2 - I_3R = -IR$
- b)  $5RI_1 - 2RI_2 - I_3R = -U + IR$   
 $-2RI_1 + 3RI_2 - I_3R = IR$
- c)  $5RI_1 - 2RI_2 - I_3R = +U - IR$   
 $-2RI_1 + 3RI_2 - I_3R = -IR$
- d)  $5RI_1 - 2RI_2 - I_3R = -U + IR$   
 $2RI_1 - 3RI_2 - I_3R = IR$

Student response:

Percent Value	Correct Response	Student Response	Answer Choices	
100.0%	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	a.	a)
-50.0%	<input type="checkbox"/>	<input type="checkbox"/>	b.	b)
-50.0%	<input type="checkbox"/>	<input type="checkbox"/>	c.	c)
-50.0%	<input type="checkbox"/>	<input type="checkbox"/>	d.	d)





Score: 10 / 10

### Question 1 (10 points)

je vektor pocetnih napona na kapacitetima s elementom :

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
33.4%	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	a. u j-tom redu, ako j-ta grana u mrezi ima

			kapacitet s pocetnim naponom $u_{cj}(0)$
33.3%			b. pozitivnim, ako se njegov polaritet podudara sa polaritetom j-te grane u grafu
33.3%			c. negativnim, ako je njegov polaritet suprotan od polariteta j-te grane u grafu
-50.0%			d. niti jedan odgovor nije točan



Score: 10 / 10

### Question 2 (10 points)

Linearni graf je suvisao ili povezan, ako se svakom paru čvorišta grafa koja nisu identična, može pridružiti otvoren put tako da je jedno čvorište toga para početno, a drugo završno čvorište puta.

Da li je definicija točna?

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
100.0%			a. da
-50.0%			b. ne

Score: 10 / 10

### Question 3 (10 points)

Osnovni tip algebarskih jednažbi mreža u matricnoj formi je:

Student response:


Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. samo opće jednažbe petlji
-50.0%			b. samo opće jednažbe

			čvorova
100.0%	▶	▶	c. opće jednađžbe petlji i čvorova
-50.0%			d. ne postoji osnovni tip

Score: 10 / 10

#### Question 4 (10 points)

Kako glasi spojna matrica grafa?

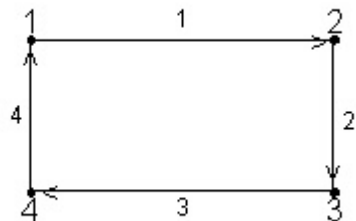

Student response:


Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. 1 1 -1 -1
-50.0%			b. 1 -1 1 1
50.0%	▶	▶	c. 1 1 1 1
50.0%	▶	▶	d. -1 -1 -1 -1
-50.0%			e. 0 0 0 0

Score: 10 / 10
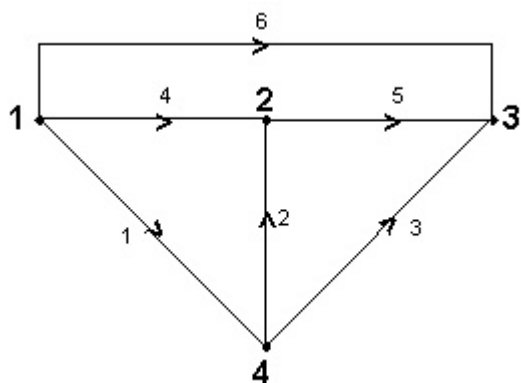
#### Question 5 (10 points)

Koliko ima temeljnih petlji u zadanom grafu?





Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. 1
-50.0%			b. 2
100.0%	▶	▶	c. 3
-50.0%			d. 4
-50.0%			e. 5

Score: 10 / 10

### Question 1 (10 points)

Koliko iznosi broj linearno nezavisnih jednadžbi napona u mreži sa 5 čvorova?

Student response:



Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. 4
-50.0%			b. 5
100.0%	▶	▶	c. ne može se odrediti bez poznavanja broja grana u mreži
-50.0%			d. 3
-50.0%			e. ne može se odrediti bez poznavanja topološke strukture mreže

Score: 10 / 10

### Question 2 (10 points)

Koliko iznosi najveći broj linearno nezavisnih jednažbi KZS za mrežu od  $N_b$  grana i  $N_v$  čvorova?

Student response:



Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. $N_b - (N_v + 1)$
-50.0%			b. $N_b - N_v$
100.0%			c. $N_v - 1$
-50.0%			d. $N_b - (N_v - 1)$
-50.0%			e. $N_v - (N_b - 1)$

Score: 10 / 10

### Question 3 (10 points)

Otpor  $R$  u grani neke mreže priključen je na čvorove  $A$  i  $B$ . Čvor  $B$  je na većem potencijalu od čvora  $A$ , a pretpostavljeni smjer struje kroz granu je od čvora  $A$  prema čvoru  $B$ . Izraz za opis struje  $I_r$  je:


Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. $I_r = (U_b - U_a)/R$
-50.0%			b. $I_r = -(U_b + U_a)/R$
100.0%			c. $I_r = (U_a - U_b)/R$
-50.0%			d. $I_r = (U_b + U_a)/R$

Score: 10 / 10

### Question 4 (10 points)

Da li su ove sheme dualne?

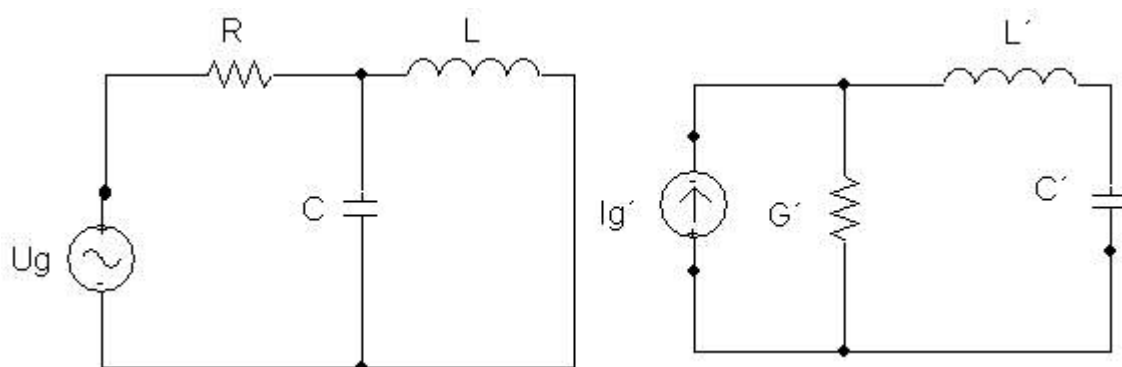


Student response:

Percent Value	Correct Response	Student Response	Answer Choices
100.0%	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	a. Da
-50.0%	<input type="checkbox"/>	<input type="checkbox"/>	b. Ne

Score: 10 / 10
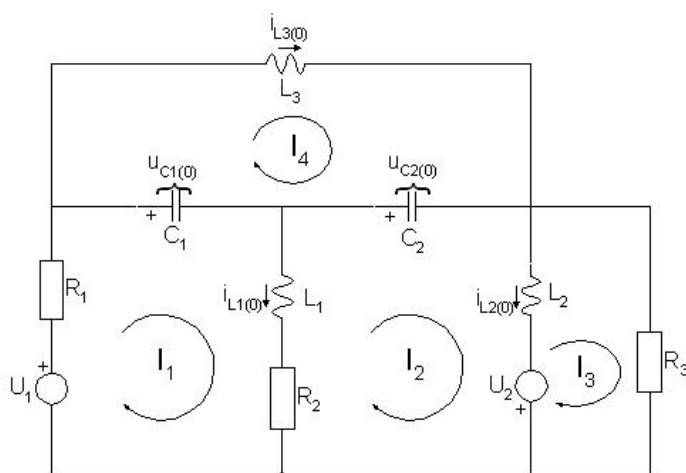
### Question 5 (10 points)

Postavi jednađzbu treće petlje mreže na slici.



a) Točan odgovor nije ponuđen

b)  $L_2 \frac{d}{dt} [i_3(t) - i_2(t)] + i_3(t)R_3 - u_2(t) = 0$

c)  $L_2 \frac{d}{dt} [i_3(t) + i_2(t)] + i_3(t)R_3 - u_2(t) = 0$

d)  $-L_2 \frac{d}{dt} [i_3(t) + i_2(t)] - i_3(t)R_3 + u_2(t) = 0$

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
100.0%			a. a)
-50.0%			b. b)
-50.0%			c. c)
-50.0%			d. d)

Score: 10 / 10

---

### Question 1 (10 points)

KZN u matričnoj normi glasi:

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
100.0%			a. $U_b(s) = U_g(s) + Z_b(s) * I_b(s) + u_c(0)/s - L_b * i_b(0)$
-50.0%			b. $U_b(s) = U_g(s) + Z_b(s) * I_b(s)$
-50.0%			c. $U_b(s) = U_g(s) + Z_b(s) * I_b(s) + u_c(0)/s$
-50.0%			d. $0 = U_g(s) + Z_b(s) * I_b(s) + u_c(0)/s - L_b * i_b(0)$

Score: 10 / 10

### Question 2 (10 points)

Linearni graf je suvisao ili povezan, ako se svakom paru čvorišta grafa koja nisu identična, može pridružiti otvoren put tako da je jedno čvorište toga para početno, a drugo završno čvorište puta.

Da li je definicija točna?

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
---------------	------------------	------------------	----------------

100.0%			a.	da
-50.0%			b.	ne

Score: 10 / 10

### Question 3 (10 points)


Pišući KZN za neku mrežu, pišemo sistem linearnih jednažbi za sve petlje. Što su varijable, a što koeficijenti?

Student response:	Percent Value	Correct Response	Student Response	Answer Choices
	-50.0%			a. varijable su struje petlji, koeficijenti 1, -1, 0
	100.0%			b. varijable su naponi grana, koeficijenti 1, -1, 0
	-50.0%			c. varijable su struje grana, koeficijenti mogu biti bilo koji brojevi
	-50.0%			d. varijable su naponi grana, koeficijenti mogu biti bilo koji brojevi

Score: 10 / 10

### Question 4 (10 points)

Da li je graf planaran?

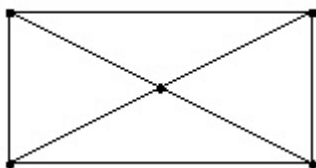


Student response:	Percent	Correct	Student	Answer Choices
-------------------	---------	---------	---------	----------------

Value	Response	Response	
100.0%			a. Da
-50.0%			b. Ne

Score: 10 / 10
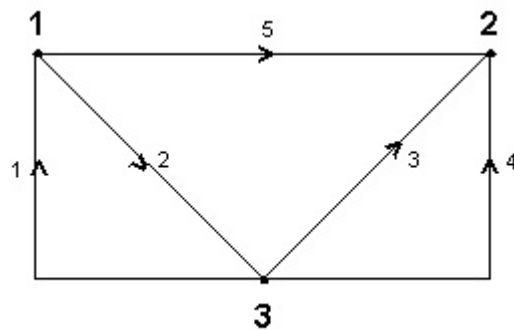
#### Question 5 (10 points)

Kako glasi spojna matrica? (1,4,5 su spone)



Student response:



Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. $\begin{bmatrix} -1 & -1 & 0 & 0 & 0 \\ 0 & 0 & -1 & -1 & 0 \\ 0 & 1 & -1 & 0 & -1 \end{bmatrix}$
-50.0%			b. $\begin{bmatrix} 1 & 1 & 0 & 0 & 0 \\ 0 & 0 & 1 & 1 & 0 \\ 0 & -1 & 1 & 0 & 1 \end{bmatrix}$
-50.0%			c. $\begin{bmatrix} 0 & 0 & 1 & 1 & 1 \\ 1 & 1 & -1 & -1 & 1 \\ 1 & 0 & 1 & 0 & 1 \end{bmatrix}$
100.0%			d. $\begin{bmatrix} 1 & 1 & 0 & 0 & 0 \\ 0 & 0 & 1 & -1 & 0 \\ 0 & 1 & 1 & 0 & -1 \end{bmatrix}$

Score: 10 / 10

#### Question 4 (10 points)

U mreži sa 4 čvora (1, 2, 3 i 4), najjednostavniji sustav jednadzbi KZS za čvorove 1, 2 i 3, dobit ćemo ako

Student response:

Percent Value	Correct Response	Student Response	Answer Choices
-50.0%			a. uzemljimo čvor 1
-50.0%			b. uzemljimo čvor 2
-50.0%			c. uzemljimo čvor 3
100.0%			d. uzemljimo čvor 4
0.0%			e. ne uzemljimo niti jedan čvor

Score: 10 / 10

---